


Complements of Electronics

Exame 14/01/2013 (23/01/2013)

1 Ebers - Moll diode : $I = I_0 \left\{ \exp\left(\frac{eV}{V_T}\right) - 1 \right\}$

Ideal opamp $V_p = V_n$ $\Delta V \approx V_T \ln\left(\frac{I}{I_0}\right)$

A1

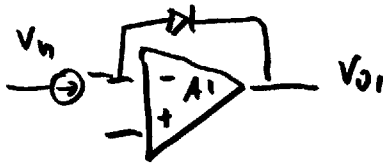


$$V_p = V_i \times \frac{R_1}{R_1 + R_2}$$

$$V_n = V_p = V_i \times \frac{R_1}{R_1 + R_2}$$

$$V_{01} = V_n - \Delta V$$

$$= + V_i \times \frac{R_1}{R_1 + R_2} - V_T \ln\left(\frac{I_{ref}}{I_0}\right)$$

A2

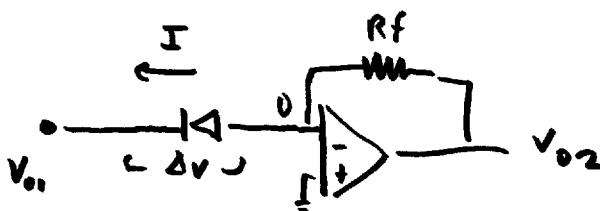

$$\Delta V = 0 - \left(+ V_i \times \frac{R_1}{R_1 + R_2} - V_T \ln\left(\frac{I_{ref}}{I_0}\right) \right)$$

$$I = I_0 \exp\left(\frac{\Delta V}{V_T}\right) = I_0 \exp\left[-\frac{V_i}{V_T} \frac{R_1}{R_1 + R_2} + \frac{V_T}{V_T} \ln\left(\frac{I_{ref}}{I_0}\right)\right]$$

$$= I_0 \exp\left(-\frac{V_i}{V_T} \frac{R_1}{R_1 + R_2}\right) \cdot \exp\left[\ln\left(\frac{I_{ref}}{I_0}\right)\right]$$

$$= I_0 \exp\left(-\frac{V_i}{V_T} \frac{R_1}{R_1 + R_2}\right) \cdot \frac{I_{ref}}{I_0}$$

$$V_{o2} = I \times R_f = R_f \cdot I_{ref} \cdot \exp\left(-\frac{V_i}{V_T} \cdot \frac{R_1}{R_1 + R_2}\right)$$

2 | op amp is ideal

- no current to and from inputs!

$$- V_n = V_p$$

Thus

$$* V_n = V_p = V_i$$


* no current to input $\Rightarrow$ no current through $R_1 \Rightarrow V_3$ (top of R_2) $= V_n = V_i$

$$* \text{Therefore } I_3 = \frac{V_3 - 0}{R_3} = \frac{V_i}{R_3}$$

$$* \beta = \infty \Rightarrow I_c = I_e = I_3 = \frac{V_i}{R_3}$$

$$\boxed{I = \frac{V_i}{R_3}}$$

3 | a) See lecture notes

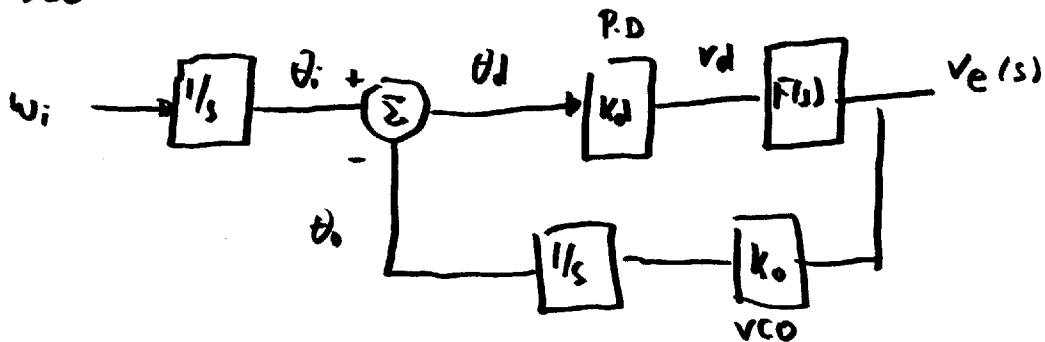

$$\theta_o = (\theta_i(s) - \theta_o(s)) k_d F(s) k_o \cdot \frac{1}{s} \Rightarrow$$

$$H(s) \equiv \frac{\theta_o(s)}{\theta_i(s)} = \frac{k_v F(s)}{s + k_v F(s)} \quad , \quad \text{with } k_v = k_d k_o$$

b) without LPF

$$H(s) = \frac{K_v}{K_v + s} = \frac{1}{1 + s/K_v} \quad (s = j\omega)$$

compares with behavior of a low-pass filter

$$\frac{1}{1 + j\omega/\omega_c} \quad \text{with cut-off frequency}$$


$$\omega_c = K_v = K_d K_o = 1 \frac{V}{\text{rad}} \times 2 \frac{\text{kHz}}{V}$$

$$2 \text{ kHz} = 2000 \times 2\pi \text{ rad/s} \Rightarrow$$

$$\omega_c = 2000 \times 2\pi \frac{\text{rad}}{\text{s}} \times \frac{V}{\text{rad}} = 4000\pi \text{ Hz}$$

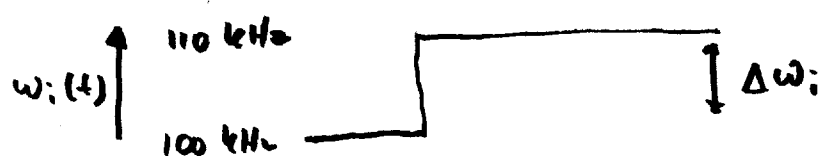c) $\frac{V_e(s)}{w_i(s)} = \frac{1}{K_o} H(s)$, because $\theta_i(s) = \frac{w_i(s)}{s}$, and $\theta_o(s) = \frac{V_e K_o}{s}$

$$= \frac{1/K_o}{1 + s/K_v} \quad \left. \vphantom{\frac{1/K_o}{1 + s/K_v}} \right\} \begin{array}{l} \text{again, like a LPF!} \\ \text{(with DC gain } 1/K_o) \end{array}$$




From circuit analysis, we know that the response of a LPF to a step function in time is a exponential approximation



$$\tau = 'RC' = 1/\omega_c = 1/k_v = \frac{1}{4000\pi} \text{ s}$$

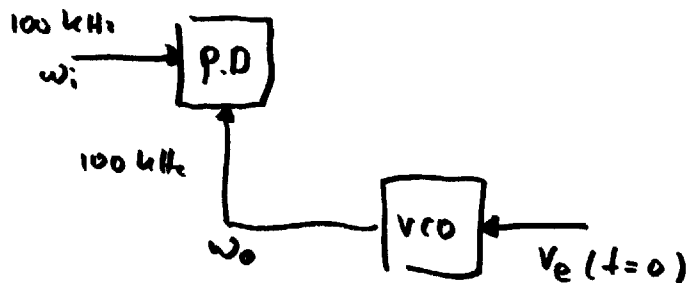
$v_e(t=0)$: given the fact that $\omega_o = \omega_i$ (we have lock), the PLL looks like this:



$$\text{VCO: } \omega_o = 100 \text{ kHz} + \frac{2 \text{ kHz}}{V} \times v_e = 100 \text{ kHz}$$

$$\text{thus } v_e = 0$$

$v_e(t=\infty)$: We again have lock

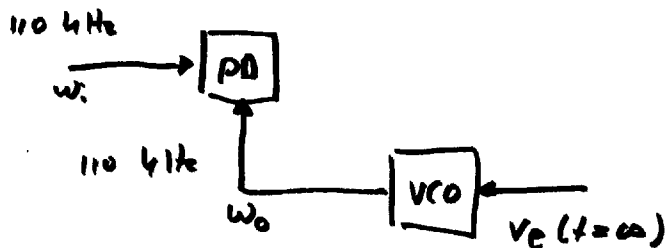

$$\omega_o = 100 \text{ kHz} + \frac{2 \text{ kHz}}{V} \times v_e = 110 \text{ kHz}$$

$$\text{thus } v_e = 5 \text{ V}$$

Δv_e can also be found by using the DC gain of the filter-like behavior,

$$\begin{aligned} \Delta v_e &= \frac{1}{K_o} \times \Delta \omega_i = \frac{1}{2} \frac{V}{\text{kHz}} \times 10 \text{ kHz} \\ &= 5 \text{ V} \end{aligned}$$

d) From electronics II we know about stability⁵ of feedback systems. For negative feedback systems like ours (note the $\oplus \ominus$ part) the transfer function was

$$\frac{v_o}{v_i} = \frac{A}{1 + A\beta}$$


and this meant analyzing $A\beta$ and see if it was equal to -1 (B.C.) or smaller, etc.

$A\beta$ in our case is

$$A\beta = K_d F(s) K_o \cdot \frac{1}{s}$$

without filter :
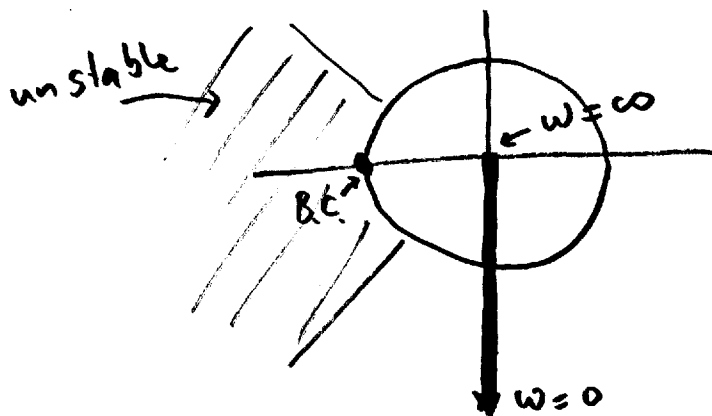
$$\begin{aligned} A\beta &= K_d K_o / s \\ &= \frac{K_d K_o}{j\omega} \end{aligned}$$




stable !

Now add a low-pass filter

$$A\beta = \frac{K_d K_o}{s (1 + s/\omega_c)} = \frac{K_d K_o}{j\omega (1 + j\omega/\omega_c)}$$

with $\omega_c = \frac{1}{\tau} = \frac{1}{RC} = \frac{1}{10^{-6} \text{ s}}$
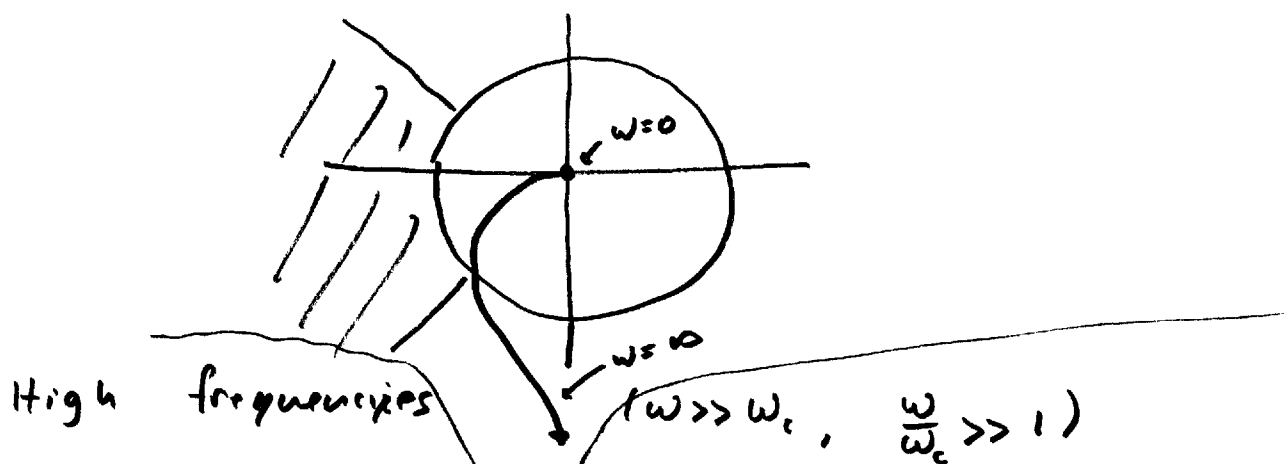
$$A\beta = \frac{k_d k_o}{j\omega - \omega^2/\omega_c}$$



$$A\beta \approx \frac{k_d k_o}{-\omega^2/\omega_c} = -0 \quad (\text{real and negative})$$

($\phi = 180^\circ$)


Low frequencies $(\omega < \omega_c, \frac{\omega}{\omega_c} \ll 1, 1 + j\frac{\omega}{\omega_c} \approx 1)$

$$A\beta \approx \frac{k_d k_o}{j\omega} = -j\infty \quad (\phi = -90^\circ)$$

This is potentially not stable, since it can enter the danger zone. Yet, too complicated to analytically solve in this exam. Make a matlab simulation.

4] See lecture notes

P.D type I is a XOR port

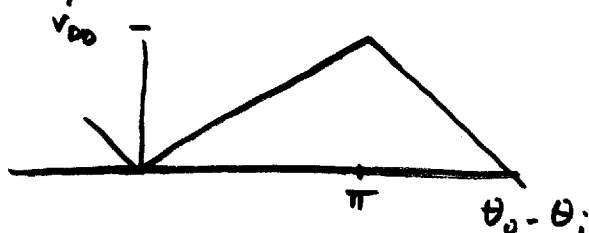

$$k_o = \frac{V_{DD}}{\pi}$$