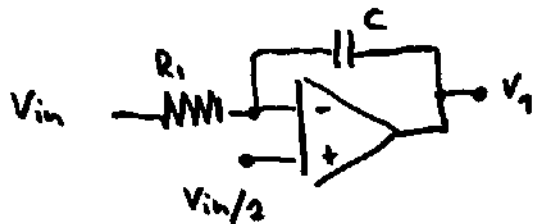


Electronic Complements

23/01/2014

1] The transistor works as an ideal switch. Open circuit or Short circuit to ground. (OC or SC)

The left opamp is an integrator. If T is OC:




$V_n = V_p = \frac{V_{in}}{2}$. The voltage drop over R_1 is thus $\frac{V_{in}}{2}$.
and with Ohm's Law $I_i = \frac{V_{in}}{2R_1}$. This current flows into C and charges it. $V_1 = V_n - \frac{Q_c}{C} = \frac{V_{in}}{2} - \frac{\int V_{in} dt}{2R_1 C} + K$

$$= V_{00} = \frac{V_{in} t}{2R_1 C} \quad \text{a linearly dropping signal}$$

yet to be determined.

when T is SC:

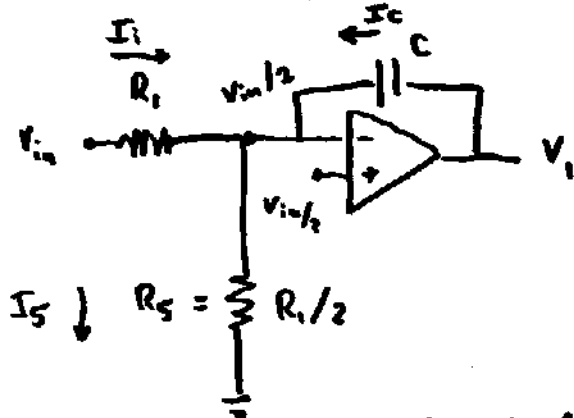

$V_n = V_p = \frac{V_{in}}{2}$. A current flows

through R_1 equal to $I_i = \frac{V_{in}}{2R_1}$

Through R_5 flows a current

$$I_s = \frac{V_{in}/2}{R_5} = \frac{V_{in}/2}{R_1/2} = \frac{V_{in}}{R_1}$$


Kirchoff: $I_c = I_s - I_i = \frac{V_{in}}{R_1} - \frac{V_{in}}{2R_1} = \frac{V_{in}}{2R_1}$

This current is pulled out of C which is thus discharged.

In fact, discharged with the same speed.

$$V_i = V_{ii} + \frac{V_{in} t}{2 R_1 C} \quad (V_{ii} \text{ to be determined})$$


The second opamp implements hysteresis

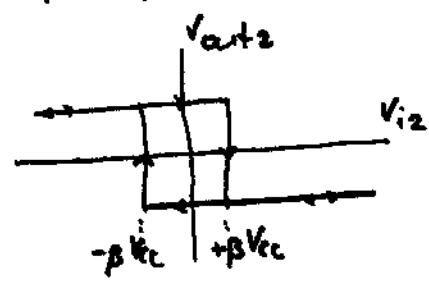

$$\beta = \frac{R_6}{R_6 + R_7}$$

Combined: The circuit charges and discharges C linearly and periodically.

b)

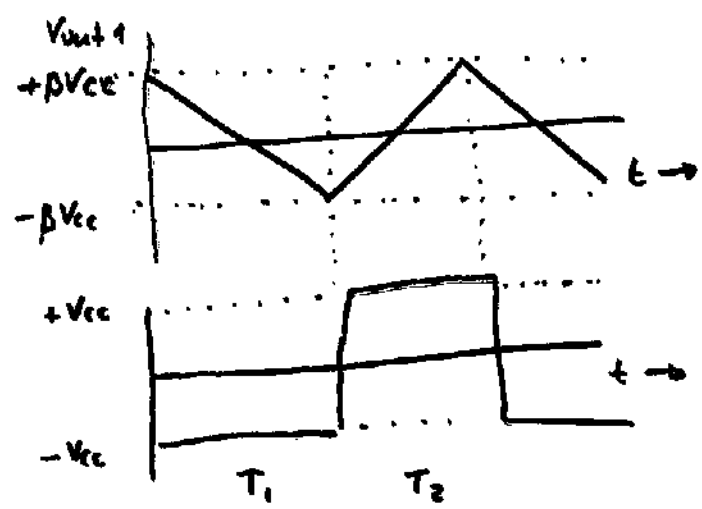

Note: $V_{ou} = +\beta V_{cc}$
 $V_{ii} = -\beta V_{cc}$

c) A half cycle T_1 is when V_{out1} goes from $+\beta V_{cc}$ to $-\beta V_{cc}$:


$$\frac{V_{in} T_1}{2 R_1 C} = 2 \beta V_{cc} \Rightarrow T_1 = \frac{4 \beta V_{cc} R_1 C}{V_{in}}$$

the same for T_2 ($T_2 = T_1$) . Thus

$$f = \frac{1}{T_1 + T_2} = \frac{1}{2 T_1} = V_{in} \cdot \frac{1}{8 \beta V_{cc} R_1 C}$$

2]

3

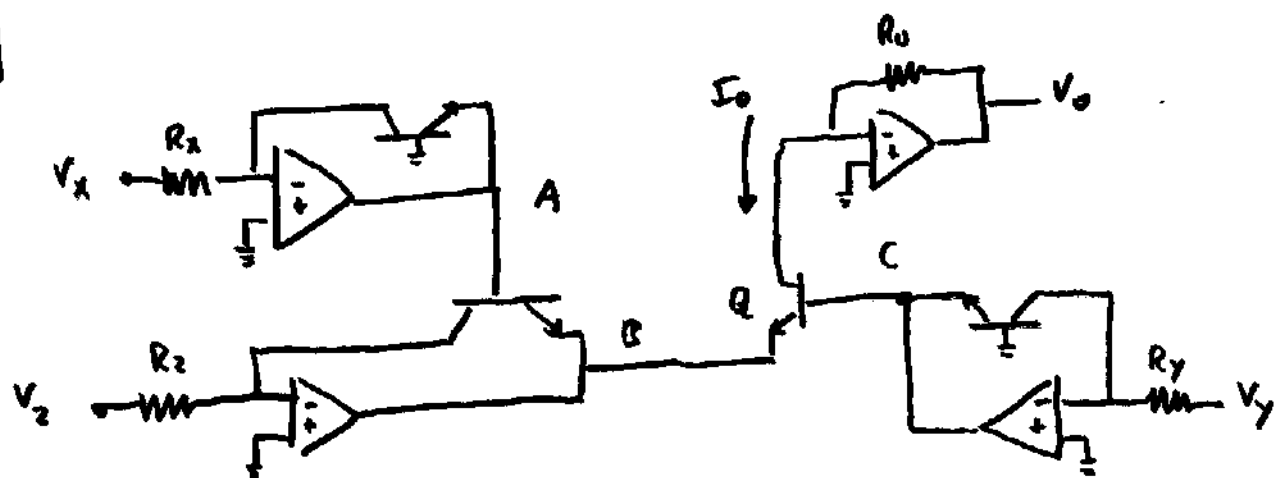

a) All voltages positive $V_x > 0, V_y > 0, V_z > 0$, 1 octant

Ebers Moll (simplified): $V_{BE} = V_T \ln \left(\frac{I_c}{I_{os}} \right)$

$$V_A = -V_T \ln \left(\frac{V_x}{R_x} \cdot \frac{1}{I_{os}} \right)$$

$$V_B = V_A - V_T \ln \left(\frac{V_z}{R_z} \cdot \frac{1}{I_{os}} \right) = -V_T \ln \left(\frac{1}{I_{os}} \cdot \left[\frac{V_x}{R_x} * \frac{V_z}{R_z} \right] \right)$$

$$V_C = -V_T \ln \left(\frac{V_y}{R_y} \cdot \frac{1}{I_{os}} \right)$$

$$I_o = \frac{V_o}{R_o}, \quad V_{BEQ} = V_T \ln \left(\frac{V_o}{R_o} \cdot \frac{1}{I_{os}} \right)$$


$$V_B = V_C - V_{BEQ} = -V_T \ln \left(\frac{1}{I_{os}} \left[\frac{V_y}{R_y} * \frac{V_o}{R_o} \right] \right)$$

$$-V_T \ln \left(\frac{1}{I_{os}} \left[\frac{V_x}{R_x} * \frac{V_z}{R_z} \right] \right) = -V_T \ln \left(\frac{1}{I_{os}} \left[\frac{V_y}{R_y} * \frac{V_o}{R_o} \right] \right)$$


$$\frac{V_x V_z}{R_x R_z} = \frac{V_y V_o}{R_y R_o} \Rightarrow V_o = \frac{V_x V_z}{V_y} \cdot \frac{R_y R_o}{R_x R_z}$$

3]

(4)

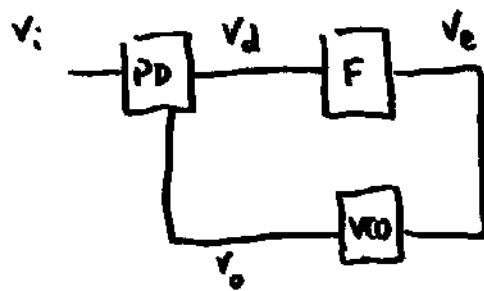

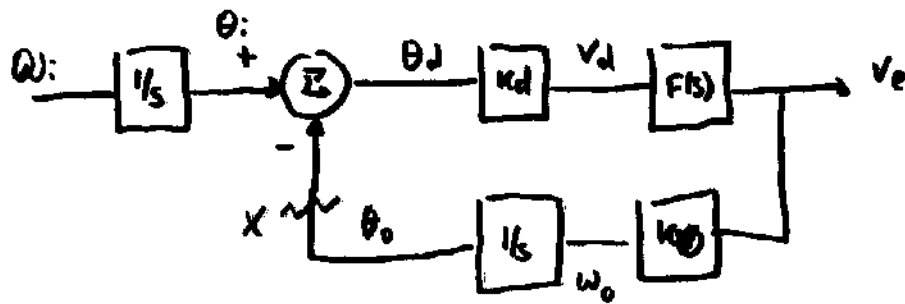a) In Laplace transform of phase, $\theta = \int \omega dt$



Open loop : cut at X, then

$$\theta_o = \frac{1}{s} \times K_O \times F(s) \times K_d \times \theta_i$$

$$T(s) \equiv \frac{\theta_o}{\theta_i} = \frac{K_O K_d F(s)}{s}$$

Closed loop

$$\theta_o = \frac{1}{s} K_O F(s) K_d (\theta_i - \theta_o)$$

$$H(s) \equiv \frac{\theta_o}{\theta_i} = \frac{T(s)}{1 + T(s)} = \frac{K_O K_d F(s)}{s + K_O K_d F(s)}$$


b) $F(s) = 1$

$$H(s) = \frac{K_v}{s + K_v} = \frac{1}{1 + s/K_v} \quad K_v = K_O K_d$$

$$\tau = \frac{1}{K_v} = \frac{1}{1V \times 2444r/V} = \frac{1}{2000} s = 0.5 \text{ ms}$$


(Behaves like filter with $\omega_c = K_v$, or $\tau = 1/K_v$!)

(5)

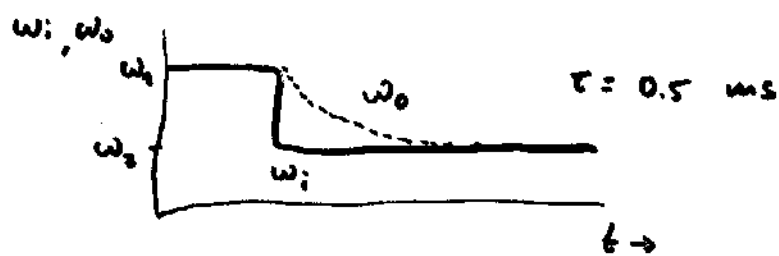

$$\omega_0 = \omega_i + (\omega_1 - \omega_i) e^{-t/\tau}$$


c)

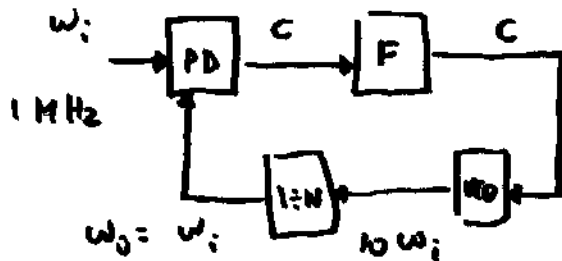lock? $\Rightarrow \omega_0 = \omega_i$

at P.D.

Thus ω at VCO =
 $10 \omega_i$, see figure.

4]

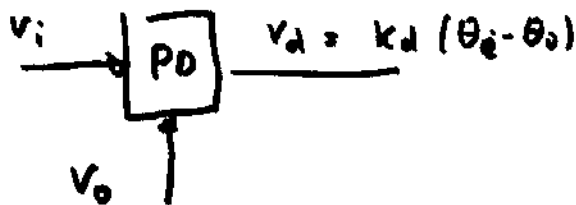

$$v_d = k_d (\theta_i - \theta_o)$$

$$\theta_i = \omega_i t = (\omega + a)t$$


$$\theta_o = \omega_o t = (\omega - a)t$$

$$\theta_i - \theta_o =$$


$$\frac{2at^2}{2at^2}$$


$$v_d = (\theta_i - \theta_o) k_d = 2k_d a t^2$$

(quadratic)

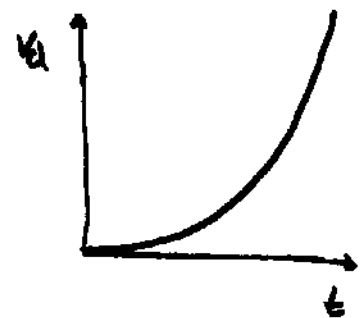


5) See lecture notes

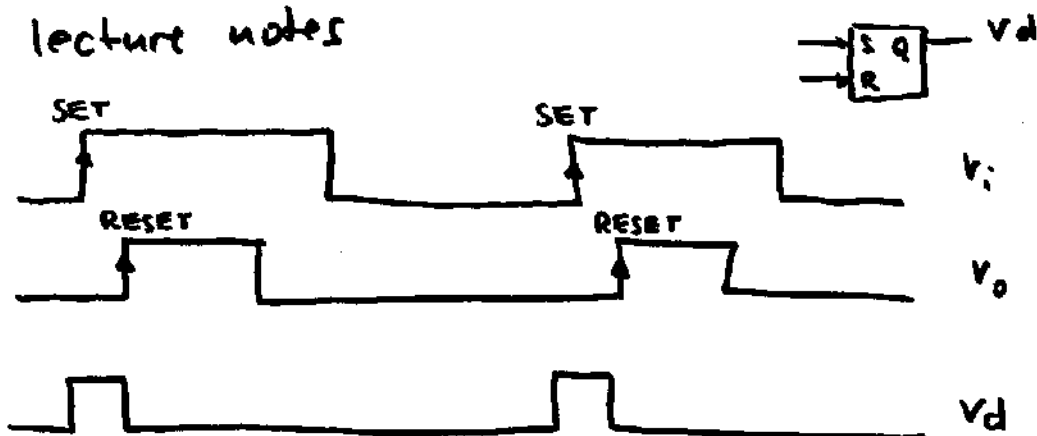

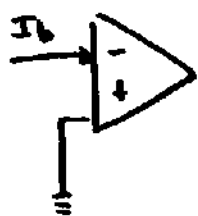

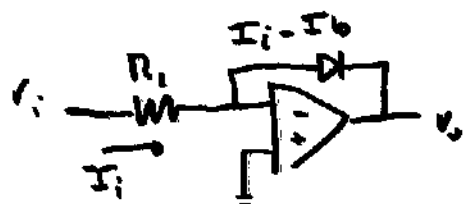A polarizing current I_b enters into the op-amp, making it non-ideal.



$$v_o = V_T \ln \left(\left(\frac{V_i}{R_i} - I_b \right) / I_{S0} \right)$$


Two ways of avoiding:

1: Inject extra current:



$$I_b = I_i + I_b - I_b = I_i$$

2: Add resistance to V_p too:

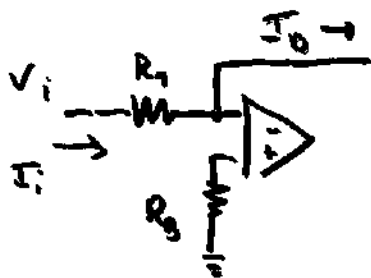

$$V_n = V_p = 0 - I_b R_b$$

$$I_i = \frac{V_i - V_n}{R_i} = \frac{V_i + I_b R_b}{R_i}$$

$$I_o = I_i - I_b = \frac{V_i + I_b R_b}{R_i} - I_b$$

We see that if $R_b = R_i$, then $I_o = \frac{V_i}{R_i}$ as desired.