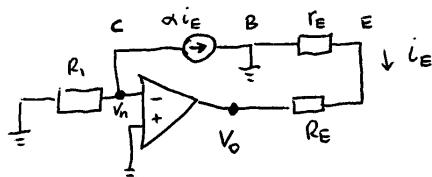


$$(a) I_E = \frac{V_i}{R_i} = \frac{8V}{1k\Omega} = 8mA \quad (V_i = V_{max}!)$$

$$r_E = \frac{V_T}{I_E} = 26mV/8mA = 3.25\Omega$$


determine β : $\beta = \frac{V_o}{V_i}$



$$\text{Vn: } \sum I = 0$$

$$V_n \cdot \frac{1}{R_1} + \alpha i_E = 0, \quad i_E = -\frac{V_o}{R_E}, \quad R_E' = R_E + r_E$$
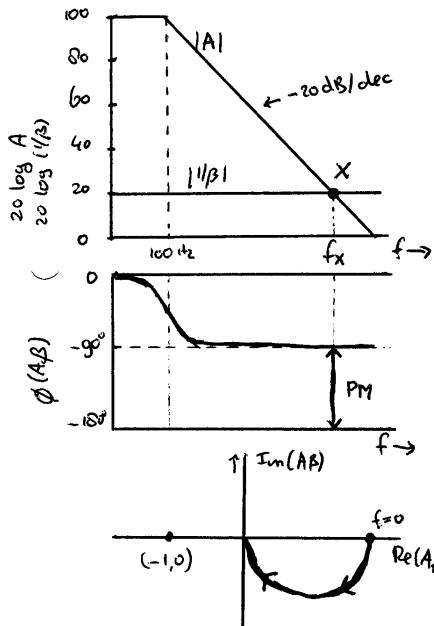
$$\Rightarrow \frac{V_n}{V_o} = \beta = \frac{R_1}{R_E'} = \frac{1k\Omega}{10k\Omega + 3.25\Omega} = \frac{1}{10}, \quad 1/\beta = 10$$



A: 1 polos, $f_p = 100$ Hz

$$A = \frac{A_0}{1+if/f_p}$$

β : 0 poles, $\beta = 0.1$

$$X: |A| = 1/\beta, \quad |AB| = 1$$

$$|A| = \frac{A_0}{1+f_x/f_p}, \quad (f_x > f_c)$$

$$|A| \sim A_0 f_p / f_x$$

$$|AB| = 1 \Rightarrow A_0 f_p / f_x = 10, \Rightarrow f_x = 1MHz$$


$$\phi(f_x) = -\tan^{-1}(f_x/f_p) = -89.99^\circ$$

margem de fase:

$$PM = 180^\circ - 89.99^\circ = 90.01^\circ$$

$PM > 45^\circ \Rightarrow$ estavel

(b)

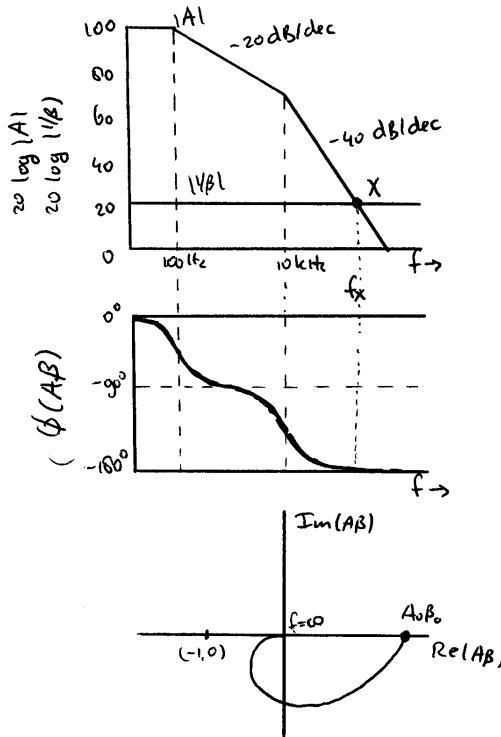

$$\beta = 0.10, \quad \frac{1}{\beta} = 10 \quad 20 \log(1/\beta) = 20 \text{ dB}$$

$$A = \frac{A_0}{(1 + i f/f_{p1})(1 + i f/f_{p2})}$$

$$X: |A\beta| = 1$$

da figura: $\phi(A\beta) \approx -180^\circ$
 \Rightarrow instável

$$\frac{A}{1+A\beta} \approx \frac{A_x}{1+(-1)} = \infty$$

determine f_x :

$$|A(f_x)| = \frac{A_0}{(1 + f_x/f_{p1})(1 + f_x/f_{p2})}$$

$$f_x \gg f_{p2} \gg f_{p1}$$

$$\begin{aligned} |A(f_x)| &= \frac{A_0}{(f_x/f_{p1})(f_x/f_{p2})} \\ &= \frac{A_0 f_{p1} f_{p2}}{f^2} \end{aligned}$$


$$\begin{aligned} |A\beta| = 1 &\Rightarrow f^2 = A_0 f_{p1} f_{p2} \beta \\ &= 10^5 \cdot 100 \cdot 10^4 \cdot 0.1 \end{aligned}$$

$$f = 100 \text{ kHz}$$

$$\begin{aligned} \phi(100 \text{ kHz}) &= -\tan^{-1}(f/f_{p1}) - \tan^{-1}(f/f_{p2}) = -89.94^\circ - 84.29^\circ \\ &= -174.23^\circ \end{aligned}$$

$$PM = 180 - 174.23^\circ = 5.77^\circ \quad (< 45^\circ \Rightarrow \text{não é estável})$$

(c)

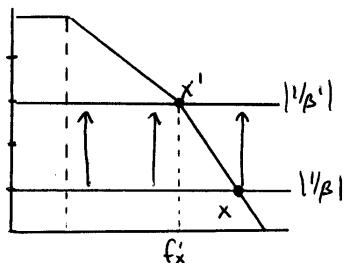


$$\phi(x') = -135^\circ \quad (PM = 45^\circ)$$

$$f_x' = 10 \text{ kHz} \quad (= f_{p2})$$


$$\begin{aligned} A(x') &= \frac{A_0 f_{p1} f_{p2}}{f^2} = \frac{10^5 \cdot 100 \cdot 10^4}{10^4 \cdot 10^4} = 10^3 \\ &\Rightarrow \beta' = 10^3 \quad (A\beta' = 1) \end{aligned}$$

$$\Rightarrow \frac{R_i}{R_E + r_E} = 10^{-3} \Rightarrow R_E = 1 \text{ M}\Omega$$


intermezzo . general description

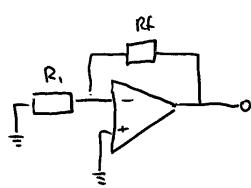

$$\beta = \frac{R_f}{R_i + R_f}$$

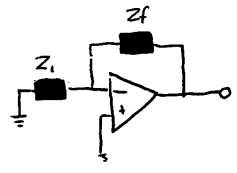

$$\beta = \frac{1/Z_i}{1/Z_i + 1/Z_f}$$

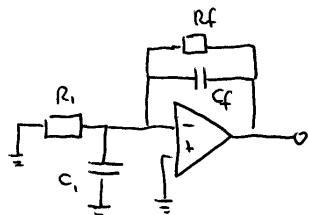

$$Z_i = \frac{1}{R_i} + sC_i$$

$$Z_f = \frac{1}{R_f} + sC_f$$

$$\beta = \frac{\frac{1}{Z_i}}{\frac{1}{Z_i} + \frac{1}{Z_f}} = \frac{\frac{1}{\frac{1}{R_i} + sC_i}}{\frac{1}{\frac{1}{R_i} + sC_i} + \frac{1}{\frac{1}{R_f} + sC_f}} = \frac{\frac{1}{R_f} + sC_f}{\frac{1}{R_f} + sC_f + \frac{1}{R_i} + sC_i}$$

$$= \frac{R_i}{R_i + R_f} \cdot \frac{1 + sR_f C_f}{1 + s(\frac{R_f R_i}{R_i + R_f})(C_i + C_f)}$$

$$\beta_0 = \frac{1}{1}$$

pole at

$$f_p = \frac{1}{2\pi(R_i // R_f)(C_i + C_f)}$$

zero at

$$f_o = \frac{1}{2\pi R_f C_f}$$

$$= 173.3 \text{ kHz}$$

$$R_i = 1 \text{ k}\Omega$$


$$R_f = R_E + r_E = 10 \text{ k}\Omega$$

$$C_i = C_f = 10 \text{ pF}$$


$$C_E = C_c = 1 \text{ nF}$$

example

end of intermezzo

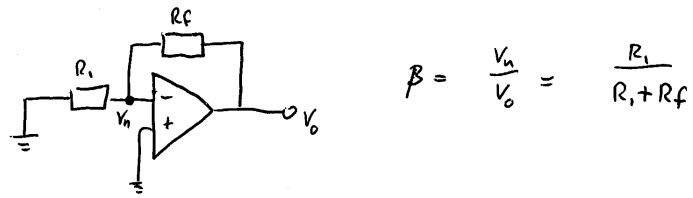

small signal analysis of log. amp.

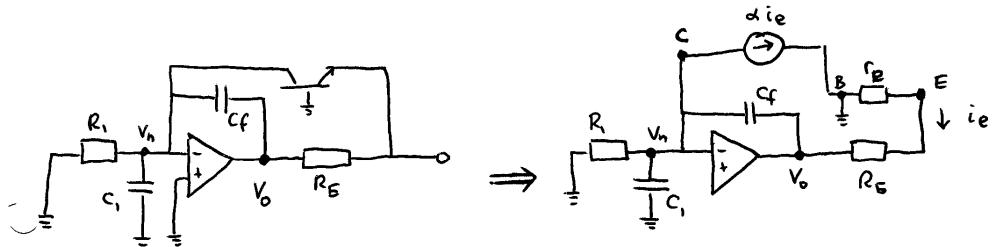

$$i_e = \frac{V_o}{R_E + r_E} = -\frac{V_o}{R_f} \quad R_f = R_E + r_E$$

$$\text{in } V_n : \sum I = 0$$

$$V_n \left(\frac{1}{R_i} + sC_i \right) + \alpha i_e + (V_n - V_o) \cdot sC_f = 0$$

$$V_n \left(\frac{1}{R_i} + sC_i \right) - \alpha \frac{V_o}{R_f} + (V_n - V_o) sC_f = 0 \quad R_f = R_E + r_E$$

$$\beta = \frac{V_n}{V_o} = \frac{\frac{d}{R_f} + sC_f}{\frac{1}{R_i} + sC_i + sC_f} \quad (\alpha=1) \Rightarrow \beta = \frac{R_i}{R_f} \frac{1 + sR_f C_f}{1 + sR_i(C_i + C_f)}$$

pole at $\omega_p = \frac{1}{2\pi R_i(C_i + C_f)}$ zero at $\omega_z = \frac{1}{2\pi R_f C_f}$

$$R_i = 1 k\Omega$$

$$R_f = 10 k\Omega$$

$$C_i = 10 pF$$

$$C_f = 1 nF$$

$$158 \text{ kHz}$$


$$15.9 \text{ kHz}$$

F.P. 3 E-III

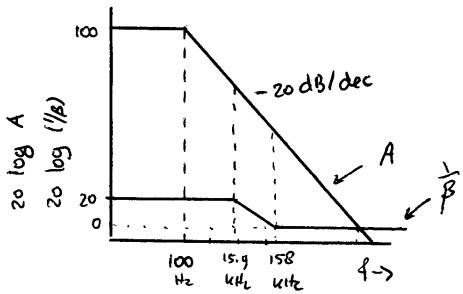
(5)

A: pole at 100 Hz $A_0 = 10^5$

β : pole at 158 kHz $\beta_0 = 0.1$
zero at 15.9 kHz



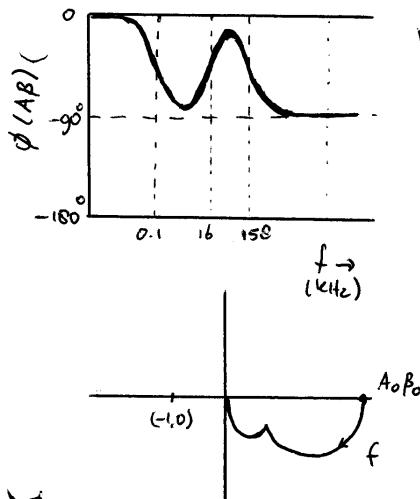
$$\beta(f=\infty) = \frac{R_f}{R_f + R_i} \cdot \frac{R_f}{R_f R_i} \cdot \frac{R_f + R_i}{= 1}$$



$$\forall f: \phi(A\beta) > -90^\circ$$

stable!

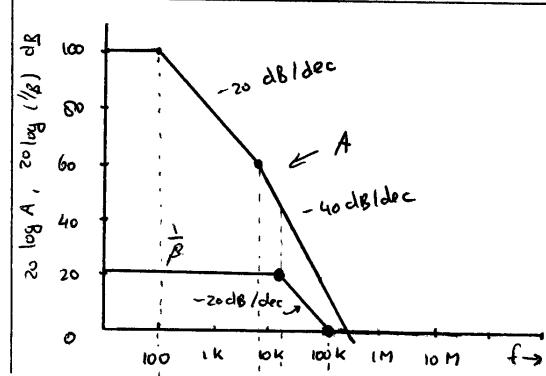


ampop de (b):

A: pole at 100 Hz


pole at 10 kHz

β : pole at 158 kHz

zero at 15.9 kHz

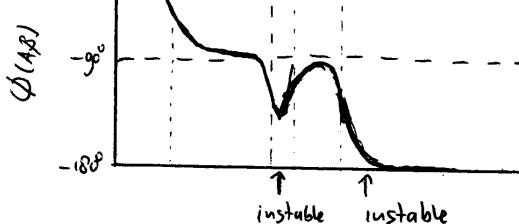

INSTABLE

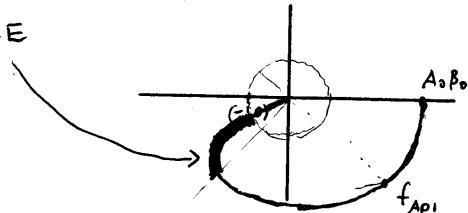

end