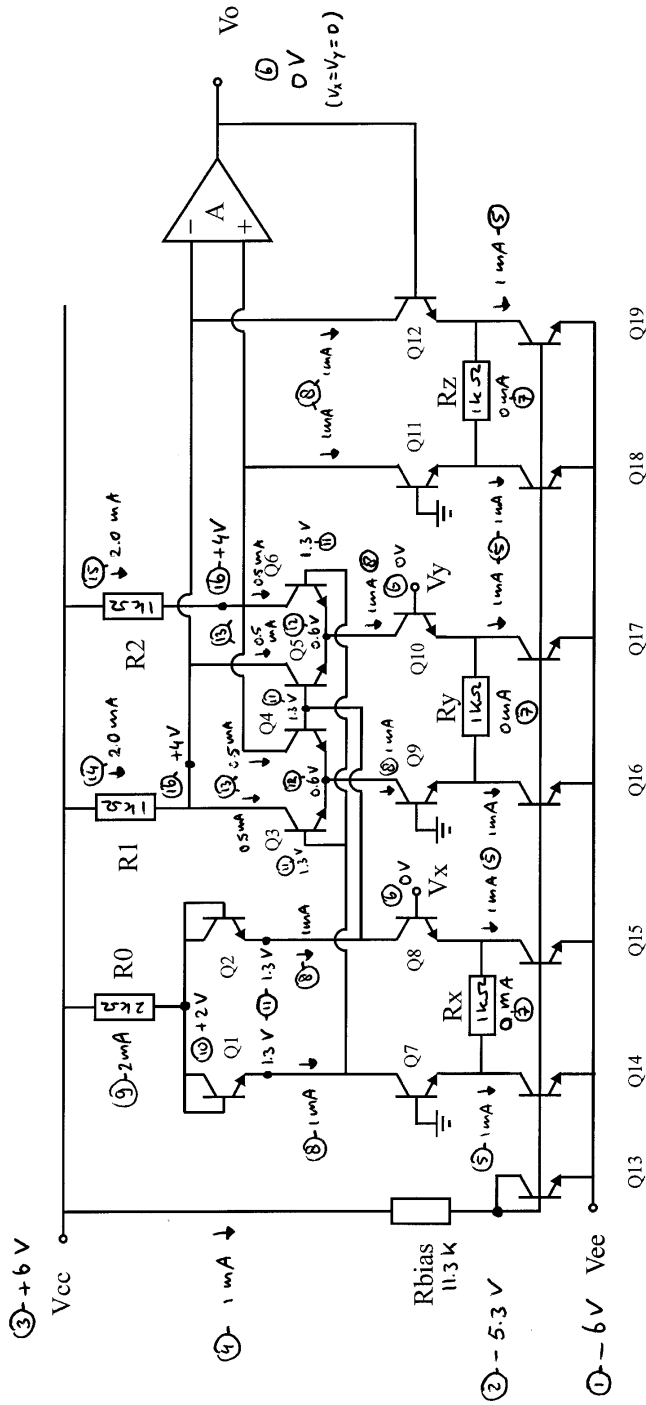


b)





* Polarização / ponto de funcionamento

1c)

$$I_3 - I_4 = \frac{I_3 + I_4}{I_1 + I_2} (I_2 - I_1) \quad \text{III a)}$$
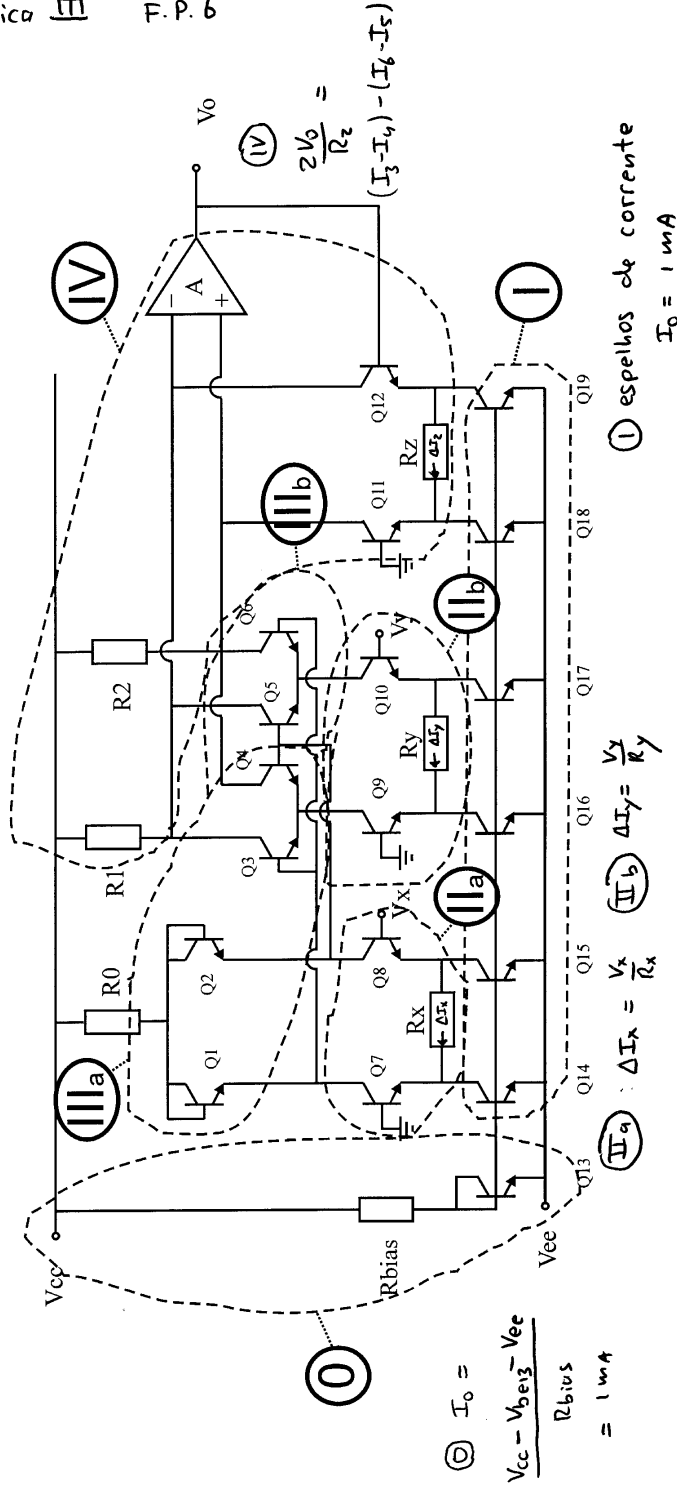
$$I_6 - I_5 = \frac{I_6 + I_5}{I_1 + I_2} (I_2 - I_1) \quad \text{III b)}$$



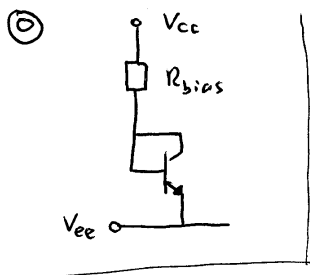

$$V_b = V_c = V_{ee} + 0.7V = -6 + 0.7V = -5.3V$$

$$I_0 = (V_{cc} - V_b) / R_{bias} = \frac{6 - 0.7 + 6V}{11.3k\Omega} = 1\mu A$$

I) 6 x espelho de corrente

$$I_x \equiv I_{14} = I_{15} = I_0 = 1\mu A$$

$$I_y \equiv I_{16} = I_{17} = I_0 = 1\mu A$$


$$I_z \equiv I_{18} = I_{19} = I_0 = 1\mu A$$

IIa) igual a folha de problemas 5

$$\Delta I_x = V_x / R_x$$

$$IIb) \Delta I_y = V_y / R_y$$

IIIa)

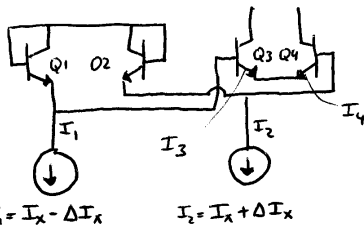

$$I_1 + I_2 = (I_x - \Delta I_x) + (I_x + \Delta I_x)$$

$$= 2 I_x$$

$$I_2 - I_1 = 2 \Delta I_x$$

Malha fechada: $\sum \Delta V = 0$

$$V_{be1} + V_{be3} - V_{be4} - V_{be2} = 0$$

$$V_T \ln \frac{I_1}{I_3} + V_T \ln \frac{I_3}{I_5} - V_T \ln \frac{I_4}{I_5} - V_T \ln \frac{I_2}{I_5} = 0$$

$$\frac{I_1 I_3}{I_4 I_2} = 1$$


$$\frac{I_3}{I_4} = \frac{I_2}{I_1}$$

$$\frac{I_3}{I_4} = \frac{I_2}{I_1}$$


$$\begin{aligned} \frac{I_3}{I_4} - 1 &= \frac{I_2}{I_1} - 1 & \frac{I_3}{I_4} + 1 &= \frac{I_2}{I_1} + 1 \\ \frac{I_3 - I_4}{I_4} &= \frac{I_2 - I_1}{I_1} & \frac{I_3 + I_4}{I_4} &= \frac{I_2 + I_1}{I_1} \\ I_3 - I_4 &= \frac{I_4}{I_1} (I_2 - I_1) & \frac{I_4}{I_1} &= \frac{(I_3 + I_4)}{(I_1 + I_2)} \end{aligned}$$

$$(I_3 - I_4) = \left(\frac{I_3 + I_4}{I_1 + I_2} \right) (I_2 - I_1)$$

III b

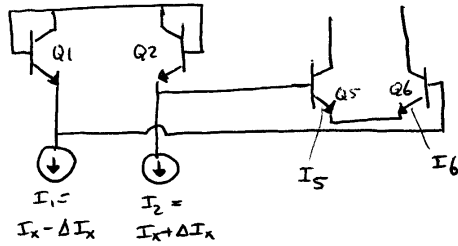


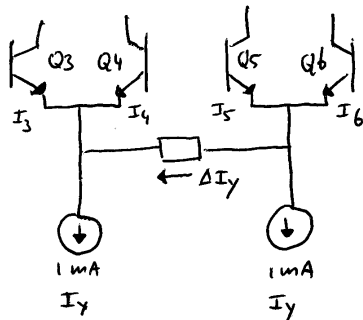
$$(I_6 - I_5) = \left(\frac{I_5 + I_6}{I_1 + I_2} \right) (I_2 - I_1)$$



$$\begin{aligned} I_3 + I_4 &= I_y - \Delta I_y \\ I_5 + I_6 &= I_y + \Delta I_y \\ \left(\begin{aligned} I_1 + I_2 &= 2 I_x \\ I_2 - I_1 &= 2 \Delta I_x \end{aligned} \right) \end{aligned}$$

$$\left. \begin{aligned} (I_3 - I_4) &= \frac{I_7 - \Delta I_7}{2 I_x} \cdot 2 \Delta I_x \\ (I_6 - I_5) &= \frac{I_7 + \Delta I_7}{2 I_x} \cdot 2 \Delta I_x \end{aligned} \right\} \begin{aligned} (I_3 - I_4) - (I_6 - I_5) &= \\ &= - 2 \frac{\Delta I_7}{I_x} \cdot \Delta I_x \end{aligned}$$

IV

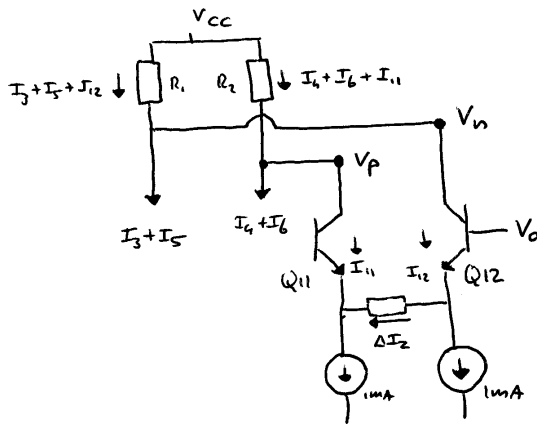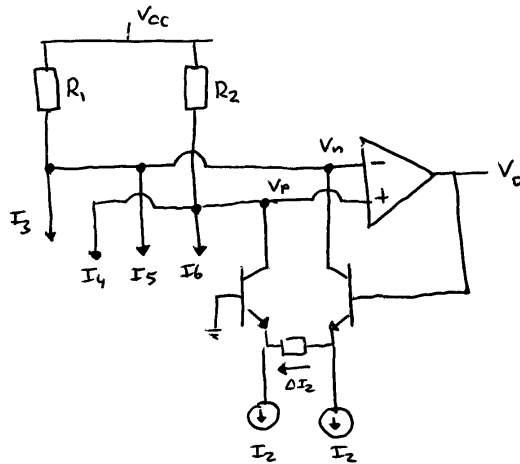

$$\Delta I_2 = \frac{V_o}{R_2}$$

$$\Downarrow$$

$$(I_{11} - I_{12}) = 2 \Delta I_2 = 2 \frac{V_o}{R_2}$$

$$V_n = V_{cc} - (I_3 + I_5 + I_{12}) \cdot R_1$$

$$V_p = V_{cc} - (I_4 + I_6 + I_{11}) \cdot R_2$$

$$R_1 = R_2$$

opamp ideal : $V_n = V_p$

$$V_n = V_p \Rightarrow I_3 + I_5 + I_{12} = I_4 + I_6 + I_{11}$$

$$\Rightarrow (I_3 - I_4) - (I_6 - I_5) = (I_{11} - I_{12})$$

$$\Rightarrow -2 \frac{\Delta I_y}{I_x} \cdot \Delta I_x = 2 \Delta I_z$$

$$\Delta I_y = \frac{V_y}{R_y}, \quad \Delta I_x = \frac{V_x}{R_x}, \quad \Delta I_z = \frac{V_0}{R_z}$$


$$\Rightarrow -\frac{V_y}{R_y} \cdot \frac{1}{I_x} \cdot \frac{V_x}{R_x} = \frac{V_0}{R_z}$$

$$\Rightarrow V_0 = -\frac{R_z}{R_x R_y I_x} \cdot V_x V_y$$

$$R_x = 1k\Omega, \quad R_y = 1k\Omega, \quad R_z = 1k\Omega, \quad I_x = 1mA$$

$$V_0 = -V_x V_y \quad (V)$$

1d:) Veja folha de problemas 5

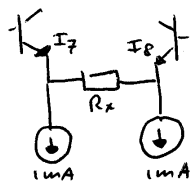


$$I_7 > 0 \text{ e } I_8 > 0 \Rightarrow$$

$$|\Delta I_x| < 1mA$$

$$\left| \frac{V_x}{R_x} \right| < 1mA \quad R_x = 1k\Omega$$


$$-1V < V_x < 1V$$
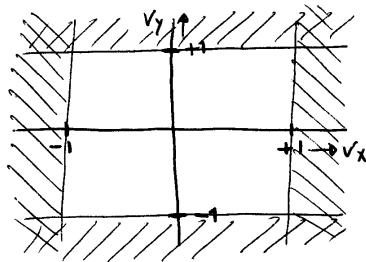
$$V_y: \text{ igual } : \quad -1V < V_y < 1V$$



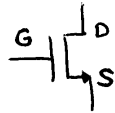2) transistor FET em zona linear/triod:

$$I_D = \beta \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right)$$




(nota: em saturação:

$$I_D = \frac{\beta}{2} (V_{GS} - V_T)^2)$$

$$\left. \begin{aligned} I_{D1} &= \beta_1 \left[(V_{GS} - \frac{V_y}{2} - V_{T1}) \left(\frac{V_x}{2}\right) - \frac{1}{2} \left(\frac{V_x}{2}\right)^2 \right] \\ I_{D2} &= \beta_2 \left[(V_{GS} - \frac{V_y}{2} - V_{T2}) \left(\frac{V_x}{2}\right) - \frac{1}{2} \left(\frac{V_x}{2}\right)^2 \right] \\ I_{D3} &= \beta_3 \left[(V_{GS} + \frac{V_y}{2} - V_{T3}) \left(\frac{V_x}{2}\right) - \frac{1}{2} \left(\frac{V_x}{2}\right)^2 \right] \\ I_{D4} &= \beta_4 \left[(V_{GS} + \frac{V_y}{2} - V_{T4}) \left(\frac{V_x}{2}\right) - \frac{1}{2} \left(\frac{V_x}{2}\right)^2 \right] \end{aligned} \right\} \Rightarrow$$
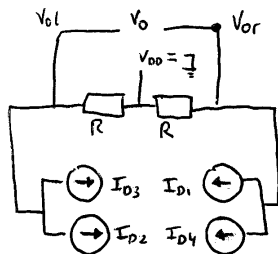
$$\begin{cases} I_{D1} + I_{D4} = \beta \cdot \left[-\frac{V_x V_y}{2} - \frac{V_x V_x}{4} \right] \\ I_{D2} + I_{D3} = \beta \cdot \left[+\frac{V_x V_y}{2} - \frac{V_x V_x}{4} \right] \end{cases} \quad \begin{aligned} \beta_1 &= \beta_2 = \beta_3 = \beta_4 \\ V_{T1} &= V_{T2} = V_{T3} = V_{T4} \end{aligned}$$



modelo pequenas sinais

$$V_{or} = R (I_{D1} + I_{D4})$$

$$V_{ol} = R (I_{D2} + I_{D3})$$

$$V_o = V_{ol} - V_{or} = R (I_{D1} + I_{D4} - I_{D2} - I_{D3})$$

$$= -\beta V_x V_y R$$