
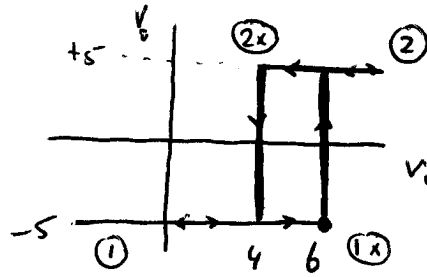


1)

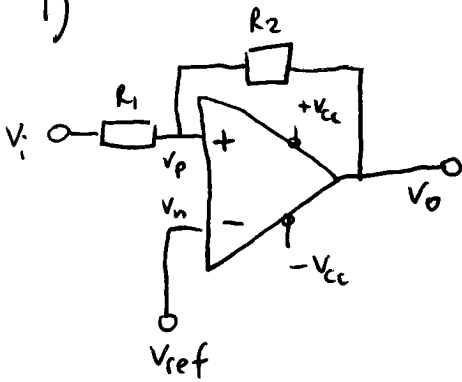

$$-V_{cc} = -5 \text{ V}$$

$$+V_{cc} = +5 \text{ V}$$

① → ①x

$$V_o = -V_{cc} = -5 \text{ V}$$

$$V_n = V_{ref}$$

$$V_p = \frac{R_1}{R_1 + R_2} \cdot V_o + \frac{R_2}{R_1 + R_2} \cdot V_i$$

em ①x:

$$V_p = \frac{R_1}{R_1 + R_2} (-5) + \frac{R_2}{R_1 + R_2} \cdot (6)$$

e tambem (agui!) $V_n = V_p$

① :

$$V_{ref} = \frac{R_1}{R_1 + R_2} (-5) + \frac{R_2}{R_1 + R_2} (6)$$

② → ②x :


$$V_o = +5 \text{ V}, \quad V_n = V_{ref} \dots$$

②

$$V_{ref} = \frac{R_1}{R_1 + R_2} (+5) + \frac{R_2}{R_1 + R_2} (+4)$$

Dois equações, tres variaveis ⇒ muitas soluções

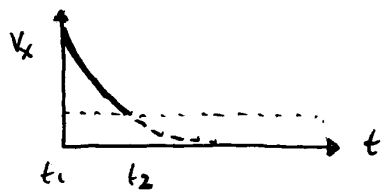exemplo: $R_1 = 1 \text{ k}\Omega$, $R_2 = 5 \text{ k}\Omega$, $V_{ref} = \frac{25}{6} \text{ V}$




tempo de relax : $\tau = RC$ } \Rightarrow
 $t = t_1 \Rightarrow V_x = 5/3$
 $t = \infty \Rightarrow V_x = 0$

$$V_x = 5/3 \exp\left(-\frac{t_2 - t_1}{RC}\right) \Rightarrow$$

em $t = t_2 : V_x = 1/3 \Rightarrow 1/3 = 5/3 \exp\left(-\frac{t_2 - t_1}{RC}\right)$

$$1/5 = \exp\left(-\frac{T_1}{RC}\right)$$

$$T_1 = RC \ln(5)$$

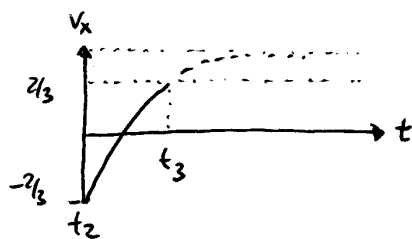

tempo de relax $\tau = RC$ } \Rightarrow
 $t = t_2 : V_x = -2/3 V_{cc}$
 $t = \infty : V_x = V_{cc}$

$$V_x = 1 - 5/3 \exp\left(-\frac{t - t_2}{RC}\right)$$

em $t = t_3 : V_x = 2/3 \Rightarrow 2/3 = 1 - 5/3 \exp\left(-\frac{t_3 - t_2}{RC}\right)$

$$1/5 = \exp\left(-\frac{T_2}{RC}\right)$$

$$T_2 = RC \ln(5)$$

$$f = \frac{1}{T_1 + T_2} = \frac{1}{2 RC \ln(5)}$$

$f = 10 \text{ kHz} \Rightarrow 2 RC \ln(5) = 10^{-4} \text{ s}$

exemplo : $R = 1 \text{ k}\Omega \Rightarrow$

$C = 31 \text{ nF}$