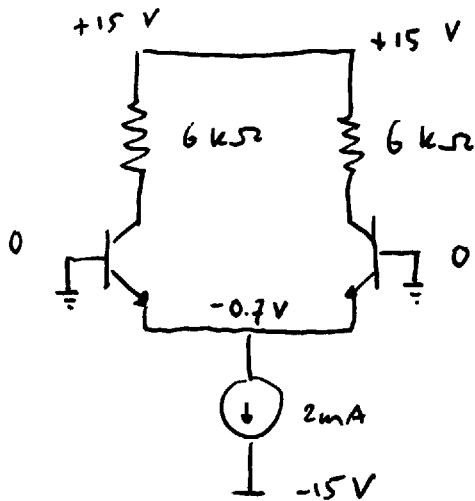




$$a) \quad I_{E1} = I_{E2} = 1 \text{ mA}$$

$$I_{C1} = I_{C2} = \frac{\beta}{\beta+1} \times 1 \text{ mA} \approx 1 \text{ mA}$$

$$I_{B1} = I_{B2} = \frac{1}{\beta+1} \times 1 \text{ mA} = 5 \mu\text{A}$$

$$V_{C1} = V_{C2} = 15 \text{ V} - 6 \text{ k}\Omega \times 1 \text{ mA} = 9 \text{ V}$$


$$V_{E1} = V_{E2} = V_{B1} - 0.7 = -0.7 \text{ V}$$

$$r_{e1} = r_{e2} = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

$$\frac{V_{O1}}{V_{i1}} = - \frac{R_c}{r_e + 2R_s}$$

$$\approx - \frac{6 \text{ k}\Omega}{200 \text{ k}\Omega} = -0.03 \text{ V/V}$$

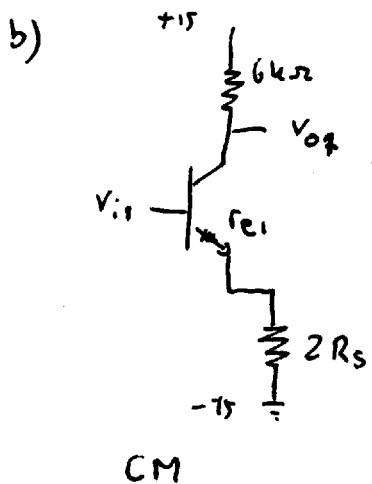
$$r_{o1} = r_{o2} \approx \frac{V_A}{I_C} = 100 \text{ k}\Omega$$



CM

Symmetry line
full circuit = 2x this half

$$CMRR = \frac{240}{0.03} = 8000$$

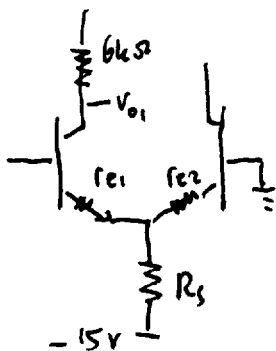

DM


$$\frac{V_{O1}}{V_{i1}} = - \frac{R_c}{r_{e1} + r_{e2} // R_s} \approx - \frac{R_c}{2r_e} = \frac{6 \text{ k}\Omega}{50 \Omega}$$

$$= -120 \text{ V/V}$$

$$\frac{V_{O2}}{V_{i2}} = - \frac{V_{O1}}{V_{i1}} = +120 \text{ V/V}$$

$$A_{dm} = \left| \frac{V_{O2} - V_{O1}}{V_{i2} - V_{i1}} \right| = \left| \frac{V_{O2} - V_{O1}}{0 - V_{i1}} \right| = \left| \frac{V_{O2}}{V_{i1}} + \frac{V_{O1}}{V_{i1}} \right| = \boxed{240 \text{ V/V}}$$

2)

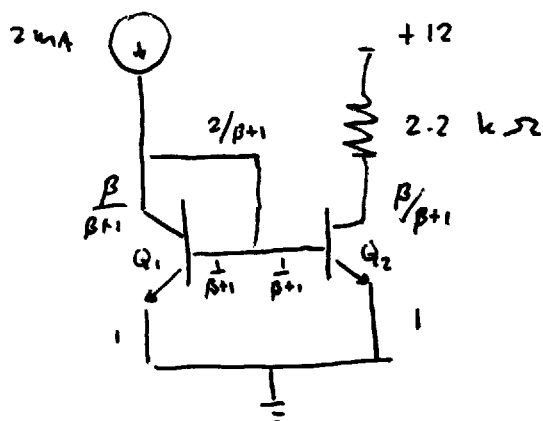

$$2 \text{ mA} = \left(\frac{\beta}{\beta+1} + \frac{2}{\beta+1} \right) \times I_{E2}$$

$$I_{E2} = \frac{\beta+1}{\beta+2} \times 2 \text{ mA}$$


$$I_{C2} = \frac{\beta}{\beta+1} I_{E2} = \frac{\beta}{\beta+1} \times \frac{\beta+1}{\beta+2} \times 2 \text{ mA}$$

$$= \frac{\beta}{\beta+2} \times 2 \text{ mA}$$

$$= 1.974 \text{ mA}$$

$$V_{C2} \approx 12 - 2.2 \text{ k}\Omega \times I_{C2} = 7.657 \text{ V}$$
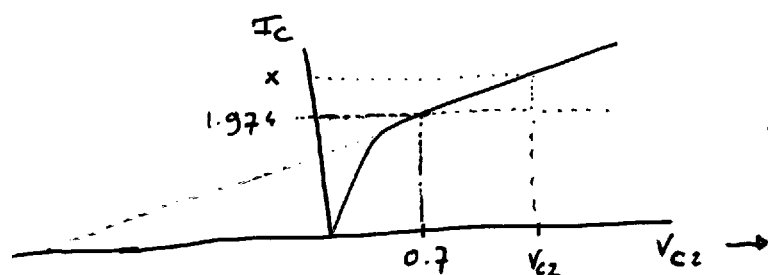
$$r_o = \frac{V_A}{I_{C2}} \approx 50 \text{ k}\Omega$$



1.974 mA seria quando $V_{C2} = V_{C1} = 0.7 \text{ V}$

$$V_{C2} = +12 \text{ V} - 2.2 \text{ k}\Omega \times I_{C2}$$

$$I_{C2} = 1.974 \text{ mA} + \frac{V_{C2} - 0.7 \text{ V}}{V_A / I_{C2}}$$

} non-linear system

approximation

$$I_{C2} = 1.974 \text{ mA} + \frac{V_{C2} - 0.7}{50 \text{ k}\Omega}$$

$$V_{C2} = +12 \text{ V} - 2.2 \text{ k}\Omega \times \left[1.974 \text{ mA} + \frac{V_{C2} - 0.7}{50 \text{ k}\Omega} \right]$$


$$V_{C2} + \frac{2.2 \text{ k}\Omega}{50 \text{ k}\Omega} V_{C2} = 12 \text{ V} - 2.2 \text{ k}\Omega \times 1.974 \text{ mA} + \frac{2.2 \text{ k}\Omega}{50 \text{ k}\Omega} \times 0.7 \text{ V}$$

$$V_{C2} = 7.365 \text{ V}$$

$$I_{C2} = (12 - V_{C2}) / 2.2 \text{ k}\Omega = 2.107 \text{ mA}$$

3)

a)

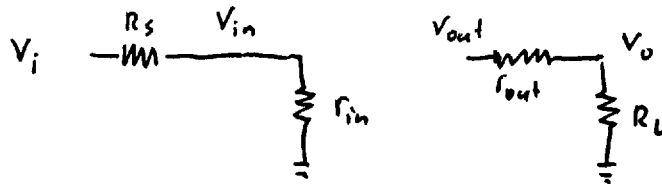


$$A_v \equiv \frac{V_o}{V_i} = \frac{V_o}{V_{out}} \cdot \underbrace{\frac{V_{out}}{V_{in}}}_A \cdot \frac{V_{in}}{V_i} \quad A = -100$$

$$\frac{V_{in}}{V_i} = \frac{r_{in}}{r_{in} + R_s} = \frac{5 \text{ k}\Omega}{5 \text{ k}\Omega + 1 \text{ k}\Omega} = \frac{5}{6}$$


$$\frac{V_o}{V_{out}} = \frac{R_L}{R_L + r_{out}} = \frac{3 \text{ k}\Omega}{3 \text{ k}\Omega + 1 \text{ k}\Omega} = \frac{3}{4}$$

$$A_v = \frac{3}{4} \times (-100) \times \frac{5}{6} = -62.5$$

b) baixas frequências / low frequencies

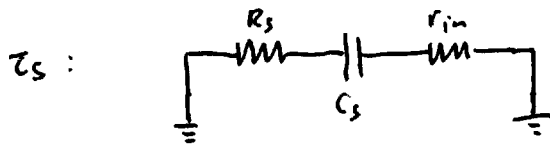
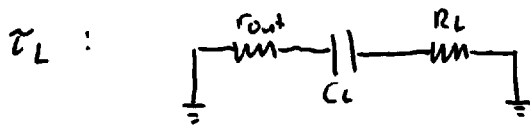
$$\tau_s = (R_s + r_{in}) C_s = (1 \text{ k}\Omega + 5 \text{ k}\Omega) \times 10 \mu\text{F} \\ = 60 \text{ ms}, \quad f_s = \frac{1}{2\pi\tau_s} = 2.65 \text{ Hz}$$





$$\tau_L = (R_L + r_{out}) C_L = (1 \text{ k}\Omega + 1 \text{ k}\Omega) \times 10 \mu\text{F} \\ = 20 \text{ ms}, \quad f_L = \frac{1}{2\pi\tau_L} = 7.96 \text{ Hz}$$

$$\omega_{tot} = \omega_s + \omega_L = \frac{1}{\tau_s} + \frac{1}{\tau_L} = 66.67 \text{ rad/s}$$

$$f_{LH} = \frac{1}{2\pi} \omega_{tot} = 10.6 \text{ Hz} = f_s + f_L$$

altas frequências / high frequencies

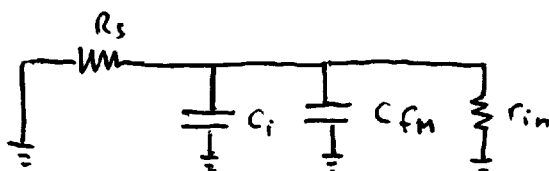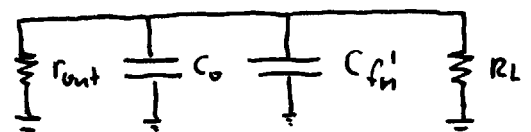 τ_{in}  τ_{out}

$$C_{fM} = (1-A) \times C_f = 101 \times 10 \text{ pF}$$

$$= 1.01 \text{ nF}$$

$$C_{fM}' = \left(1 - \frac{1}{A}\right) \times C_f = 1.01 \times 10 \text{ pF}$$

$$= 10.1 \text{ pF}$$

$$\tau_{in} = (R_s // r_{in}) \times (C_i + C_{fM})$$

$$= (1 \text{ k}\Omega // 5 \text{ k}\Omega) \times (10 \text{ pF} + 1010 \text{ pF})$$

$$= 8.50 \times 10^{-7} \text{ s}$$

$$f_{in} = \frac{1}{2\pi \tau_{in}} = 187 \text{ kHz}$$

$$\tau_{out} = (R_L // r_{out}) \times (C_o + C_{fM}')$$

$$= (3 \text{ k}\Omega // 1 \text{ k}\Omega) \times (10 \text{ pF} + 10.1 \text{ pF})$$

$$= 1.51 \times 10^{-8} \text{ s}$$



$$f_{out} = \frac{1}{2\pi \tau_{out}} = 10.6 \text{ MHz}$$

$$\tau_{tot} = \tau_{in} + \tau_{out} = 8.65 \times 10^{-7} \text{ s}$$

$$f_{Htot} = \frac{1}{2\pi \tau_{tot}} = 184 \text{ kHz}$$

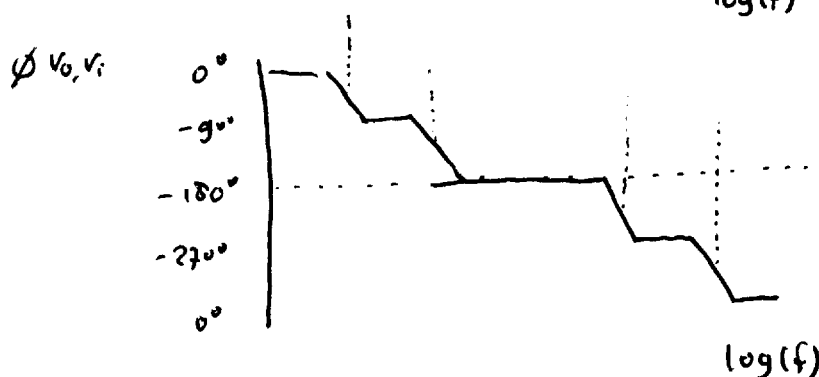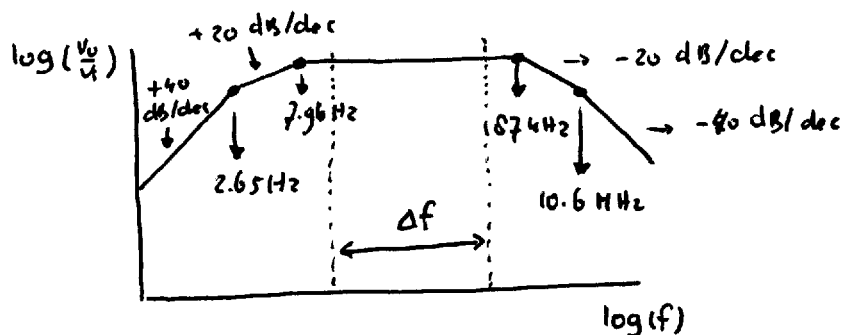c) Bandwidth



$$\Delta f = 184 \text{ kHz} - 10.6 \text{ MHz}$$




4) a)
$$A_v = \frac{A}{1 + A\beta} = \frac{A(\omega)}{1 + A(\omega)\beta(\omega)} = \frac{A(f)}{1 + A(f)\beta(f)}$$

b)


Bode plots
of A , $1/\beta$
and β

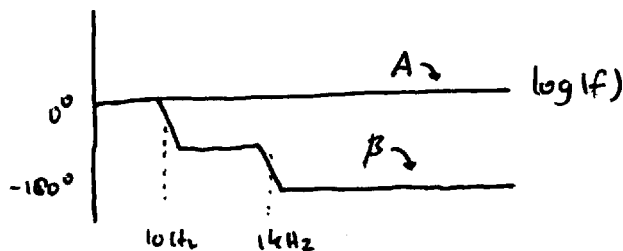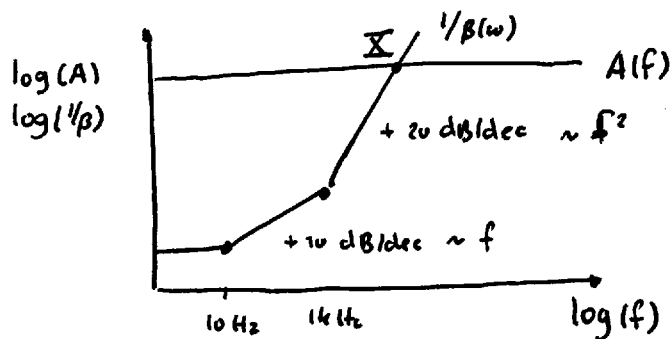

Nyquist plot
of $A\beta$

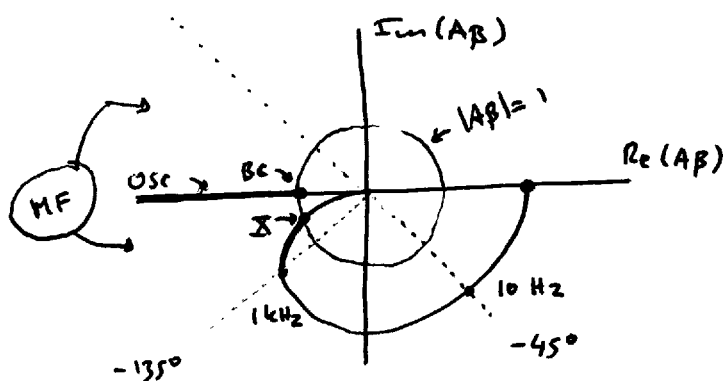

The circuit does not oscillate with guarantee, but has the risk to oscillate between 1 kHz, where it enters the phase margin zone (MF); and X, where it enters the zone $|A\beta| < 1$ that is safe.

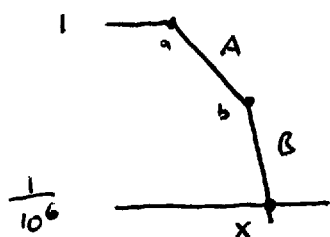

a : 10 Hz, $|\beta| = 1$

A : $|\beta| = 1 \times 10^6 \text{ Hz} / f$

b : 1 kHz, $|\beta| = 1 \times 10^6 \text{ Hz} / 1 \text{ kHz} = 0.01$


B : $|\beta| = 0.01 \times (1 \text{ kHz})^2 / f^2$

X : $|A\beta| = 1 \Rightarrow |\beta| = \frac{1}{A} = 10^{-6} = 0.01 \times \frac{(1 \text{ kHz})^2}{f^2}$

$\Rightarrow f_X = 100 \text{ kHz}$

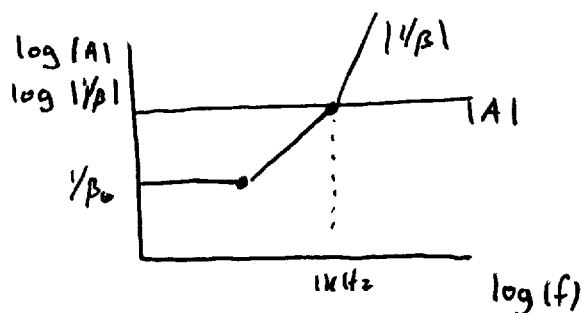c) 1 kHz - 100 kHz

possible solutions: - reduce β_0
- reduce A



Make $|A|$ and $1/\beta$ cross at 1 kHz

- reduce β_0 : $\beta = \frac{\beta_0}{(1 + jf/10 \text{ Hz}) \cdot (1 + jf/1 \text{ kHz})}$

At 1 kHz $|\beta| = 1/|A| = 10^{-6}$

$\Rightarrow \beta_0 \times 10 \text{ Hz} / 1 \text{ kHz} = 10^{-6}$

$\Rightarrow \beta_0 = 10^{-4}$


- reduce A : At 1 kHz $|\beta| = 1/|A|$

$1 \times \frac{10 \text{ Hz}}{1 \text{ kHz}} = 1/A \Rightarrow A = 10^2$

5) $V_A = \infty$
 $r_{out} = R_C \parallel r_o = 14 \text{ } \Omega$
 $R_L = 14 \text{ } \Omega \rightarrow \text{max power transfer}$

a) class A : the complete wave appears on the output, albeit with offset ($V_i = 0 \Rightarrow V_o \neq 0$)

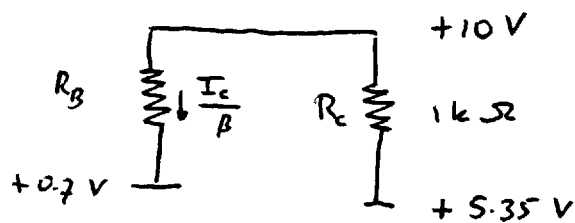b) We want V_o to be halfway between $+V_{CC}$ and V_B
 let's say between $+10 \text{ V}$ and $+0.7 \text{ V} \rightarrow V_o = +5.35 \text{ V}$





$$I_C = \frac{(10\text{ V} - 5.35\text{ V})}{1\text{ k}\Omega} = 4.65\text{ mA}$$

$$I_B = \frac{1}{\beta} I_C = 46.5\text{ }\mu\text{A}$$

$$I_B = \frac{(10\text{ V} - 0.7\text{ V})}{R_B} = 46.5\text{ }\mu\text{A} \Rightarrow R_B = 200\text{ k}\Omega$$

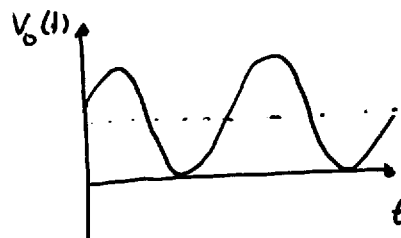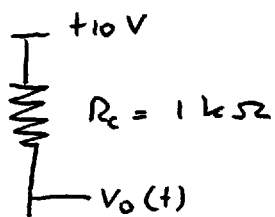c) ignoring I_B and P_B , and using $V_{CE} = +5\text{ V}$



$$V_O(t) = 5\text{ V}(1 + \sin \omega t)$$

$$P_L(t) = V_L(t) \cdot I_L(t)$$

$$= [10\text{ V} - 5\text{ V}(1 + \sin \omega t)] \times \frac{[10\text{ V} - 5\text{ V}(1 + \sin \omega t)]}{R_C}$$

$$= \frac{25\text{ V}^2}{R_C} [1 - \sin \omega t]^2$$

$$\bar{P}_L = \frac{1}{T} \int_0^T P_L(t) dt = 25\text{ mW} \frac{1}{T} \int_0^T (1 - \sin \omega t)^2 dt$$

$$= 25\text{ mW} \times (1 + \frac{1}{2}) = \underline{37.5\text{ mW}}$$

$$P_S(t) = V_S(t) \cdot I_S(t) = +10\text{ V} \times I_L(t)$$

$$= 10\text{ V} \times [10\text{ V} - 5\text{ V}(1 + \sin \omega t)] / R_C$$

$$= 50\text{ mW} - 50\text{ mW} \sin \omega t$$

$$\bar{P}_S = 50\text{ mW}$$

$$\eta = \frac{37.5\text{ mW}}{50\text{ mW}} = 75\%$$

d) 12.5 mW (50 - 37.5) in transistor

$$\begin{aligned} T_J &= 40^\circ + 12.5 \text{ mW} \times 40^\circ \text{C} / \text{W} \\ &= 40.5^\circ \text{C} \end{aligned}$$