

$$I_c + I_B = 2 \text{ mA}$$

$$I_E = I_B + I_c = 2 \text{ mA}$$

$$\beta = 99, I_c = \beta I_B$$

$$\beta I_B + I_B = 2 \text{ mA}$$

$$I_B = \frac{2 \text{ mA}}{\beta + 1} = 20 \text{ } \mu\text{A}$$

$$I_c = 1.98 \text{ mA}, I_E = 2.0 \text{ mA}$$


$$V_E = 0, V_B = 0.7 \text{ V}, V_C = V_B + I_B \times 100 \text{ k}\Omega = 2.7 \text{ V}$$

note: for DC analysis

- C = open circuit
- signal sources to ground  $\perp$

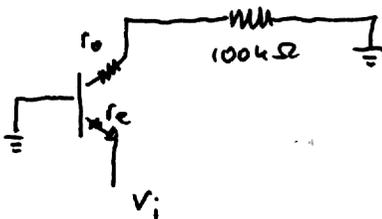c) For AC (small signal) analysis

- voltage sources : ground  $\perp$
- current sources : open circuit  $\text{---} \dots$
- capacitors : short circuit  $\text{---} \parallel \text{---} \Rightarrow \text{---}$



$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \text{ } \Omega$$


$$r_o = \frac{V_A}{I_c} = \frac{100 \text{ V}}{2 \text{ mA}} = 50 \text{ k}\Omega$$

From Electronics I : Common Base Amp. Gain

$$+ \frac{\text{everything at collector}}{\text{everything at emitter}} = \frac{100 \text{ k}\Omega // 50 \text{ k}\Omega}{25 \text{ } \Omega} = 1333$$


Why gain is like this?

(2)

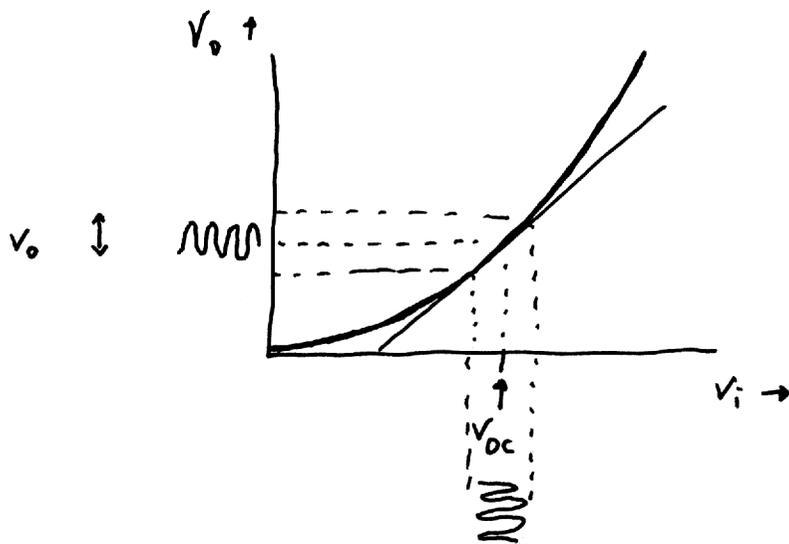

$$\bar{V}_i(t) = V_{Dc} + v_i \sin(\omega t)$$
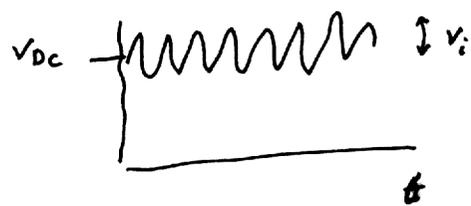
$$\bar{V}_o(t) = V_{Dc} + v_o \sin(\omega t + \phi)$$



$$v_o = \frac{dV_o}{dV_i} \times v_i$$

small signal

$$A_v \equiv \frac{v_o}{v_i} = \frac{dV_o(v_i)}{dV_i}$$

$$= \frac{dV_o}{dI_c} \cdot \frac{dI_c}{dI_B} \cdot \frac{dI_B}{dV_i} \quad (*)$$

$$\frac{dI_B}{dV_i} :$$

Ebers Moll

$$I_c = I_0 \left[ \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] + \dots$$

$$\approx I_0 \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$I_B = \frac{I_c}{\beta} = \frac{I_0}{\beta} \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$= \frac{I_0}{\beta} \exp\left(-\frac{V_i}{V_T}\right)$$

$$V_{BE} = V_B - V_E = -V_i$$

B = ground

E = input

$$\frac{dI_B}{dV_i} = \frac{I_0}{\beta} \exp\left(-\frac{V_i}{V_T}\right) \times \left(-\frac{1}{V_T}\right) = -\frac{I_B}{V_T} = -\frac{I_c}{\beta V_T} = -\frac{I_E}{(\beta+1)V_T}$$

$$\equiv -\frac{1}{(\beta+1)} \cdot \frac{1}{r_e} = -\frac{1}{r_{\pi}}$$


$r_e$  and  $r_{\pi}$  are parameters (virtual resistances)

to describe the behavior

$$\frac{dI_B}{dV_i} = -\frac{1}{r_{\pi}} = -\frac{1}{\beta+1} \cdot \frac{1}{r_e} = -\frac{g_m}{\beta+1}$$

$$\frac{dI_c}{dI_b} = \beta$$


$$\frac{dV_o}{dI_c} :$$

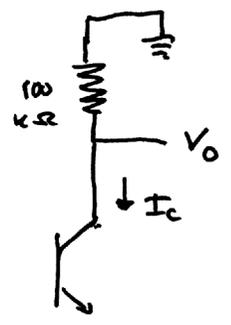

Forgetting  $r_o$  of transistor, it is obvious that

$$\frac{dV_o}{dI_c} = -100 \text{ k}\Omega$$

Including  $r_o$  of transistor

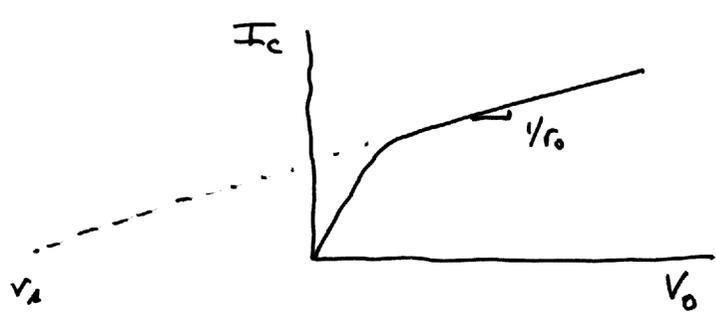

$$\frac{dI_c}{dV_o} \equiv \frac{1}{r_o} = \frac{1}{50 \text{ k}\Omega}$$

$$\Rightarrow \frac{dV_o}{dI_c} = 50 \text{ k}\Omega$$

Combining two effects : 
$$\frac{dV_o}{dI_c} = 50 \text{ k}\Omega // 100 \text{ k}\Omega = 33.3 \text{ k}\Omega$$

Everything in (\*) :

$$A_v = \frac{dV_o}{dI_c} \cdot \frac{dI_c}{dI_b} \cdot \frac{dI_b}{dV_i} = (-33.3 \text{ k}\Omega) \times (\beta) \times \left(-\frac{g_m}{\beta+1}\right)$$

everything at collector  $\rightarrow$   $33.3 \text{ k}\Omega$   $\times$   $\frac{\beta}{\beta+1}$   
 everything at emitter  $\rightarrow r_e$


d)  $r_i \equiv \frac{1}{\frac{dI_i}{dV_i}}$

$$I_i = -I_E = -I_{E0} \exp\left(\frac{V_{BE}}{V_T}\right) = -I_{E0} \exp\left(-\frac{V_i}{V_T}\right)$$


$$\frac{dI_i}{dV_i} = -I_{E0} \exp\left(-\frac{V_i}{V_T}\right) \cdot \left(-\frac{1}{V_T}\right) = \frac{I_{E0}}{V_T} = \frac{1}{r_e} = g_m$$

$$r_i = r_e$$

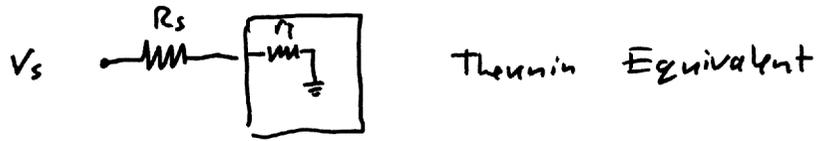$r_i$  represents the losses due to the non-infinite input resistance (ideal:  $r_{in} = \infty$ ,  $i_{in} = 0$ ,  $v_{in}$  unaltered)



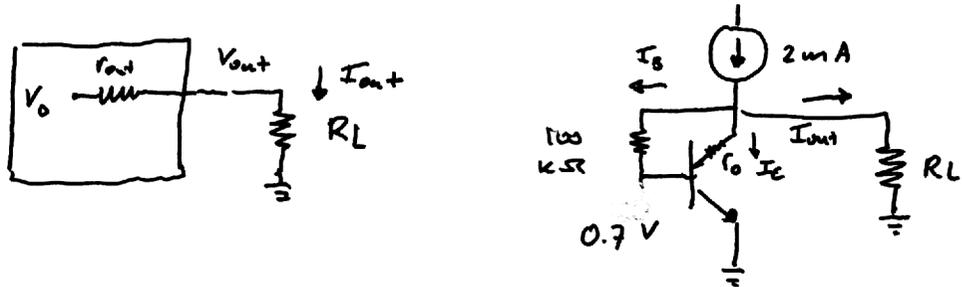e)  $r_{out}$  represents if loading the amplifier ( $I_{out} \neq 0$ ) changes the signal  $V_{out}$  or not.



If  $R_L = \infty$  :  $V_{out} = V_0 = 2.7 V$   
 $I_{out} = \emptyset$


$V_{out}$  is a function of  $I_{out}$   $V_{out}(I_{out})$

$$r_{out} = \frac{dV_{out}}{dI_{out}} = \left/ \frac{dI_{out}}{dV_{out}} \right.$$

$$I_{out} = 2 \text{ mA} - I_B - I_C$$

$$\frac{dI_{out}}{dV_{out}} = \frac{dI_{out}}{dV_C} = 0 - \frac{1}{100 \text{ k}\Omega} - \frac{1}{r_o}$$

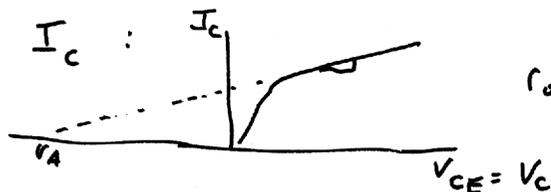
$$I_B = \frac{V_C - V_B}{100 \text{ k}\Omega} = \frac{V_C - 0.7 \text{ V}}{100 \text{ k}\Omega}$$



$$r_o = \frac{V_A}{I_C} = 50 \text{ k}\Omega$$

$$r_{out} = \left/ \frac{dI_{out}}{dV_{out}} \right. = \frac{1}{\frac{1}{100 \text{ k}\Omega} + \frac{1}{r_o}} = 100 \text{ k}\Omega \parallel 50 \text{ k}\Omega = 33.3 \text{ k}\Omega$$

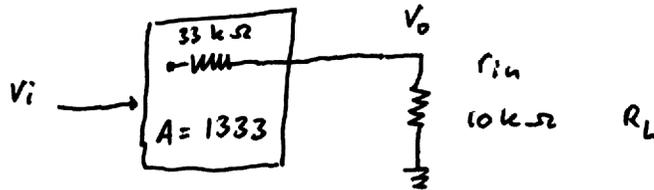$r_{out}$  is important because we will be able to calculate the gain when we connect a load with finite impedance





without knowing anything (else) about our amplifier, with the parameter  $r_{out}$  ( $= 33\text{ k}\Omega$ ) we can calculate the gain of the total circuit

$$\frac{V_o}{V_i} = A_v \times \frac{R_L}{R_L + r_{out}} = 1333 \times \frac{10\text{ k}\Omega}{10\text{ k}\Omega + 33\text{ k}\Omega} = 310$$

NOTE

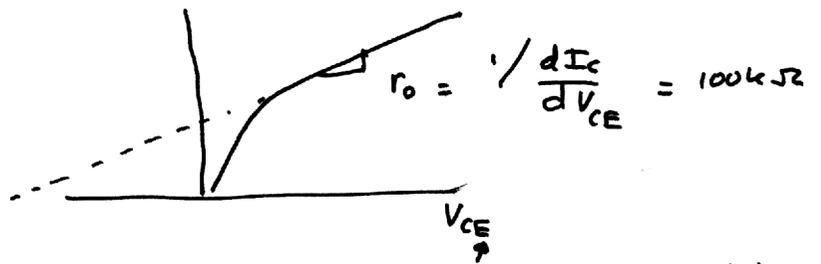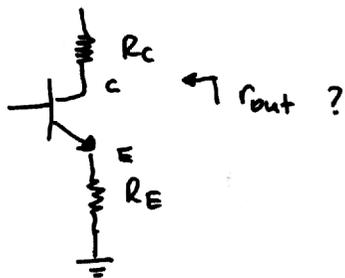Careful with calculation of (output) resistance when feedback takes place. Imagine the circuit below:



E is not ground!

What is total output resistance? One might think

$$r_{out} = (r_o + R_E) \parallel R_C$$

WRONG! Why? Feedback!

Feedback we want to know  $\frac{dI_c}{dV_c}$

- Imagine  $V_c$  raised
- $I_c$  rises (Early voltage  $\rightarrow r_o$ , etc.) 
- $I_E$  rises
- $V_E$  rises ( $V_E = I_E \times R_E$ )
- $V_B - V_E$  drops !!!
- $I_B$  drops (Ebers-Moll  $I_0 [\exp(\frac{V_{BE}}{V_T}) - 1]$ )
- $I_E = (\beta + 1) \cdot I_B$  and  $I_c = \beta I_B$  drop !!




$I_c$  rises less than expected

$\frac{dI_c}{dV_c}$  is less than expected

$r_{out}$  is much larger than expected.

Small signal equivalent ( $\pi$ -hybrid)

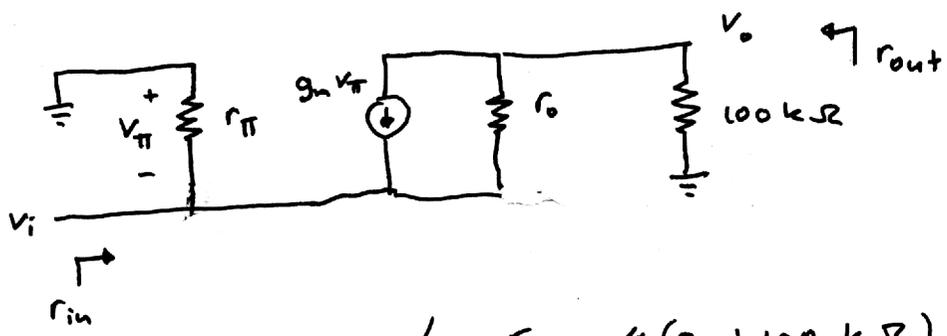

$r_{in} \neq r_{\pi} \parallel (r_o + 100 \text{ k}\Omega)$  !

$r_{out} = 100 \text{ k}\Omega \parallel r_o$