

Figure 69 shows the circuit of the feedback loop β for the Colpitts Oscillator. The resistance R is the output resistance of the opamp. Ideally this is zero, but any real opamp has finite output resistance and this is essential, the feedback loop β is per definition the part of the output V_o that appears at the input V_i of our amplifier (that has a gain equal to $A = -R_f/R_1$), that can be found by considering the voltage dividers in the circuit:

$$\beta \equiv \frac{V_i}{V_o} = \frac{Z}{Z + R} \times \frac{Z_{C2}}{Z_{C2} + Z_L} \quad (206)$$

First, the second voltage divider composed of C_2 ($Z_{C2} = 1/sC_2$) and L ($Z_L = sL$), with $s = j\omega$ is given by

$$\frac{Z_{C2}}{Z_{C2} + Z_L} = \frac{1}{1 - \omega^2 LC_2}. \quad (207)$$

The impedance Z is given by

$$Z = [(1/sC_1)^{-1} + (1/sC_2 + sL)^{-1}]^{-1}. \quad (208)$$

Substituting this in (206) gives

$$\beta = \frac{1}{(1 - \omega^2 LC_2) + j\omega RC_1[C_2/C_1 + (1 - \omega^2 LC_2)]}. \quad (209)$$

Oscillation will occur when the loop gain $A\beta$ is unity. Since A is purely real, this means that β must be real too. This implies

$$RC_1[C_2/C_1 + (1 - \omega^2 LC_2)] = 0. \quad (210)$$

--

Trivial solutions are $R = 0$ (ideal amplifier) or $C_1 = 0$. The non-trivial solution is

$$\omega = \sqrt{\frac{1}{L(C_1 \oplus C_2)}}, \quad (211)$$

with $C_1 \oplus C_2$ the series sum capacitance of C_1 and C_2 , $C_1 \oplus C_2 = (1/C_1 + 1/C_2)^{-1}$. At this frequency the feedback loop is, according to Eq. (209), $\beta = -C_1/C_2$. Thus, if our amplifier has a gain A such that the total loop-gain is unity the Barkhausen criterion will be met; if

$$A\beta = \left(-\frac{R_f}{R_1}\right) \times \left(-\frac{C_1}{C_2}\right) = 1 \quad (212)$$

the circuit will oscillate at the frequency given by

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{L(C_1 \oplus C_2)}}, \quad (213)$$

Note that the output resistance of the opamp does not enter into the final results. It only has effect in the *quality* of oscillation; the lower R the better ('sharper') the oscillation frequency.

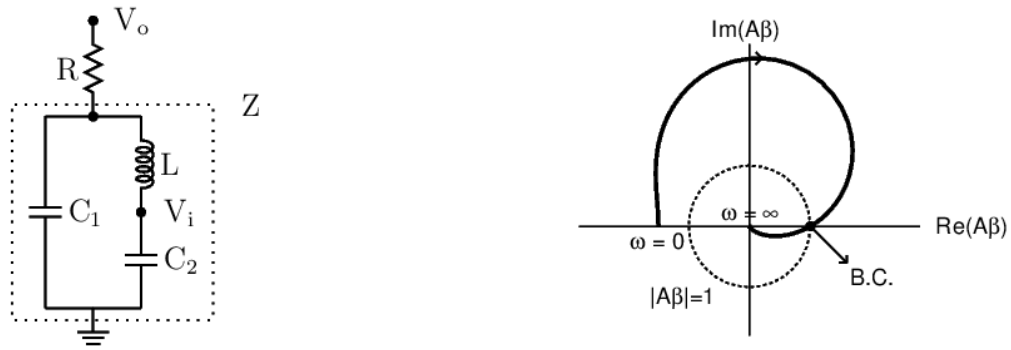


Fig. 69: Left: Circuit of the feedback loop of the Colpitts Oscillator. The resistance R is the output resistance of the opamp. Right: Nyquist plot for an example that meets the condition (Barkhausen Criterion, B.C.) of oscillation, for $R_f/R_1 = C_2/C_1$. (Exercise 16)

(excerpt from the upcoming book Electronic Instrumentation, P. Stallinga)