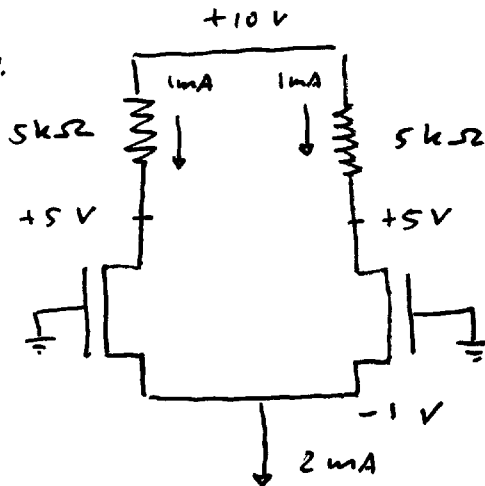


1:

a) Bias:



$$V_T = 0$$

$$k = 2 \text{ mA/V}^2$$

SAT: $I_{D1} = \frac{k}{2} V_{GS}^2 = I_{D2} = 1 \text{ mA} \Rightarrow$


$$\frac{2 \text{ mA/V}^2}{2} \cdot (0 - V_S)^2 = 1 \text{ mA} \Rightarrow$$

$$V_S = -1 \text{ V}$$

(check if in saturation : $V_{DS} > V_{GS} - V_T : 6 > 1 \text{ ok!}$)

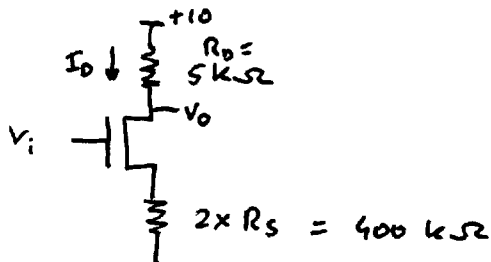b) Common mode gain:

Equivalent circuit . use technique of symmetry



$$A_V = \frac{dV_O}{dV_i} = - \frac{dI_D}{dV_G} \times R_D$$

$$I_D = \frac{k}{2} (V_G - V_S)^2 \quad . \quad V_S = -1 \text{ V} + (I_D - 1 \text{ mA}) \cdot 2 R_S$$

$$I_D = \frac{k}{2} (V_G + 1 \text{ V} + (I_D - 1 \text{ mA}) \cdot 2 R_S)^2$$

$$V_G = -1 \text{ V} + \frac{I_D - 1 \text{ mA}}{1 \text{ mA}} \cdot 2 R_S + \sqrt{\frac{2}{k}} \sqrt{I_D}$$


$$\frac{dV_G}{dI_D} = + 2 R_S + \sqrt{\frac{2}{k}} \cdot \frac{1}{2 \sqrt{I_D}} = + 400 \text{ k}\Omega + 500 \Omega = 399.5 \text{ k}\Omega$$

$$\frac{dI_0}{dV_G} = \frac{1}{\frac{dV_G}{dI_0}} = \frac{1}{399.5 \text{ k}\Omega} \approx 2.5 \mu\text{S}$$

$$A_v^{cm} = -2.5 \mu\text{S} \times 5 \text{ k}\Omega = -0.0125$$

Common mode gain = $\boxed{-0.0125}$

differential mode gain :

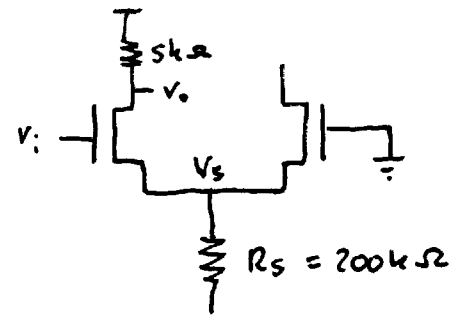

Assumption : $I_{D1} + I_{D2} = I_S$
 $= \text{constant} = 2\text{mA}$

$$\Rightarrow V_S = -1\text{V} + \frac{V_i}{2}$$

$$I_{D1} = \frac{k}{2} (V_{G1} - V_S)^2$$

$$= \frac{k}{2} (V_i + 1\text{V} - \frac{V_i}{2})^2 = \frac{k}{2} (\frac{V_i}{2} + 1\text{V})^2$$

$$g_m = \frac{dI_{D1}}{dV_i} = 2 \frac{k}{2} (\frac{V_i}{2} + 1\text{V}) \cdot \frac{1}{2} = \frac{k}{2} (\frac{V_i}{2} + 1\text{V})$$

small signal $V_i \approx 0 \Rightarrow g_m = \frac{k}{2} \times 1\text{V}$


$$= \frac{2\text{mA}/\text{V}^2}{2} \times 1\text{V} = 1\text{mS}$$

$$A_v = \frac{dV_o}{dV_i} = -\frac{dI_{D1}}{dV_i} \times R_D = -g_m R_D = -1\text{mS} \times 5\text{k}\Omega = \boxed{-5}$$

$$\text{CMRR} = \left| \frac{-5}{-0.0125} \right| = 400$$

Note : we can use knowledge of electronics I to find a faster answer :

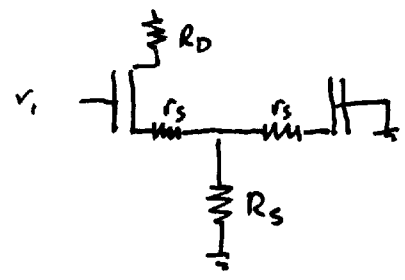The gain of common-source amplifier is given by : all resistance at drain divided by all resistance at source with a minus sign.



The r_s resistances are modelling resistances equivalent to r_e for bipolar transistor. They are virtual

resistances that describe behavior of I_s (I_E). For

bipolar r_e was found to be $(\frac{\beta+1}{\beta} g_m)^{-1}$

$$r_e \equiv \frac{1}{\frac{\partial I_E}{\partial V_{BE}}} = \frac{1}{\frac{\beta+1}{\beta} \cdot \frac{dI_C}{dV_{BE}}} = \frac{1}{\frac{\beta+1}{\beta} \cdot g_m}$$

For a FET


$$r_s \equiv \frac{1}{\frac{\partial I_S}{\partial V_{GS}}} = \frac{1}{\frac{\partial I_D}{\partial V_{GS}}} = \frac{1}{g_m} \quad \left| \quad \begin{aligned} g_m &= \frac{dI_D}{dV_{GS}} = kV_{GS} \\ &= \frac{k/2 V_{GS}^2}{1/2 V_{GS}} = \frac{2I_D}{V_{GS}} \end{aligned} \right.$$

The gain of the common-source configuration above is thus

$$\frac{V_o}{V_i} = - \frac{R_D}{r_s + r_s \parallel R_S} \approx - \frac{R_D}{2r_s} \quad \left\{ \begin{aligned} r_s &= 1/g_m \\ g_m &= \frac{2I_D}{V_{GS}} = \frac{2 \mu A}{1V} \\ &= 2 \text{ mS} \\ r_s &= 500 \Omega \end{aligned} \right.$$

$$= - \frac{5000}{1000} = -5$$

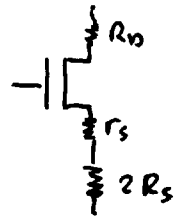The common mode common source configuration:



$$\frac{V_o}{V_i} = - \frac{R_D}{r_s + 2R_S} \approx - \frac{5000}{400000} = -0.0125$$


$$c) \quad r_{in} \equiv \left. \frac{1}{\frac{\partial I_{in}}{\partial v_{in}}} \right|_{I_{in} = I_G = 0} \Rightarrow r_{in} = \infty$$

$$r_{out} \equiv \left. \frac{1}{\frac{\partial I_{out}}{\partial v_{out}}} \right|_{v_{out} = 0} = R_D \parallel r_o \quad , \quad r_o = \infty \Rightarrow r_{out} = R_D$$

↑
of FET

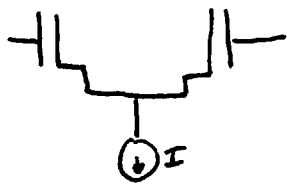2 : For a differential pair based on bipolar transistors:
See page 490 of Sedra (Large-Signal operation of the
BJT Differential Pair)

For a differential pair based on FETs:
See page 527 of Sedra (MOS differential amplifiers)



$$I_{D1} = \frac{K}{2} (V_{GS1} - V_T)^2$$

$$I_{D2} = \frac{K}{2} (V_{GS2} - V_T)^2$$

$$\sqrt{I_{D1}} = \sqrt{\frac{K}{2}} (V_{GS1} - V_T) \quad , \quad \sqrt{I_{D2}} = \sqrt{\frac{K}{2}} (V_{GS2} - V_T)$$

$$\sqrt{I_{D1}} - \sqrt{I_{D2}} = \sqrt{\frac{K}{2}} (V_{GS1} - V_{GS2}) = \sqrt{\frac{K}{2}} v_i \quad (A)$$

$$I_{D1} + I_{D2} = I \quad (B)$$

combine (A) and (B) :

$$I_{D1} = \frac{I}{2} + \sqrt{KI} \frac{v_i}{2} \sqrt{1 - \frac{(v_i/2)^2}{I/K}}$$

$$I_{D2} = \frac{I}{2} - \sqrt{KI} \frac{v_i}{2} \sqrt{1 - \frac{(v_i/2)^2}{I/K}}$$

note : $\frac{I}{2} = \frac{K}{2} (V_{GS} - V_T)^2$ (when $V_{GS1} = V_{GS2}$; bias)


$$I_{D1} = \frac{I}{2} + \frac{I}{2} \left(\frac{V_i}{V_{GS0} - V_T} \right) \sqrt{1 - \frac{1}{2} \left(\frac{V_i}{V_{GS0} - V_T} \right)^2}$$

$$I_{D2} = \frac{I}{2} - \frac{I}{2} \left(\frac{V_i}{V_{GS0} - V_T} \right) \sqrt{1 - \frac{1}{2} \left(\frac{V_i}{V_{GS0} - V_T} \right)^2}$$

↑
offset

↑
linear

↑
non-linear

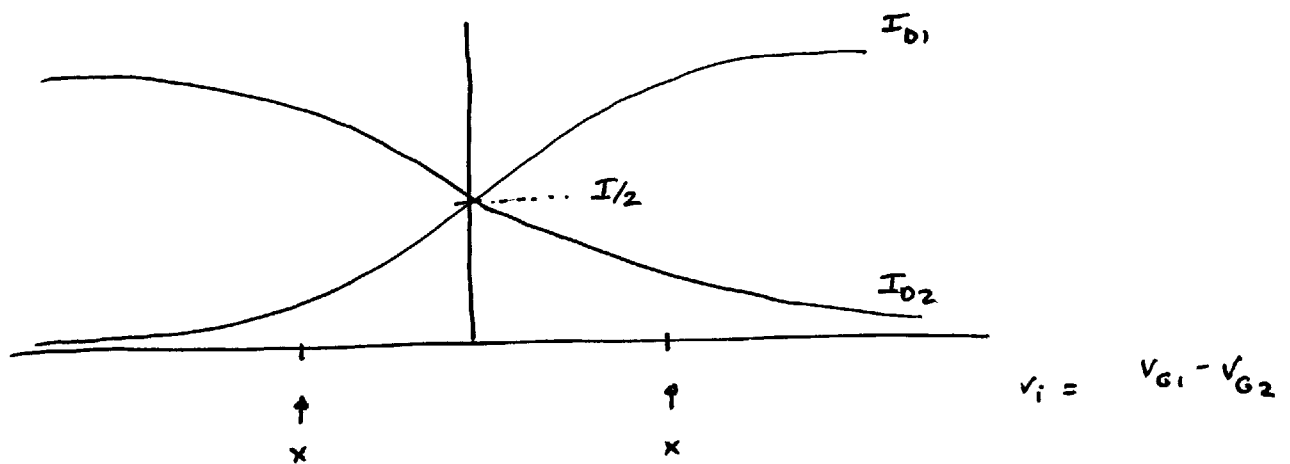

x: when $\frac{1}{2} \left(\frac{V_i}{V_{GS0} - V_T} \right)^2$ becomes significant relative to 1

$$\frac{1}{2} \left(\frac{V_i}{V_{GS0} - V_T} \right)^2 \sim 1 \Rightarrow V_i \approx \sqrt{2} \times (V_{GS0} - V_T)$$

This is easily in the volts range. compare this to the bipolar transistor that operates in the 10's of mV range.