
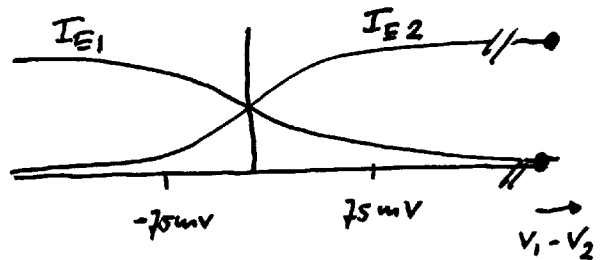


1: see lecture notes

2:

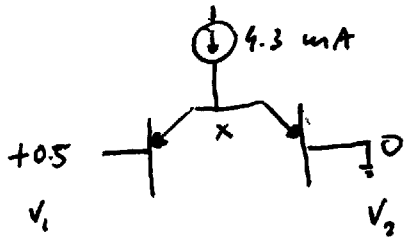


$$v_1 - v_2 = 500 \text{ mV} \rightarrow I_{E2} \approx 4.3 \text{ mA}, I_{E1} = 0$$

$$V_x = V_{E1} = V_{E2} = +0.7 \text{ V}$$


$$V_{BE1} = 0.2 \text{ V (closed)}$$

$$V_{BE2} = 0.7 \text{ V (open)}$$

$$I_{C1} = 0, I_{C2} = 4.3 \text{ mA}$$

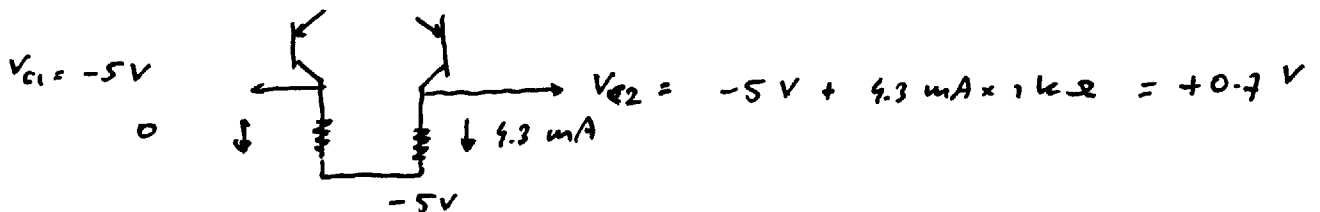


3:

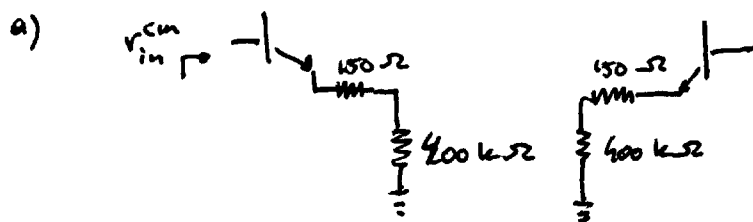

$$r_{in}^{cm} = (\beta + 1) \cdot [r_e + 150 \Omega + 400 \text{ k}\Omega] \approx 40 \text{ M}\Omega$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega$$
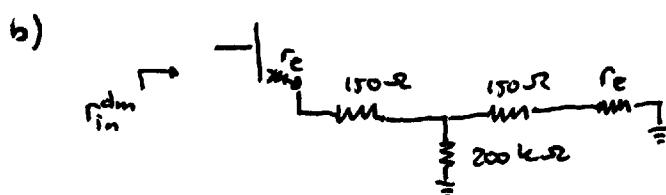
$$r_o = \frac{V_A}{I_C} = \frac{100 \text{ V}}{0.5 \text{ mA}} = 200 \text{ k}\Omega$$



$$r_{in}^{dm} = (\beta + 1) [r_e + 150 \Omega + (150 \Omega + r_e) // 200 \text{ k}\Omega] \approx (\beta + 1) \cdot 2 (50 \Omega + 150 \Omega) = 40 \text{ k}\Omega$$

$$c) A_{dm} = \frac{10 \text{ k}\Omega}{(r_e + 150 \Omega) + (r_e + 150 \Omega) \parallel 200 \text{ k}\Omega}$$

$$\approx \frac{10 \text{ k}\Omega}{2 (r_e + 150 \Omega)} = 25$$

$$d) A_{cm} = \frac{10 \text{ k}\Omega}{r_e + 150 \Omega + 400 \text{ k}\Omega} \approx \frac{1}{40}$$

$$e) CMRR \equiv \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{25}{1/40} = 1000$$

(= 30 dB [or 60 dB power])

//