

$$R_i = 20 \text{ k}\Omega$$

$$R_s = 830 \text{ }\Omega$$

$$C_i = 20 \text{ nF}$$

$$R_{G1} = 330 \text{ k}\Omega$$

$$R_D = 2 \text{ k}\Omega$$

$$C_s = 1 \text{ }\mu\text{F}$$

$$R_{G2} = 1.5 \text{ M}\Omega$$

$$R_L = 40 \text{ k}\Omega$$

$$C_L = 20 \text{ nF}$$

$$r_d = 100 \text{ k}\Omega, C_{gs} = 4 \text{ pF}, C_{ds} = 0.5 \text{ pF}, C_{gd} = 1.2 \text{ pF}$$

$$g_m = 3.4 \text{ mS}$$

$$\begin{aligned} \frac{v_o}{v_i} &= \frac{v_o}{v_g} \cdot \frac{v_g}{v_i} = - \frac{R_D // r_d // R_L}{1/g_m} \cdot \frac{R_{G1} // R_{G2}}{R_{G1} // R_{G2} + R_i} \\ &= - \frac{1.869 \text{ k}\Omega}{1/3.4 \text{ mS}} \cdot \frac{270.5 \text{ k}\Omega}{270.5 \text{ k}\Omega + 20 \text{ k}\Omega} \\ &= - 6.36 \cdot 0.93 = - 5.9 \end{aligned}$$

$$\tau_i = (R_i + R_{G1} // R_{G2}) \cdot C_i =$$

$$f_i = \frac{1}{2\pi\tau_i} = 27.4 \text{ Hz}$$

$$\tau_L = (R_D // r_d + R_L) \cdot C_L =$$

$$f_L = 189.6 \text{ Hz}$$


$$\tau_s = (R_s // 1/g_m) \cdot C_s =$$

$$f_s = 735.1 \text{ Hz}$$

$$f_{\text{total}} = 27.4 + 189.6 + 735.1 = 950 \text{ Hz}$$

in

IN:

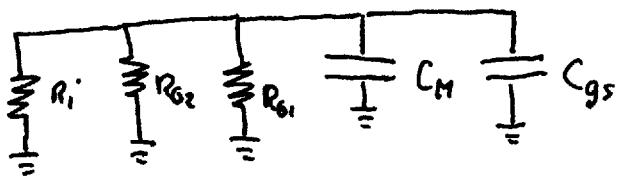


$$\begin{aligned}
 C_M &= C_{gd} \cdot (1 - A) \\
 &= 1.2 \mu F \cdot (1 - (-6.36)) \\
 &= 8.83 \mu F
 \end{aligned}$$

$$\tau_{in} = (C_M + C_{gs}) \times (R_{G1} // R_{G2} // R_i) = 2.4 \times 10^{-7} \text{ s}$$

$$f_{in} = 666 \text{ kHz}$$

OUT:

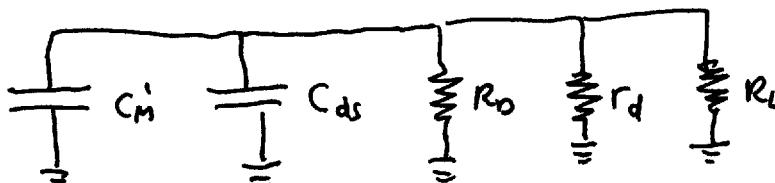

$$C_M' = C_{gd} (1 - \frac{1}{A}) = 1.39 \mu F$$

$$\tau_{out} = (C_M' + C_{ds}) \times (R_D // r_d // R_L) = 3.53 \times 10^{-9} \text{ s}$$

$$f_{out} = 45 \text{ MHz}$$

$$\tau_{total} = 2.4 \times 10^{-7} \text{ s} + 3.53 \times 10^{-9} \text{ s} = 2.43 \times 10^{-7} \text{ s}$$

$$f_{total} = \frac{1}{2\pi \tau_{total}} = 650 \text{ kHz}$$

