

# Electronics II

## Frequency analysis


P. Stallinga

1)

A certain commercial amplifier has the following parameters

- Voltage gain:  $A = -100$  V/V.
- Input resistance:  $r_{in} = 5$  k $\Omega$ .
- Output resistance:  $r_{out} = 1$  k $\Omega$ .
- Capacitance between the input and output:  $C_f = 10$  pF.
- Capacitance between the input and the box (ground) and the output and the box (ground):  $C_i = C_o = 10$  pF.

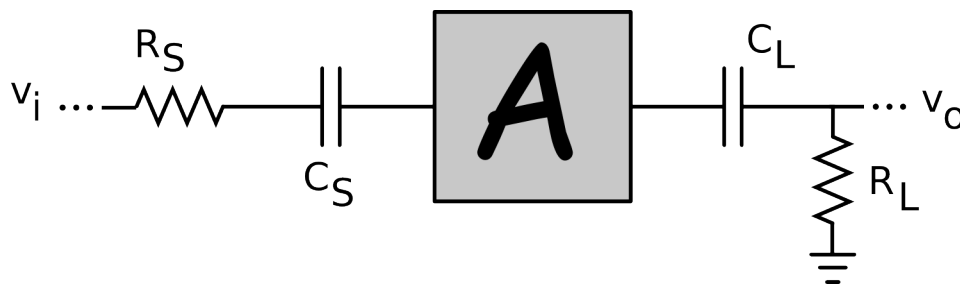
Based on this amplifier the following circuit was designed



$$R_S = 1 \text{ k}\Omega, R_L = 3 \text{ k}\Omega, C_S = C_L = 10 \text{ }\mu\text{F}.$$

- Determine the mid-frequency gain of the complete circuit.
- Schematically draw Bode plots of the behavior of the circuit in terms of frequency.
- Determine the band-width of the circuit.

2)

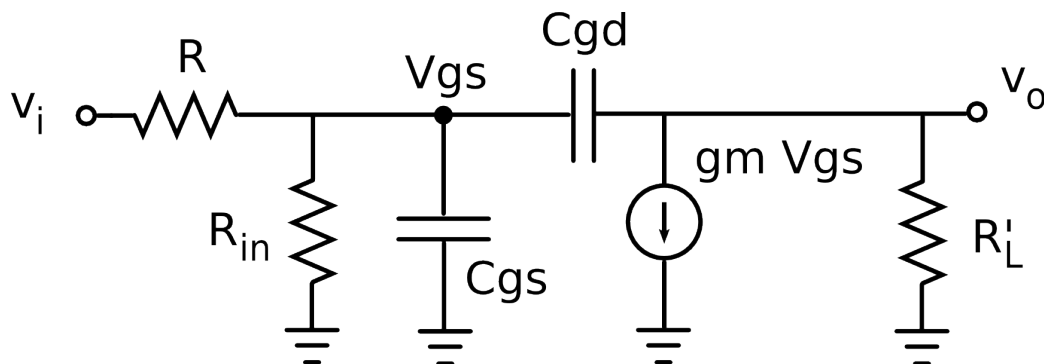

The figure above shows an equivalent circuit of an common-source FET amplifier. The input signal comes from a signal generator with an output resistance  $R$ .  $R_{in}$  represents the input resistance of the FET stage and is caused by the gate-bias resistances.  $R'_L$  is the parallel equivalent resistance composed

of load  $R_L$ , drain resistance  $R_D$  and FET output resistance  $r_o$ . Capacitors  $C_{gs}$  and  $C_{gd}$  are internal capacitors of the FET.

$R = 100 \text{ k}\Omega$ ,  $R_{in} = 420 \text{ k}\Omega$ ,  $C_{gs} = C_{gd} = 1 \text{ pF}$ ,  $g_m = 4 \text{ mA/V}$ ,  $R_L' = 3.33 \text{ k}\Omega$ .

- a) Determine the mid-band gain,  $A_v = v_o/v_i$ .
- b) Determine the bandwidth of the circuit.