
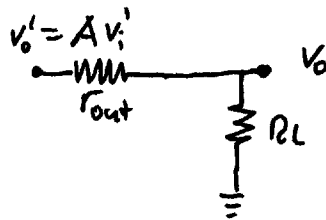


Mid frequencies : no capacitor limits the gain

C_s, C_L : short circuit (HPF)

C_f, C_i, C_o : open circuit (LPF)

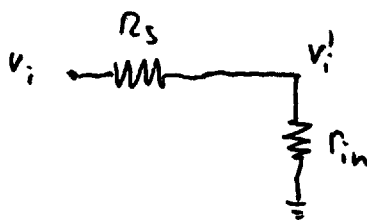

$$R_s = 1 \text{ k}\Omega$$

$$R_L = 3 \text{ k}\Omega$$


$$r_{in} = 5 \text{ k}\Omega$$

$$r_{out} = 1 \text{ k}\Omega$$

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v'_o} \cdot \frac{v'_o}{v'_i} \cdot \frac{v'_i}{v_i}$$

$$= \frac{R_L}{R_L + r_{out}} \cdot A \cdot \frac{r_{in}}{r_{in} + R_s} = \frac{3}{4} \times (-100) \times \frac{5}{6} = -62.5$$


low frequencies
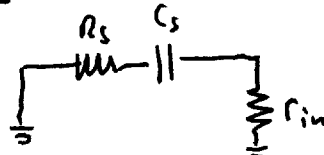
$$\tau_s =$$


$$= C_s \times (R_s + r_{in})$$

$$= 10 \mu\text{F} \times (1 \text{ k}\Omega + 5 \text{ k}\Omega)$$

$$= 60 \text{ ms}, f_s = \frac{1}{2\pi\tau_s} = 2.65 \text{ Hz}$$
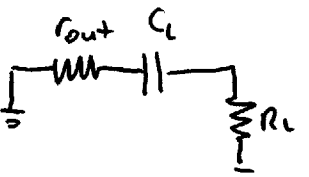
$$\tau_L =$$


$$= C_L \times (r_{out} + R_L)$$

$$= 10 \mu\text{F} \times (1 \text{ k}\Omega + 3 \text{ k}\Omega)$$

$$= 40 \text{ ms}, f_L = \frac{1}{2\pi\tau_L} = 4.0 \text{ Hz}$$

$$\frac{1}{\tau_{tot}} = \frac{1}{\tau_L} + \frac{1}{\tau_S} = \frac{1}{40 \text{ ms}} + \frac{1}{60 \text{ ms}} = \frac{1}{24 \text{ ms}}$$

$$f_{L_{tot}} = \frac{1}{2\pi \tau_{tot}} = f_S + f_L = 6.6 \text{ Hz}$$

High frequencies




$$C_{fM} = (1 - A') \times C_f = 760 \text{ pF}$$

$$C_{fM}' = (1 - \frac{1}{A'}) \times C_f = 10.13 \text{ pF}$$

$$A' = -100 \times \frac{R_L}{R_L + r_{out}} = -75$$

(see drawing)

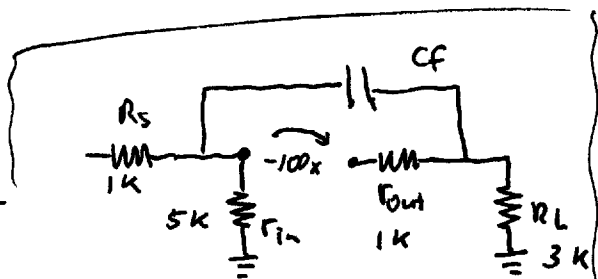

$$\tau_{in} = (C_{fM} + C_i) \times R_S \parallel r_{in} = 770 \text{ pF} \times (1 \text{ k}\Omega \parallel 5 \text{ k}\Omega) = 6.42 \times 10^{-7} \text{ s}$$

$$f_{in} = \frac{1}{2\pi \tau_{in}} = 248 \text{ kHz}$$

$$\tau_{out} = (C_{fM}' + C_o) \times (r_{out} \parallel R_L) = 20.1 \text{ pF} \times (1 \text{ k}\Omega \parallel 3 \text{ k}\Omega) = 1.5 \times 10^{-8} \text{ s}$$

$$f_{out} = \frac{1}{2\pi \tau_{out}} = 10.5 \text{ MHz}$$

$$f_{total, H} = \frac{1}{2\pi (\tau_{in} + \tau_{out})} = 242 \text{ kHz} \quad (\approx f_{in})$$

c) band width: $\Delta f = 242 \text{ kHz} - 6.6 \text{ Hz}$

