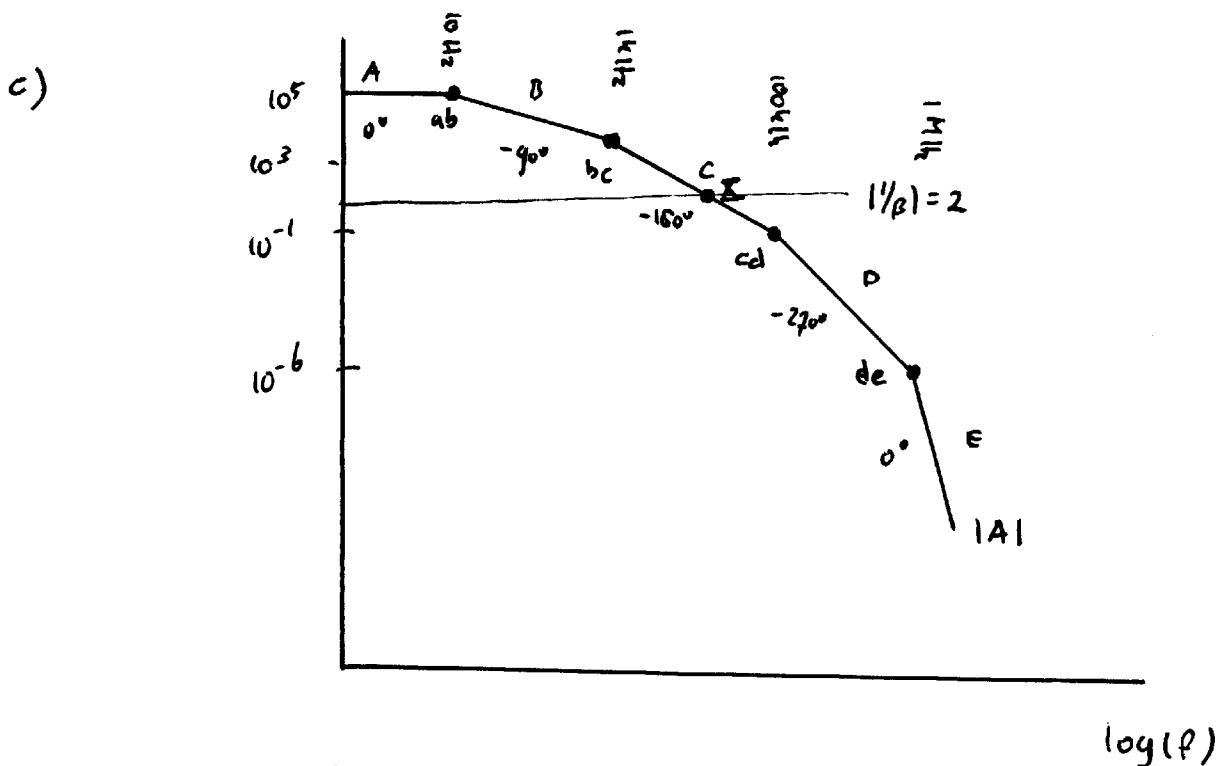



b) $A = 10^5, \beta = 0.5 \Rightarrow \frac{v_o}{v_i} = \frac{10^5}{1 + 10^5 \cdot 0.5} = \frac{10^5}{50001} \approx 2$




Summary :

A	0°	~ 1	⇒ 10 ⁵
ab	-45°	10 Hz	⇒ 10 ⁵
B	-90°	~ 1/f	⇒ 10 Hz × 10 ⁵ / f
bc	-135°	1 kHz	⇒ 10 ³
C	-180°	~ 1/f ²	⇒ (1 kHz) ² × 10 ³ / f ²
cd	-225°	100 kHz	⇒ 10 ⁻¹
D	-270°	~ 1/f ³	⇒ (100 kHz) ³ × 10 ⁻³ / f ³
de	-315°	1 MHz	⇒ 10 ⁻⁶
E	0°	~ 1/f ⁴	⇒ (1 MHz) ⁴ × 10 ⁻⁶ / f ⁴

It is immediately clear that the crossing point of $|A|$ and $1/|\beta|$ occurs at a frequency between 1 kHz and 100 kHz, and the phase is -180° at this point.

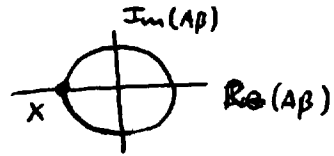

More or less at the Barkhausen point.

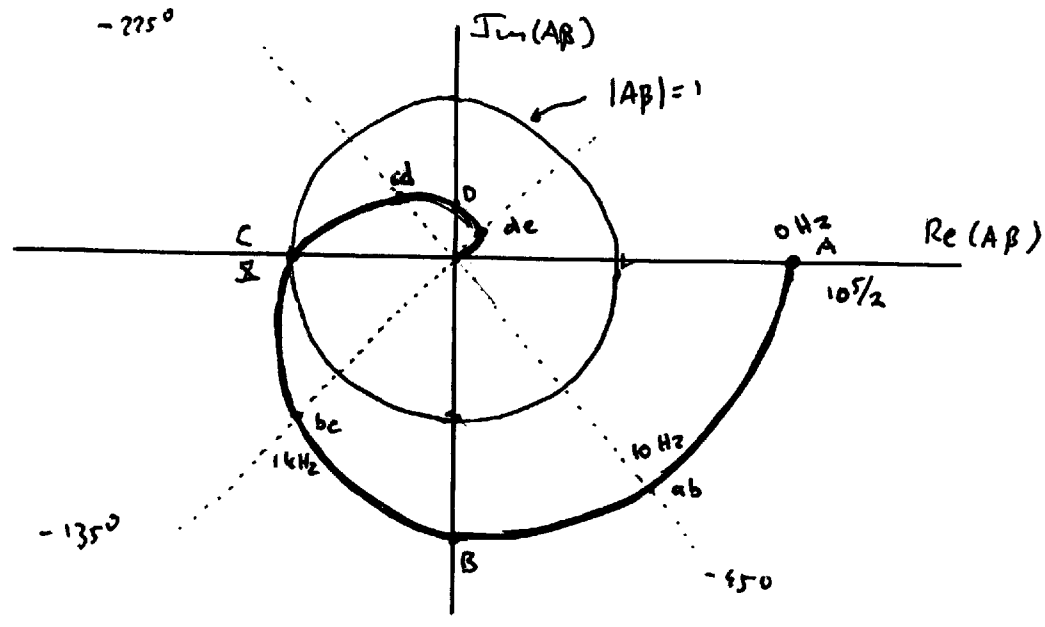

Analyzing the Nyquist plot above, it is clear that the circuit can (and will) oscillate in the frequency range $bc - X$

X can be found by the equation for line segment C

$$|A| = \frac{(1 \text{ kHz})^2 \times 10^3}{f^2} = 1/|\beta| = 2$$

$$f = \sqrt{\frac{(1 \text{ kHz})^2 \times 10^3}{2}} = 22,4 \text{ kHz}$$

d) For this effect the $1/\beta$ line has to pass through the second pole (bc). For that we can use line segment B

$$|A| = \frac{10 \text{ Hz} \times 10^5}{f}$$

In bc (1 kHz) this gives

$$|A| = \frac{10 \text{ Hz} \times 10^5}{1 \text{ kHz}} = 10^3 = 1/\beta \Rightarrow$$

$$\beta = \frac{1}{1000}$$

e)

