

Electronics



UAlg
2011

MIEET

1^o ano




UAlg

UNIVERSIDADE DO ALGARVE





Peter Stallinga, UAlg 2011



MIEET. The levels of knowledge

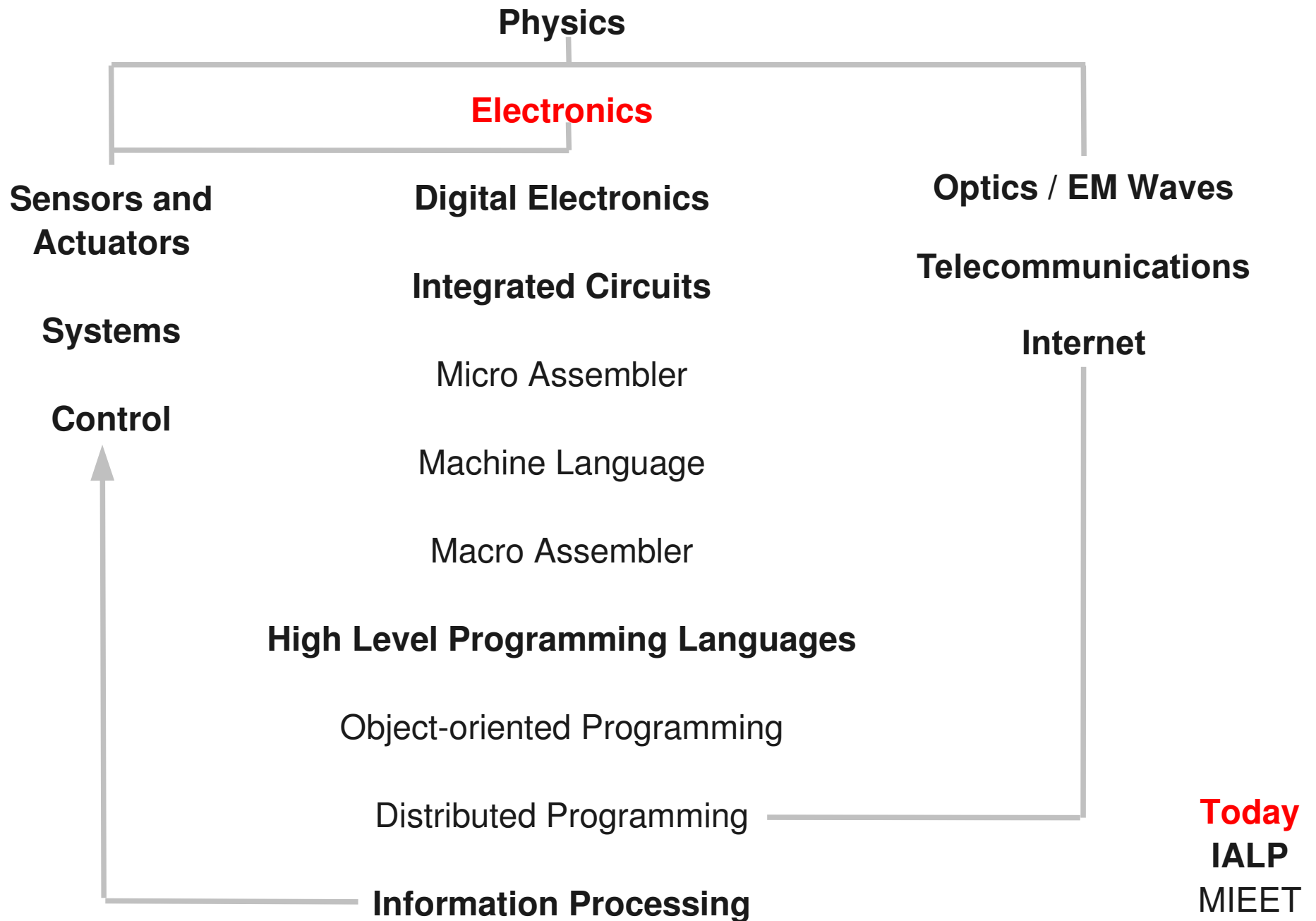


Current - Voltage

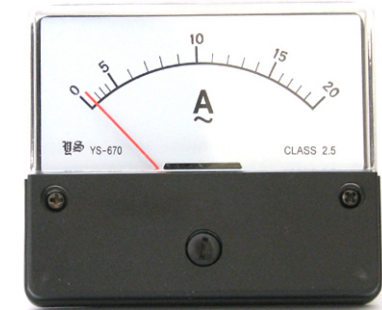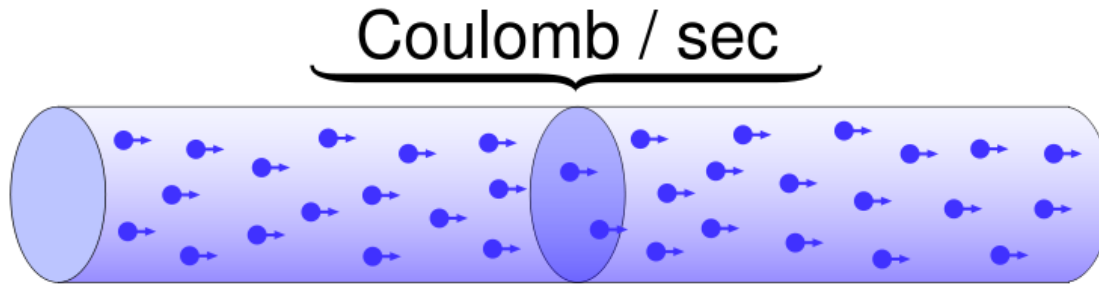

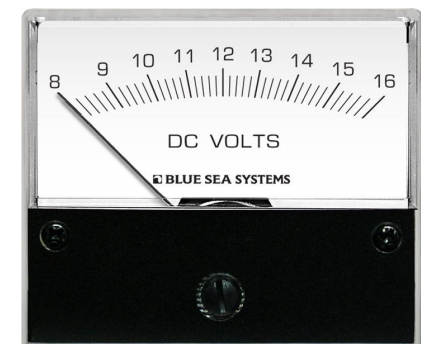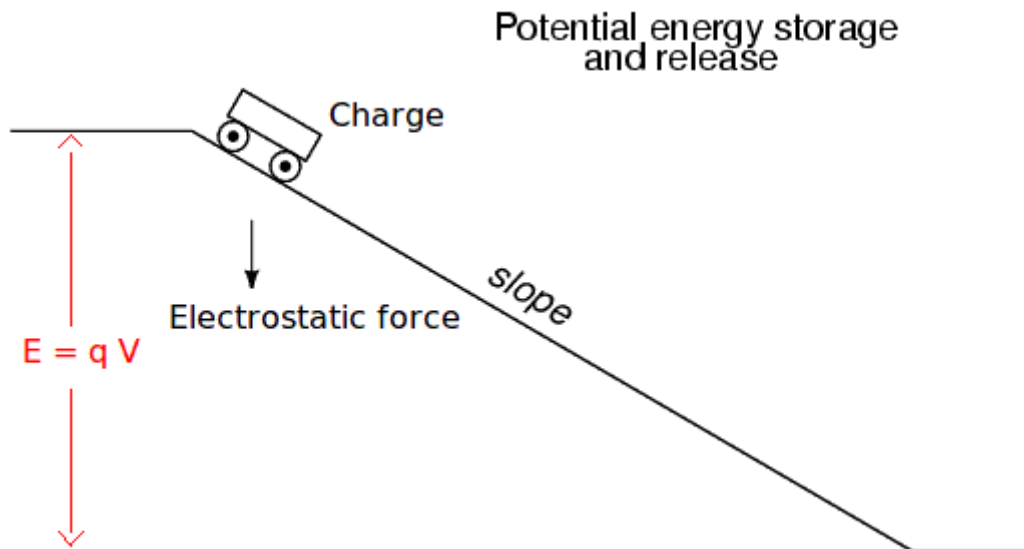
Current is the passage of charge
Voltage is the potential energy



Power

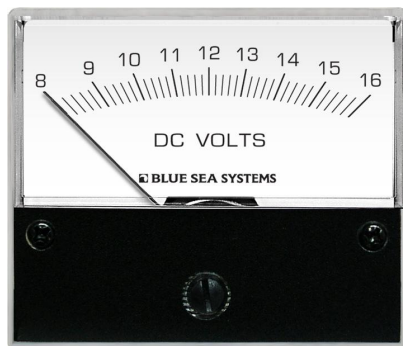

X

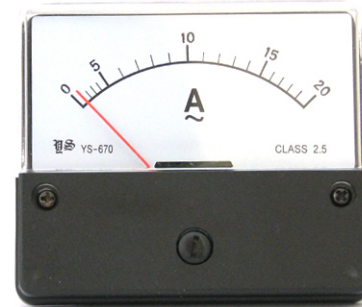

=



$$V \times I = P$$

Ohm's Law

Linear relation between voltage (V) and current (I)




$$R = V / I$$

$$V = R \times I$$

$$I = V / R$$

Ohm's Triangle

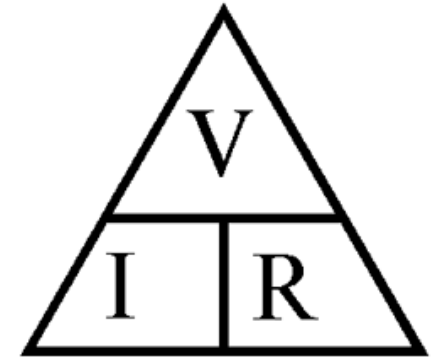

Cover the variable you want to find and perform the resulting calculation (*Multiplication/Division*) as indicated.


Resistance is the ability of an object to 'resist' the flow of current. Like 'friction'. Slows down the charge and ($I = n \times v$) reduces the current

The current is proportional to applied power divided by resistance


Power, current, voltage, resistance

$$R = V / I$$



$$P = V \times I$$

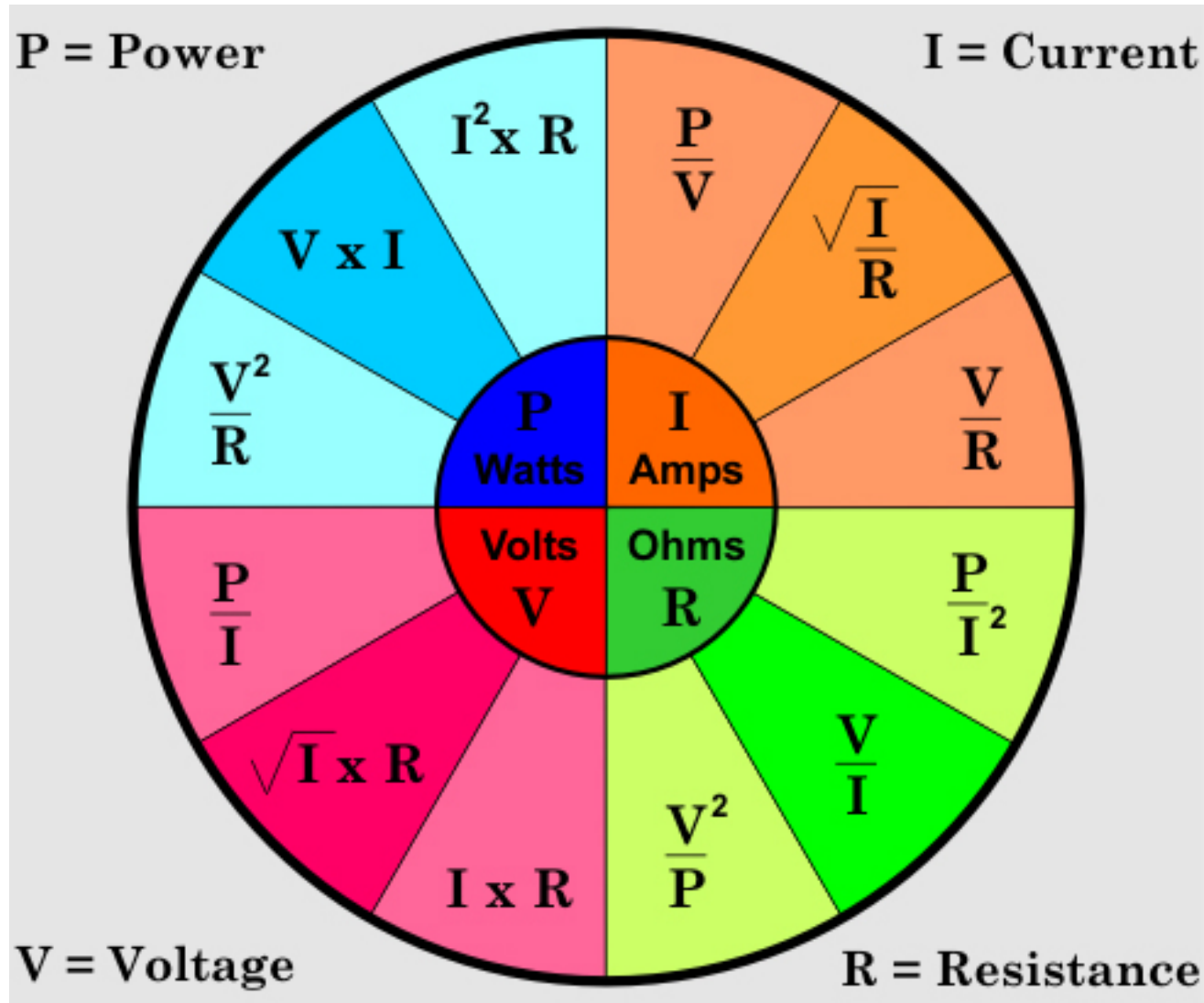



Symbols for electronic components

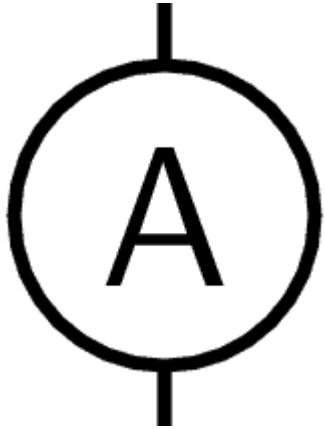

Amperimeter

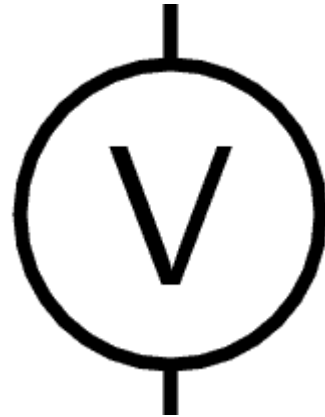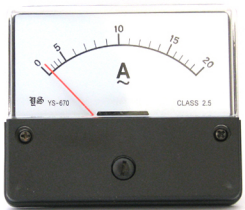


Voltmeter

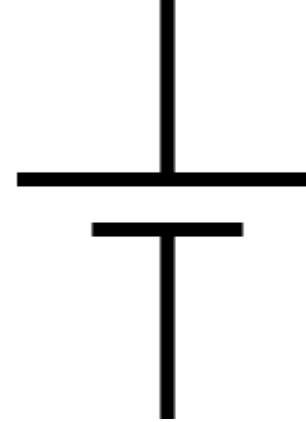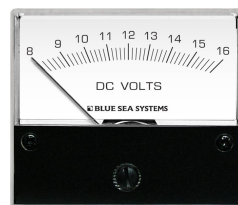



Voltage source



Resistance

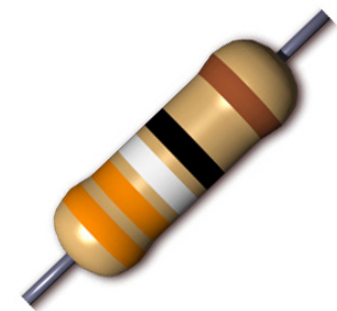

Measuring

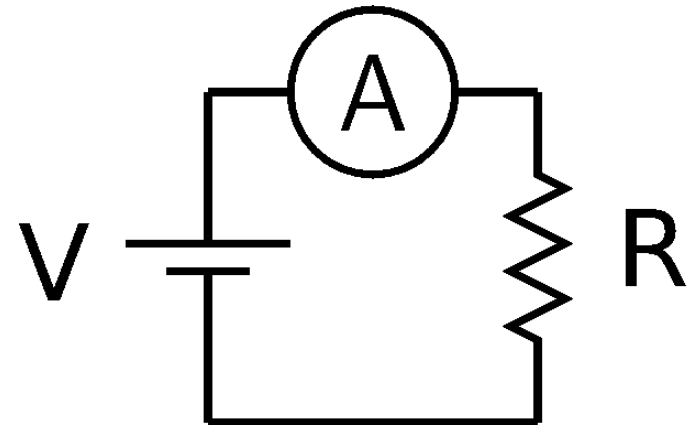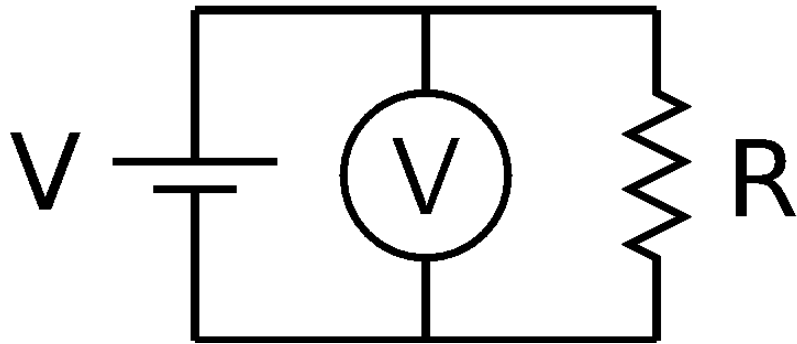

Applying a voltage to a resistance

Measuring voltage and current.



For the measuring of current we have to open the circuit and insert the amperimeter

Notes:

The voltmeter has infinite resistance ($I = V/R = 0$)

The current meter has zero resistance ($V = I \times R = 0$)

Measuring example

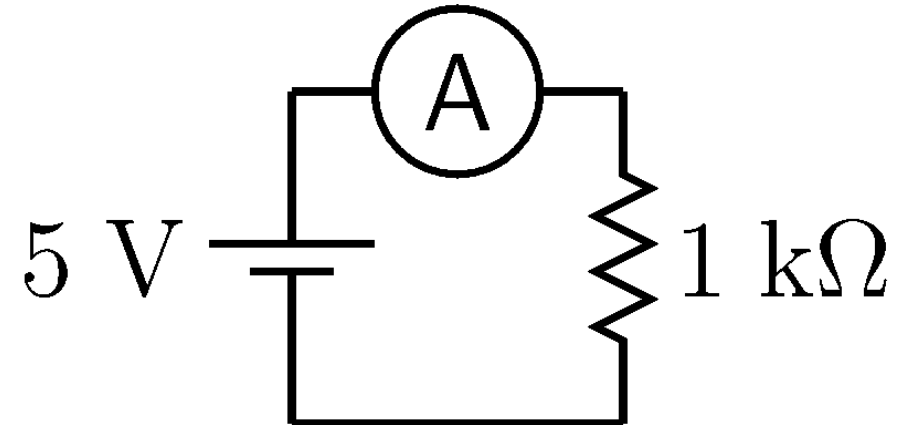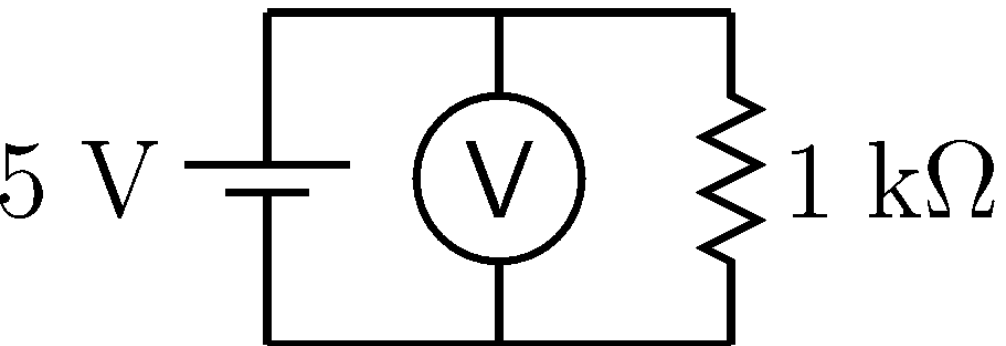




Example:

Voltmeter will indicate 5 V

Current meter will indicate 5 mA, because $(5 \text{ V}) / (1 \text{ k}\Omega) = 0.005$

The resistance is $R = (5 \text{ V}) / (5 \text{ mA}) = 1 \text{ k}\Omega$




Measuring with a multimeter

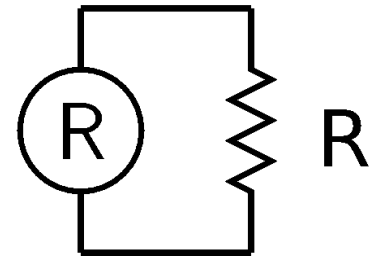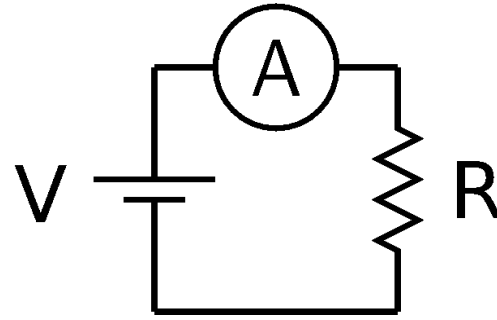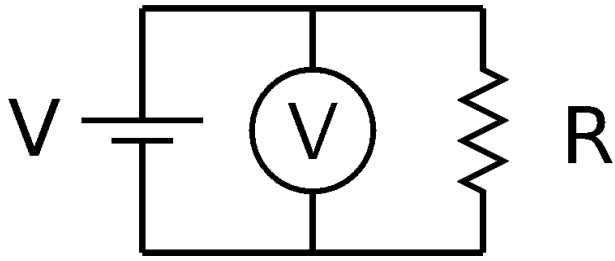

A multimeter can directly measure resistance
(apply voltage, measure current and do the calculation)

A multimeter can also (still) measure current and voltage


Multimeter

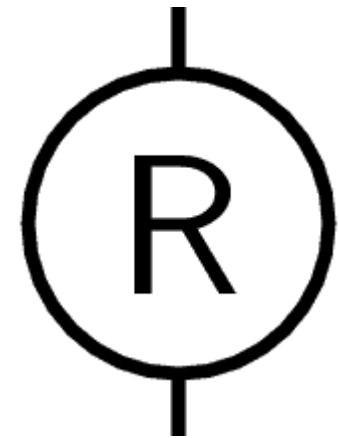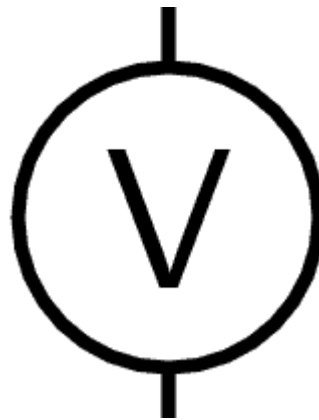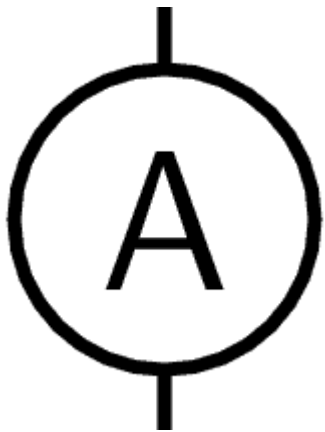

... and more (β , C, f, AC/DC)

Wrong connection

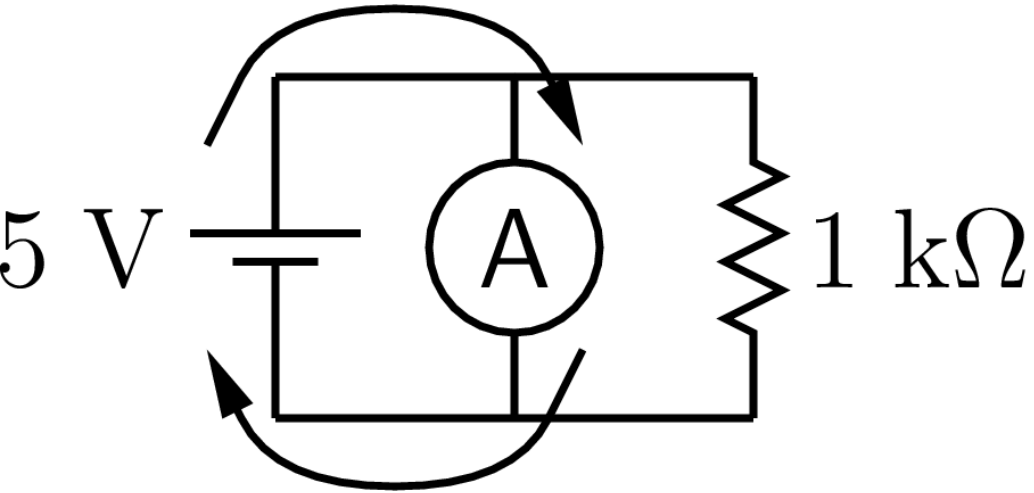
An amperimeter in the place of a voltmeter:



The current meter has zero resistance

$$I = V / R = (5 \text{ V}) / (0) = \infty$$

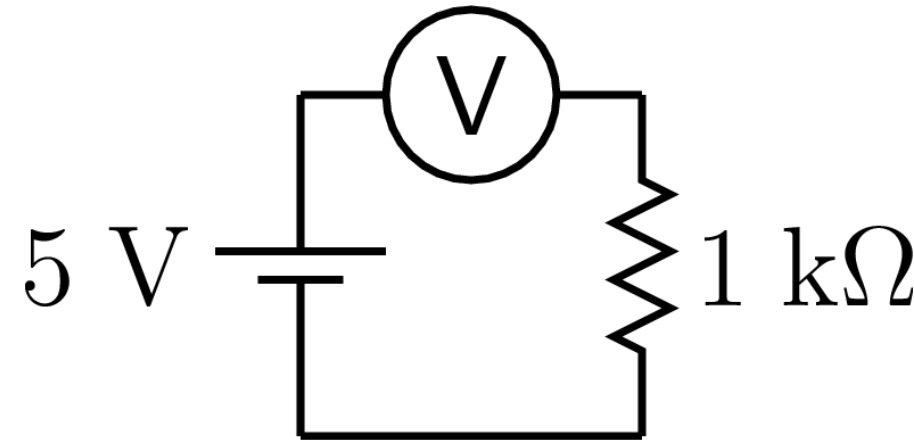A voltmeter in the place of an amperimeter:



The voltmeter has infinite resistance

$$I = V / R = (5 \text{ V}) / (\infty) = 0$$




You just nuked the multimeter!

Kirchhoff's Circuit Laws (KCL)

1: Kirchhoff's Law of Loops

Going back to same place (closed loop) means same energy potential (V)

$$\sum \Delta V = 0$$

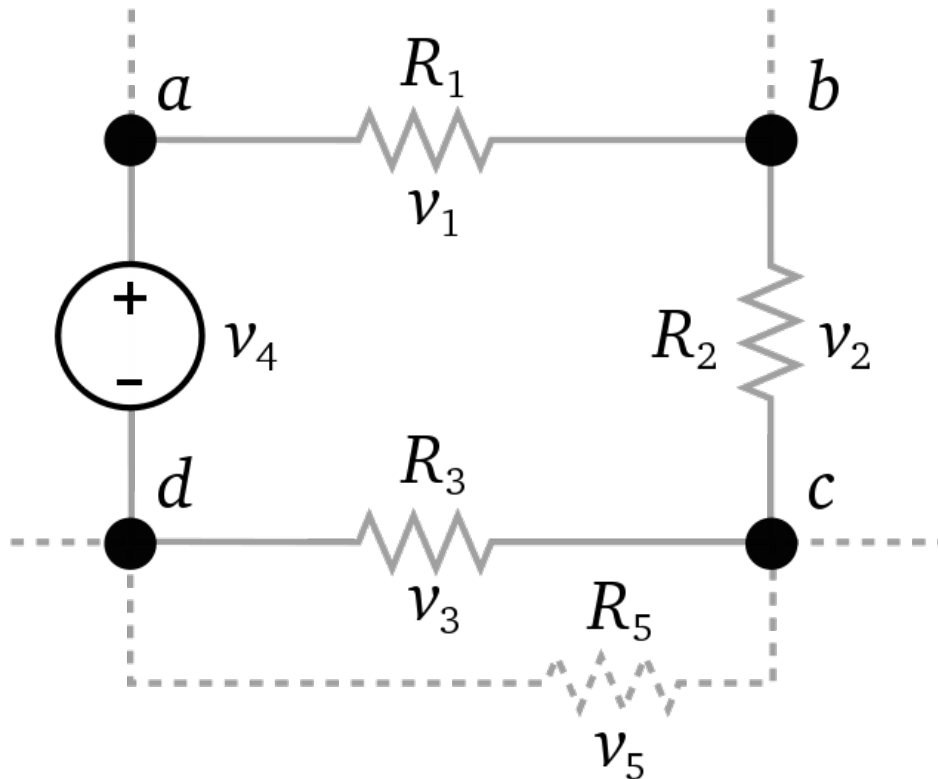


Walking from $a \rightarrow b \rightarrow c \rightarrow d \rightarrow a$
We must return to same potential.



Kirchhoff's Circuit Laws (KCL)


2: Kirchhoff's Law of Junctions

$$\sum \Delta I = 0$$

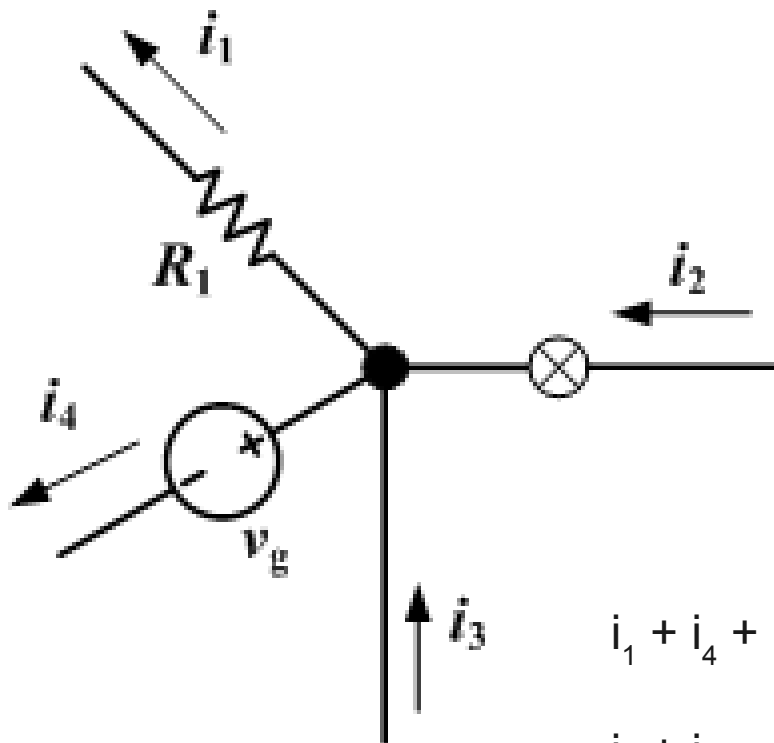

$$i_1 + i_4 + (-i_2) + (-i_3) = 0$$


$$i_1 + i_4 = i_2 + i_3$$

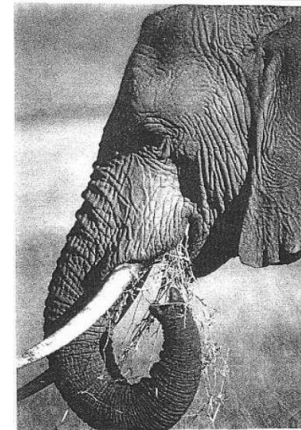

“What goes in, must come out”

Cannot accumulate charge!


Series / parallel

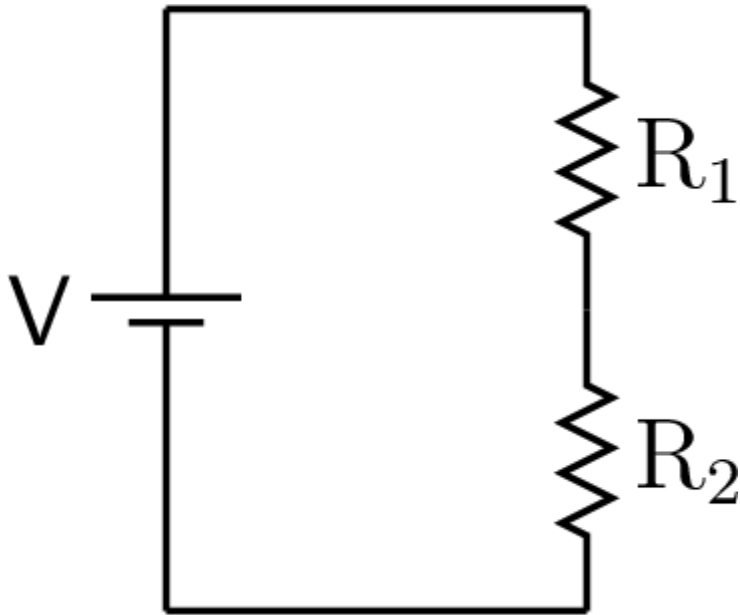

What will be the effective resistance of two resistances 'in series'?


Calculate the current and use Ohm's Law $R = V / I$

Series / parallel

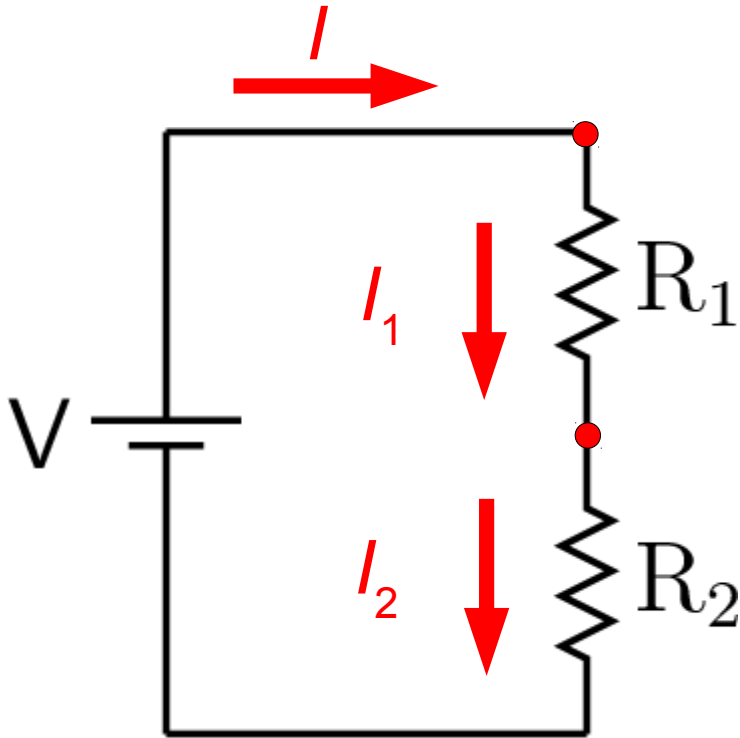

Kirchhoff: $I_1 = I_2 = I$

Series / parallel

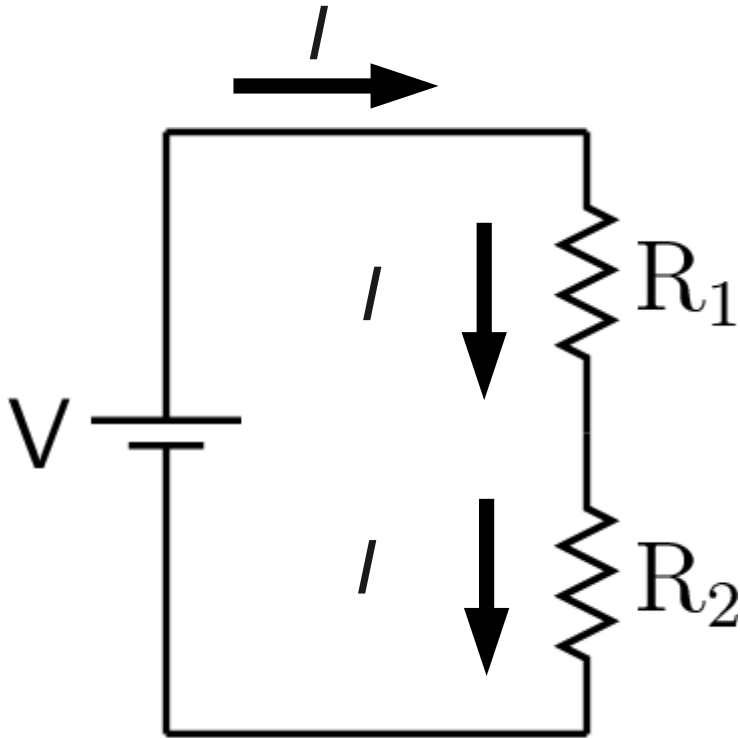

Kirchhoff: $I_1 = I_2 = I$

Ohm: $V = I \times R$

Kirchhoff: sum of $\Delta V = 0$

$$\Delta V_1 = I \times R_1$$


$$\Delta V_2 = I \times R_2$$

$- V$

 +

$$I \times R_1 + I \times R_2 - V = 0$$

Series / parallel

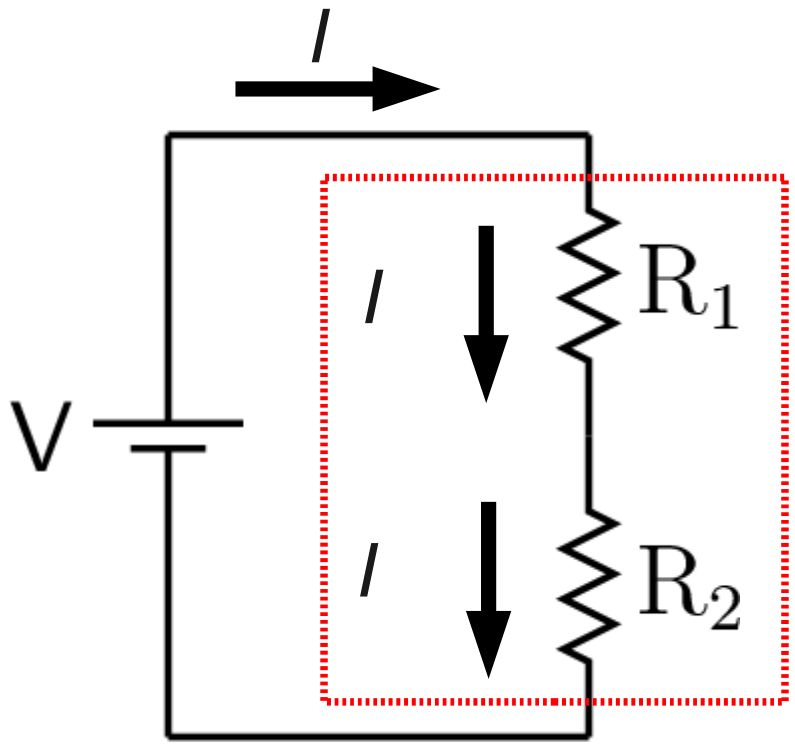

Kirchhoff: $I_1 = I_2 = I$

Ohm: $V = I \times R$

Kirchhoff: sum of $\Delta V = 0$

$$\Delta V_1 = I \times R_1$$


$$\Delta V_2 = I \times R_2$$

$$I \times R_1 + I \times R_2 - V = 0$$

Series:

$$V = I \times (R_1 + R_2)$$
$$R = V / I = R_1 + R_2$$


Series / parallel

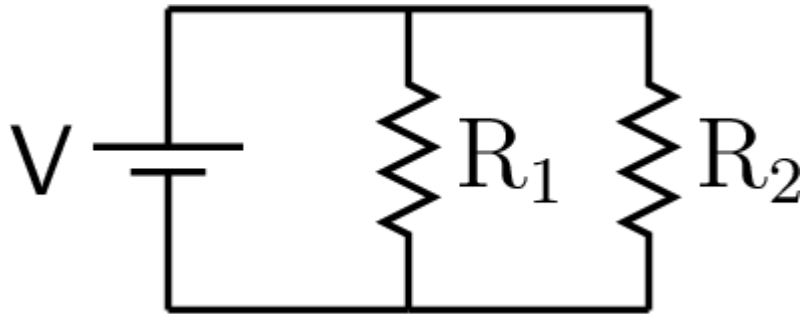

What will be the effective resistance of two resistances 'in parallel'?



Calculate the current and use Ohm's Law $R = V / I$

Series / parallel

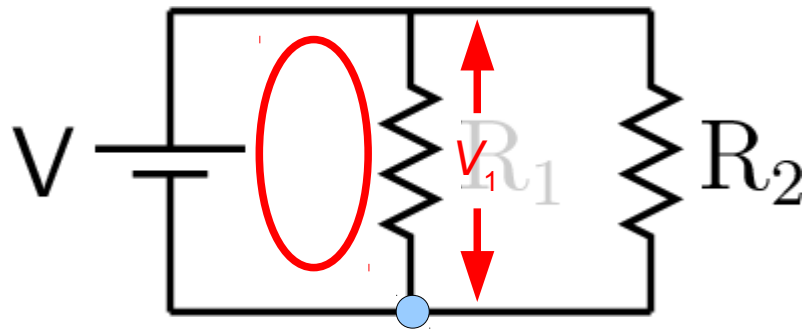


Kirchhoff's Law Loops:

$$V_1 + (-V) = 0:$$
$$V_1 = V$$

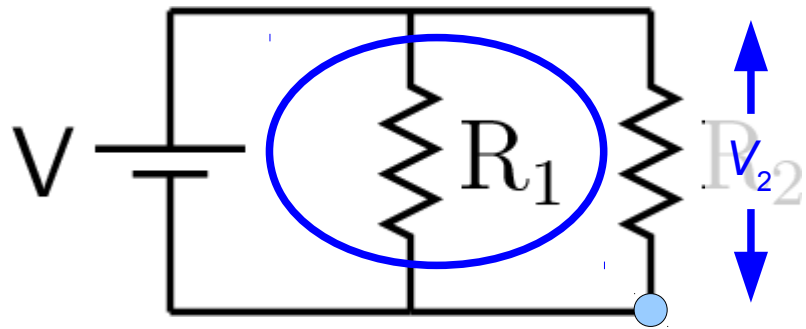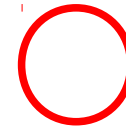


$$V_2 + (-V) = 0:$$
$$V_2 = V$$

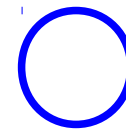


Series / parallel

Ohm's Law:

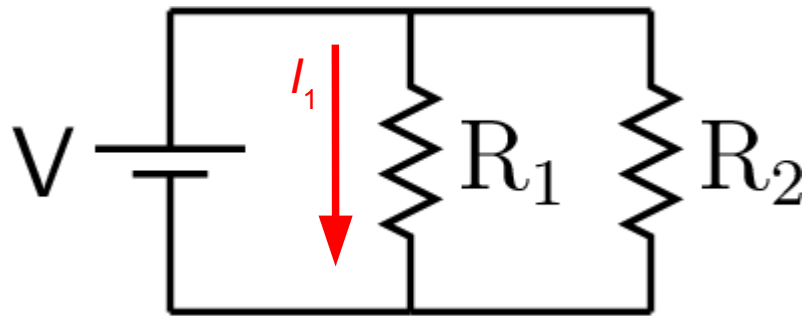


$$I_1 = V / R_1$$

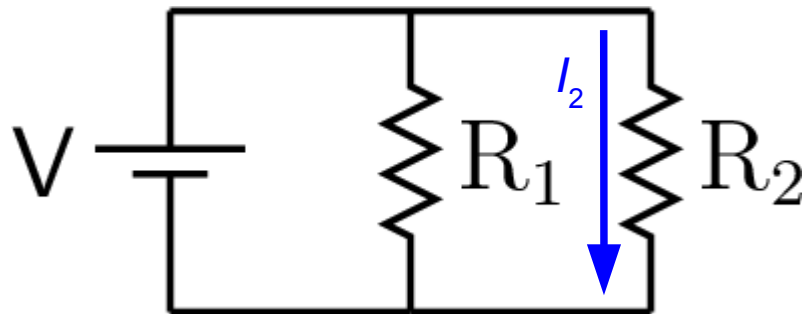

$$I_2 = V / R_2$$

Series / parallel

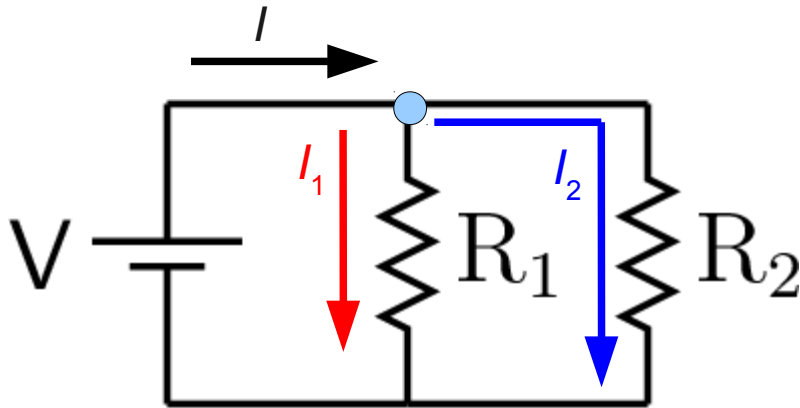

Ohm's Law:

$$I_1 = V / R_1$$

$$I_2 = V / R_2$$

Kirchhoff's Junction Law:

$$I = I_1 + I_2 = V / R_1 + V / R_2$$

Ohm's Law: $R = V / I =$

$$\frac{V}{V / R_1 + V / R_2}$$


$$\text{Parallel:}$$
$$= (1/R_1 + 1/R_2)^{-1}$$

$$= \frac{R_1 R_2}{R_1 + R_2}$$


(only for case with two resistors!)

Voltage divider

What is the voltage halfway?

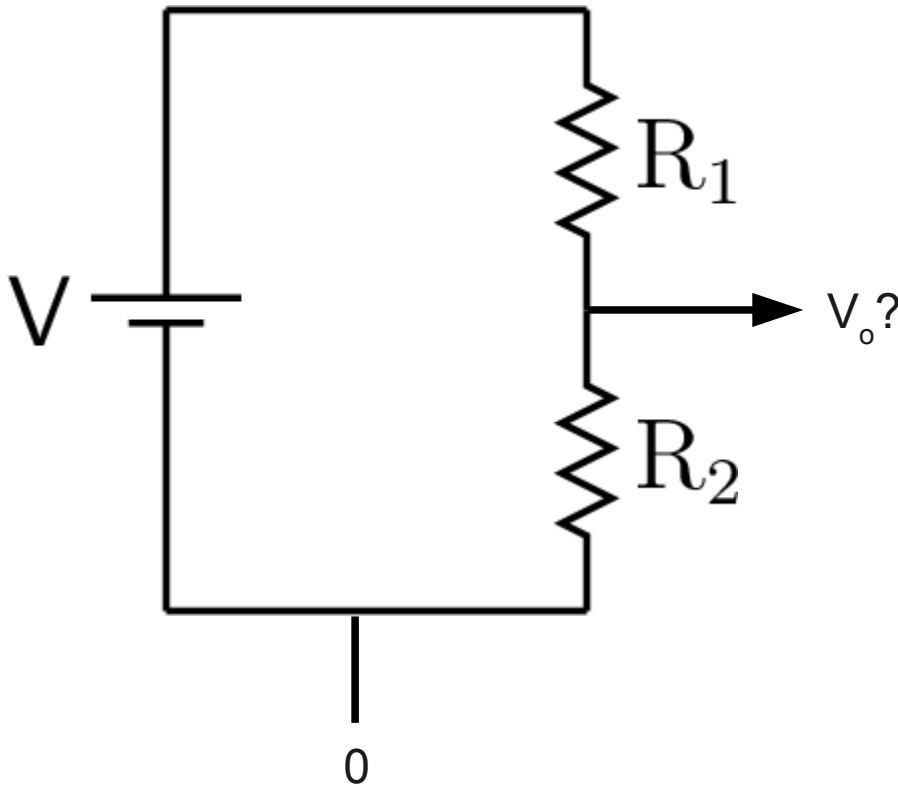

Voltage divider

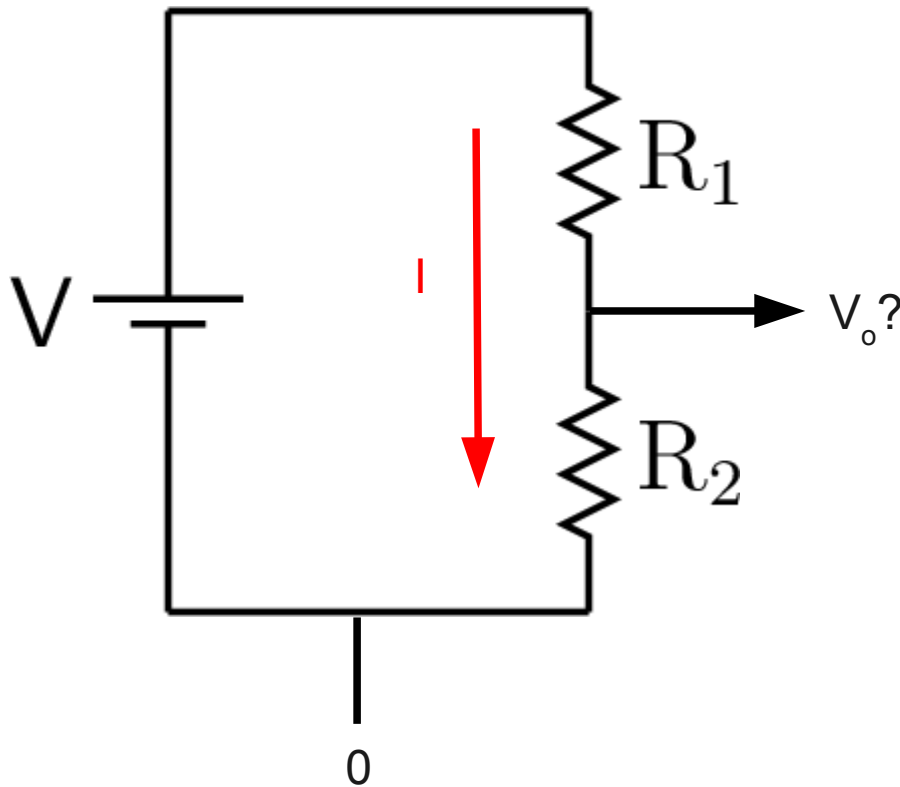


What is the voltage halfway?

Resistances in series: $R = R_1 + R_2$

$$I = V / R = V / (R_1 + R_2)$$

Voltage divider

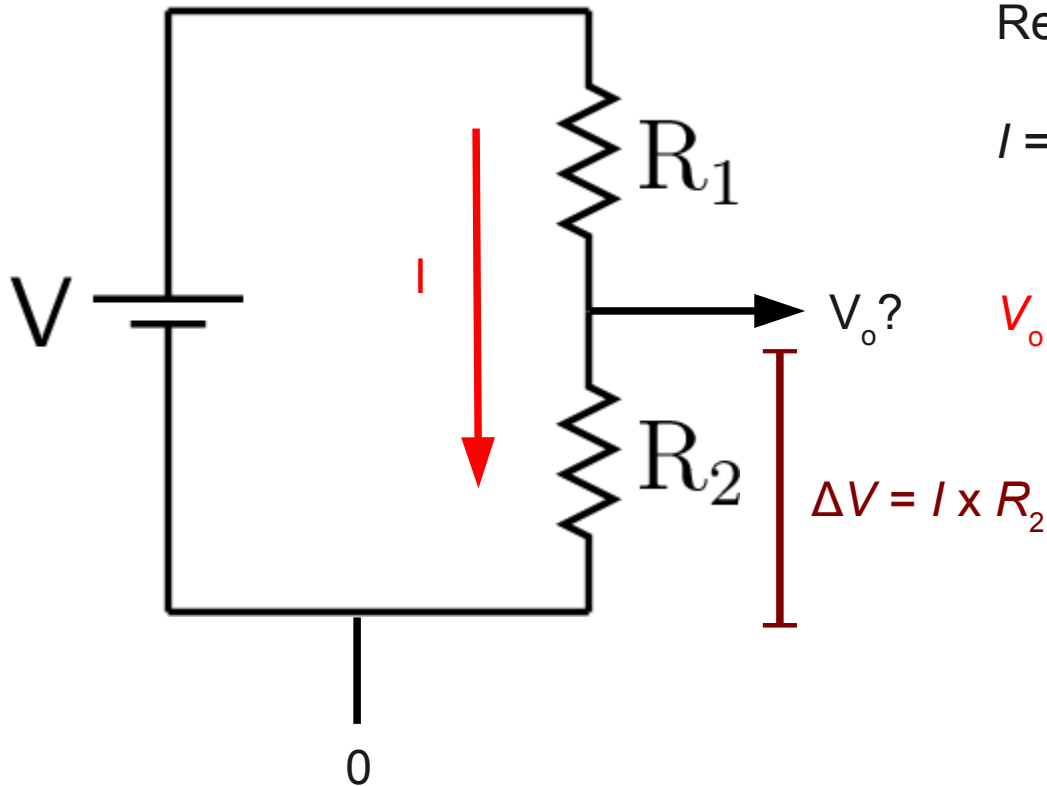

What is the voltage halfway?

Resistances in series: $R = R_1 + R_2$

$$I = V / R = V / (R_1 + R_2)$$

$$V_o = 0 + I \times R_2 = V \frac{R_2}{R_1 + R_2}$$

Non-ohmic

Not everything behaves according to Ohm's Law

A capacitor is an element that has the capacity to **store** charge (instead of letting it pass).

The capacitance is by definition the amount of charge it can store per volt:

$$C = Q/V$$

$$V = Q/C$$

$$Q = C \times V$$



Current of a capacitor

If $Q = C \times V$, then: changes of voltage cause changes of stored charge:

$$\Delta Q = C \times \Delta V$$

How fast we do it matters

$$\Delta Q / \Delta t = C \times \Delta V / \Delta t$$

In the mathematical limit:

$$dQ / dt = C \times dV / dt$$


But, the left side is the **definition of current**

$$I = C \times dV / dt$$

Current in a capacitor is proportional to the speed of changes of the applied voltage



Capacitance example

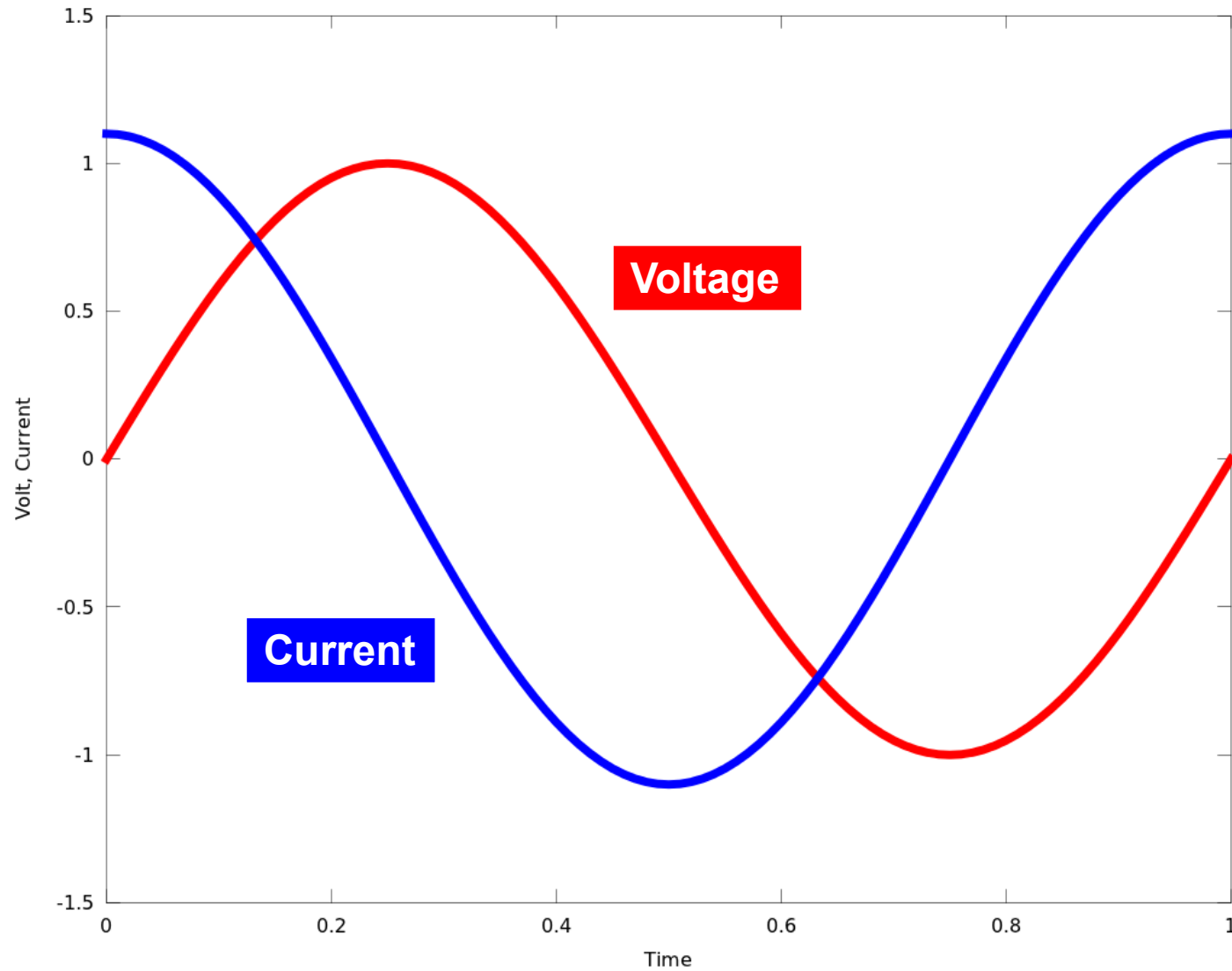


Other components




Coil (inductor)




Diode

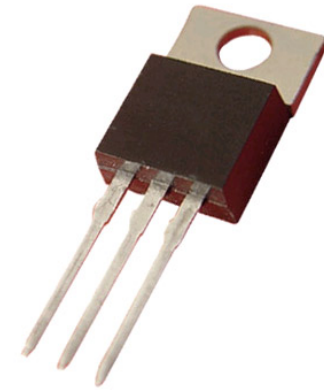

Transistor

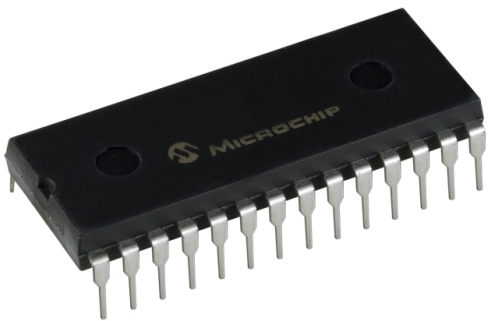

Integrated circuit

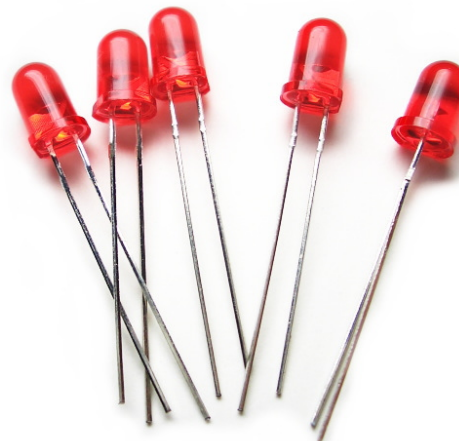

Light-emitting diode
(LED)


Other components



Fuses



Variable resistor /
Potentiometer

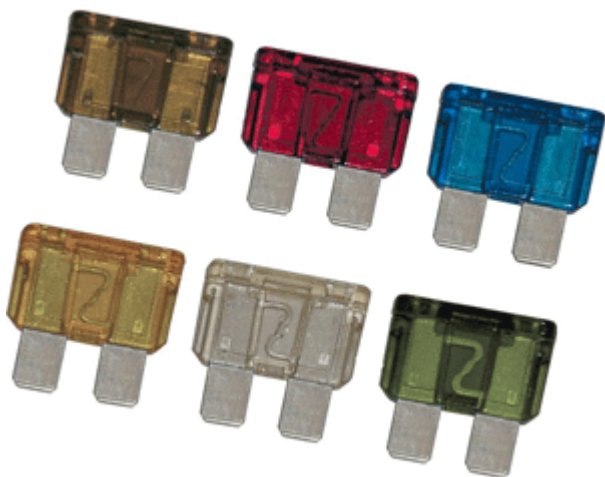

Car fuses



Connector

Other equipment



Variable voltage /
current source




Signal source, $V(t)$



Oscilloscope: Visualize
 $V(t)$

Resistance color code

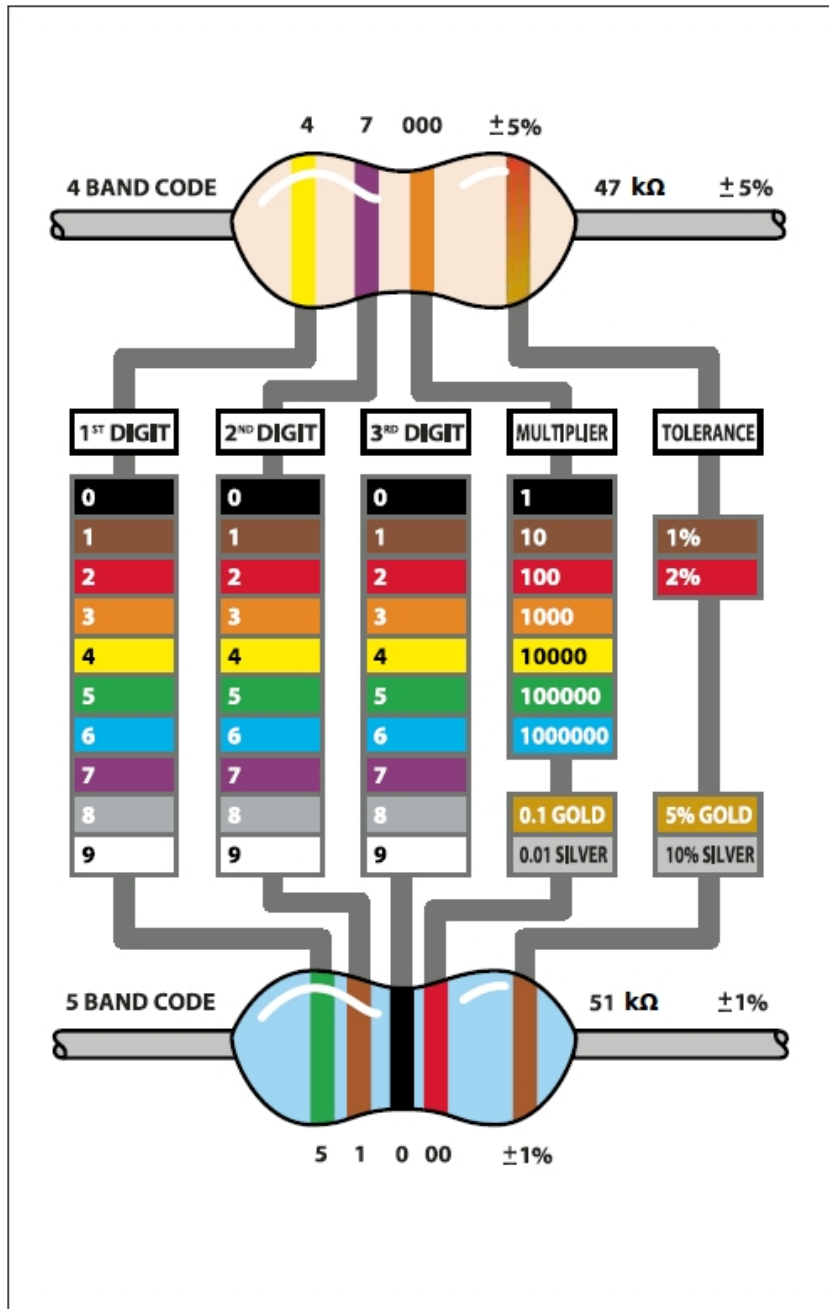

Never again forget this code!