

# Instrumentation




MIEET

1º ano



Peter Stallinga, UAAlg 2011

# MIEET. The levels of knowledge

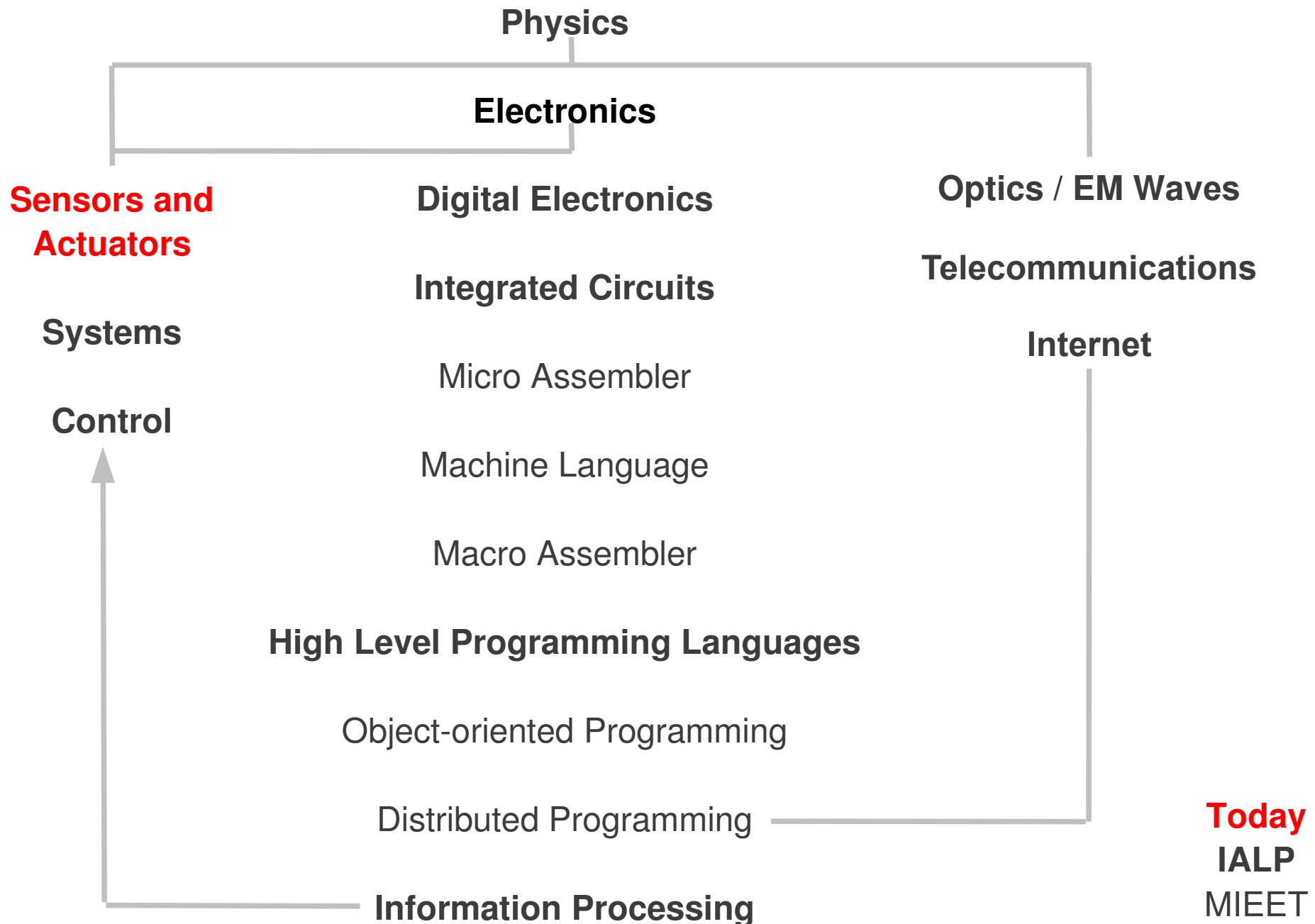

# Instrumentation


Signal Acquisition. Sensors. Actuators

ADC-DAC

# Instrumentation
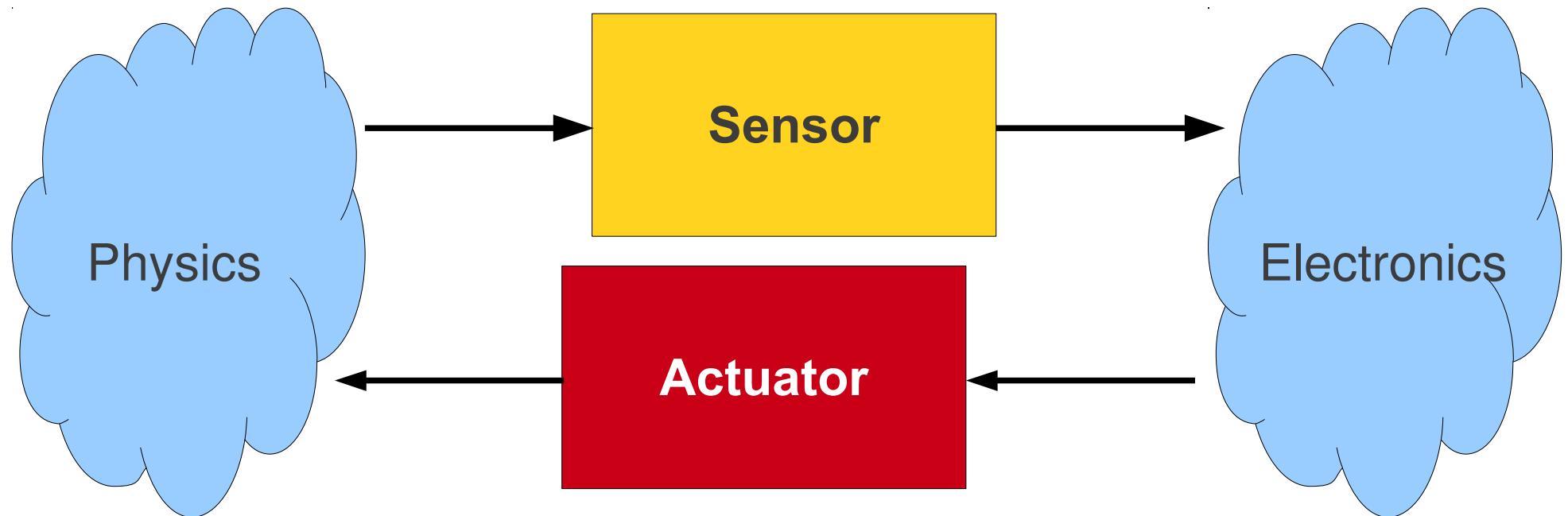
## Transducers: Sensors & Actuators

Translation of information ('signal') from a physical domain to an electronic domain




# Transducers ADC-DAC

ADC (Analog-Digital Converter)

DAC (Digital-Analog Converter)

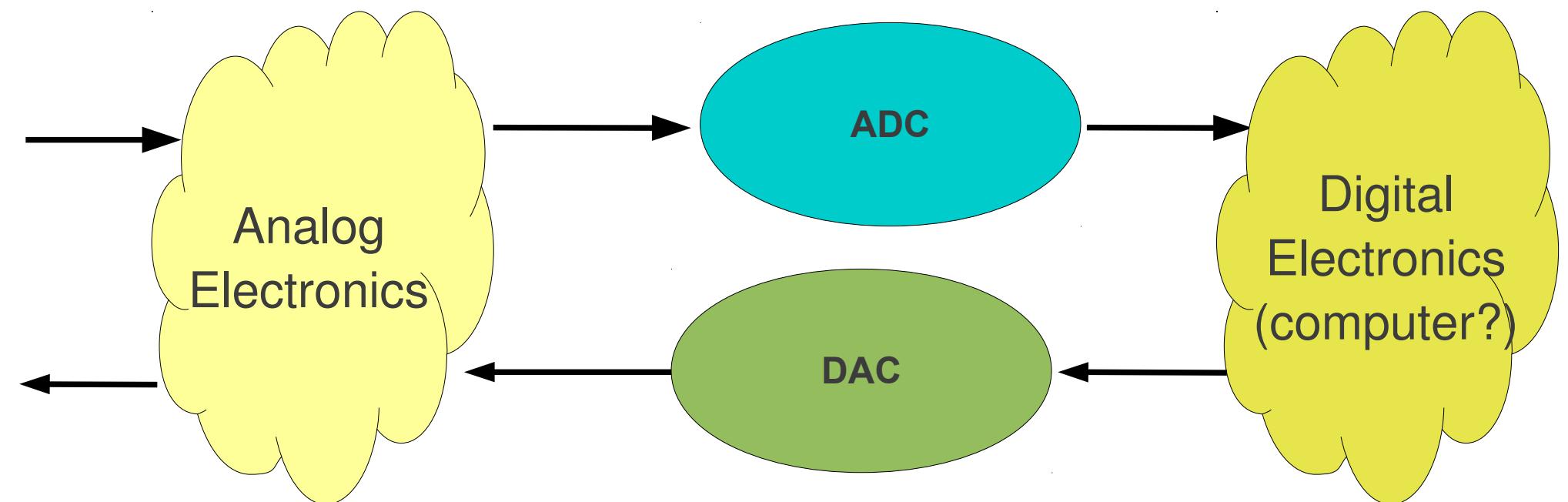Translate signal from **analog** (electronics) to **digital** (electronics) domain and back




# ADC/DAC

ADC (Analog-Digital Converter)

DAC (Digital-Analog Converter)

Translate signal from **analog** (electronics) to **digital** (electronics) domain and back

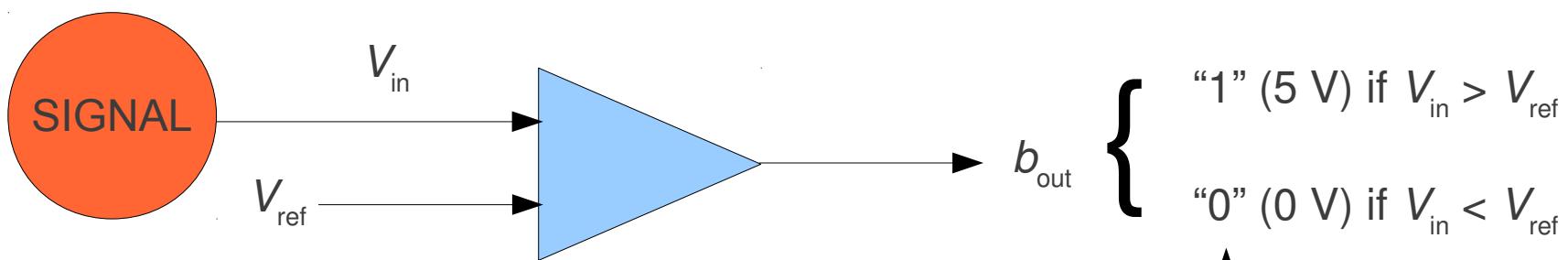

Simple 1-bit ADC:  
comparator


"1" (5 V) if  $V_{in} > V_{ref}$   
"0" (0 V) if  $V_{in} < V_{ref}$

↑

"0" and "1" are  
only **our** (human)  
interpretation

# 1-bit ADC (comparator)


Simple 1-bit ADC:  
comparator

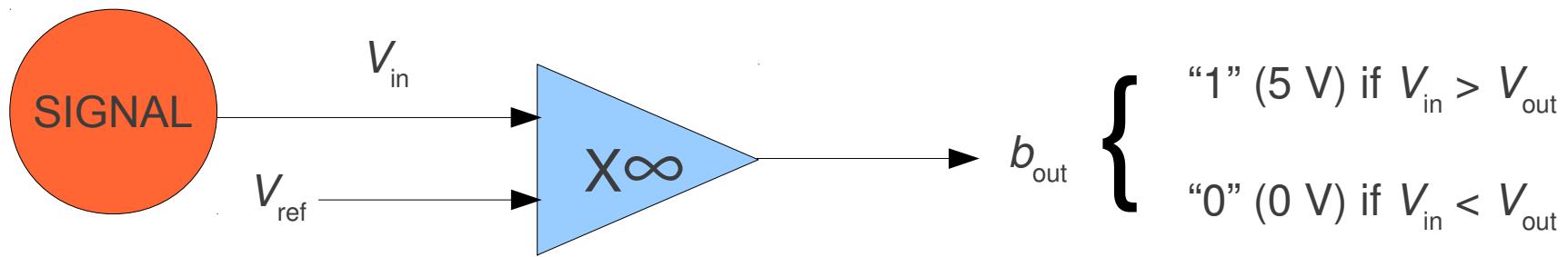


A comparator is an infinite-gain differential amplifier

$$V_{out} = \infty(V_{in} - V_{ref}) = \pm V_{CC}$$

# ADC voltage divider

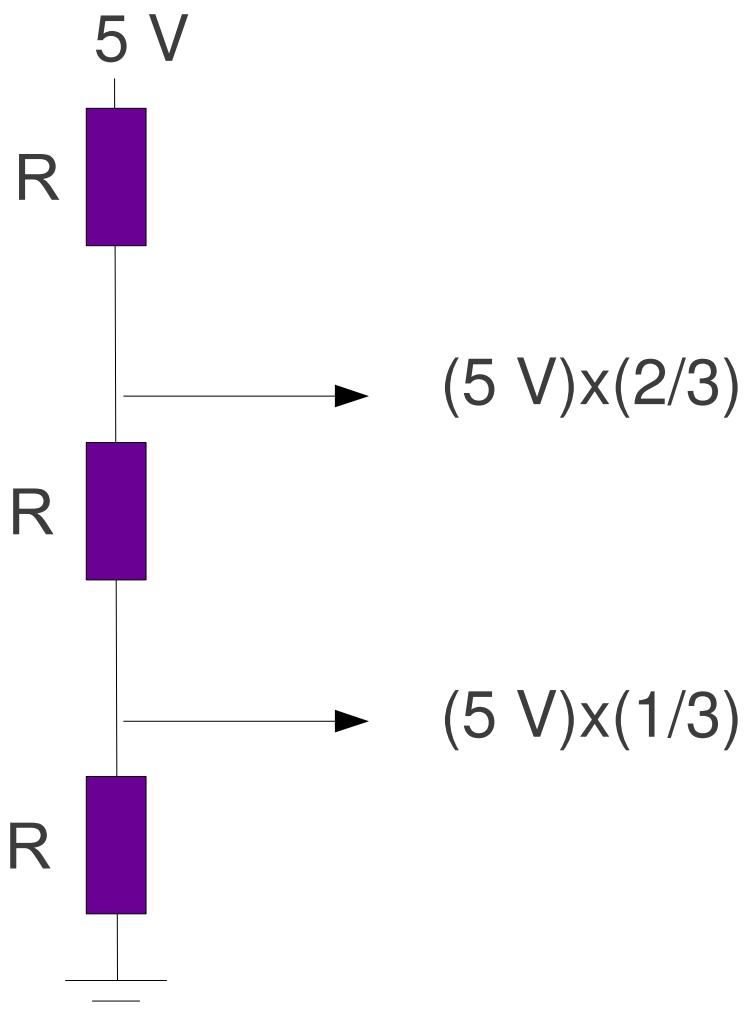

# 2-bit ADC?

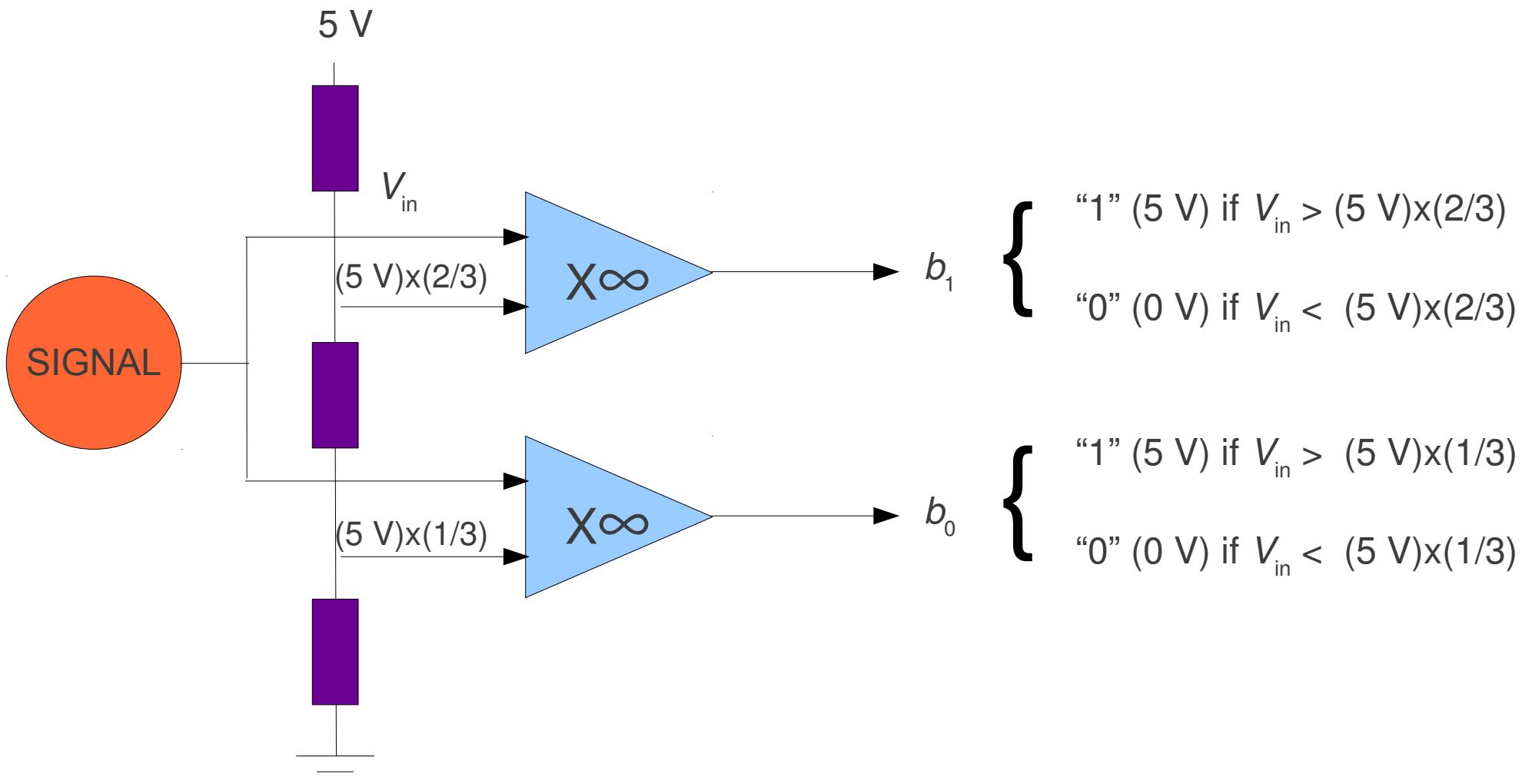


This is **not a 2-bit ADC**: Number of possibilities is not  $2^2 = 4$ :

$b_1 b_0 = 00, 01, 10, 11$  (3 possibilities)

↑  
Not possible!!!

# 2-bit ADC

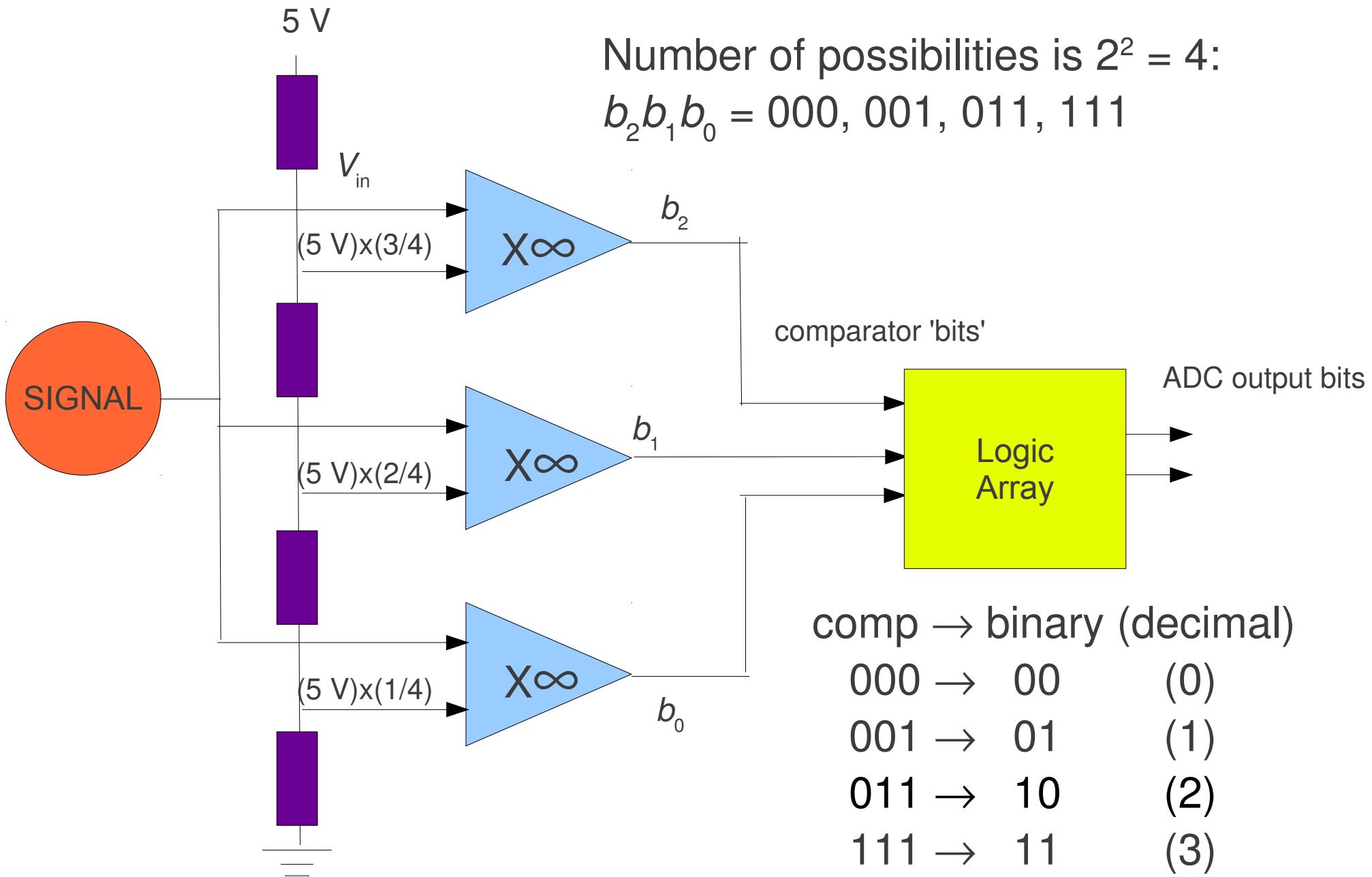

# Sensors & Actuators

## Sensors & Actuators

Translation of information ('signal') from a physical domain to an electronic domain

For example: a resistor

The resistance value of a resistor depends on the temperature  
If we know the resistance value we know the temperature!



PTC: (positive temperature coefficient) resistor, “thermistor”


# An electronic thermometer

Sensor


$$R(T)$$




# An electronic thermometer

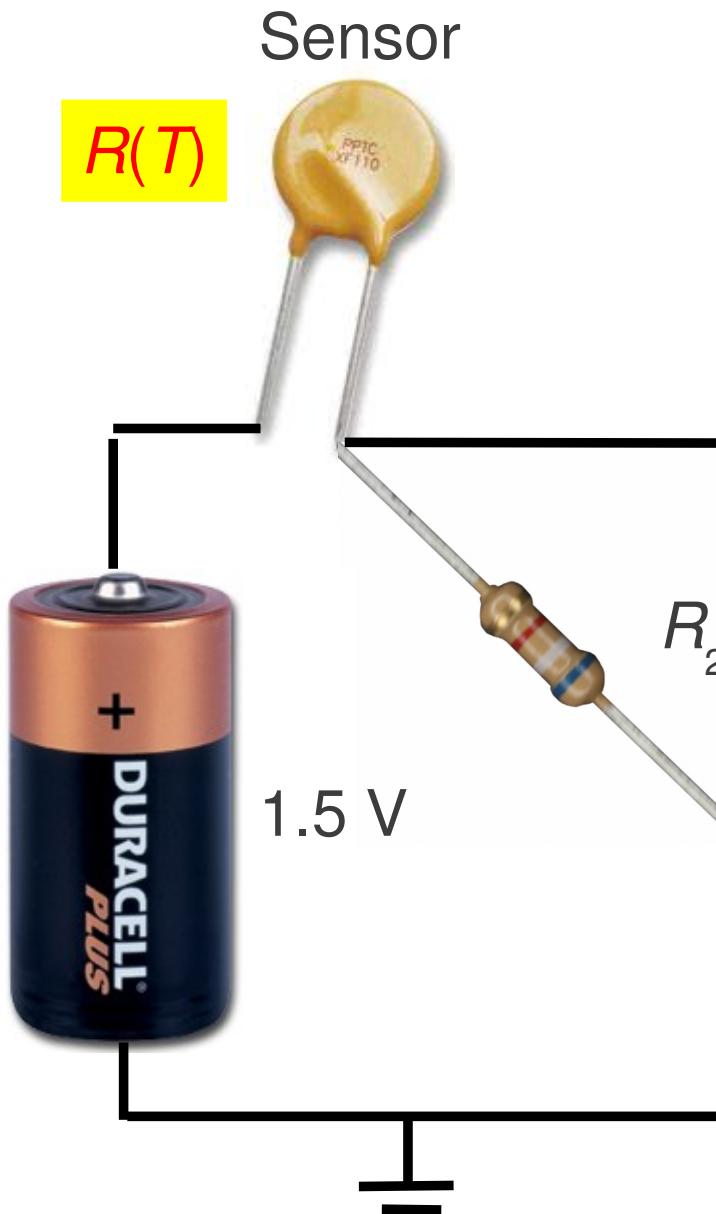

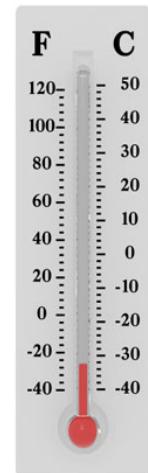
$$V(T) = (1.5 \text{ V}) \times \frac{R_2}{R(T) + R_2}$$



# A system: temperature measurement

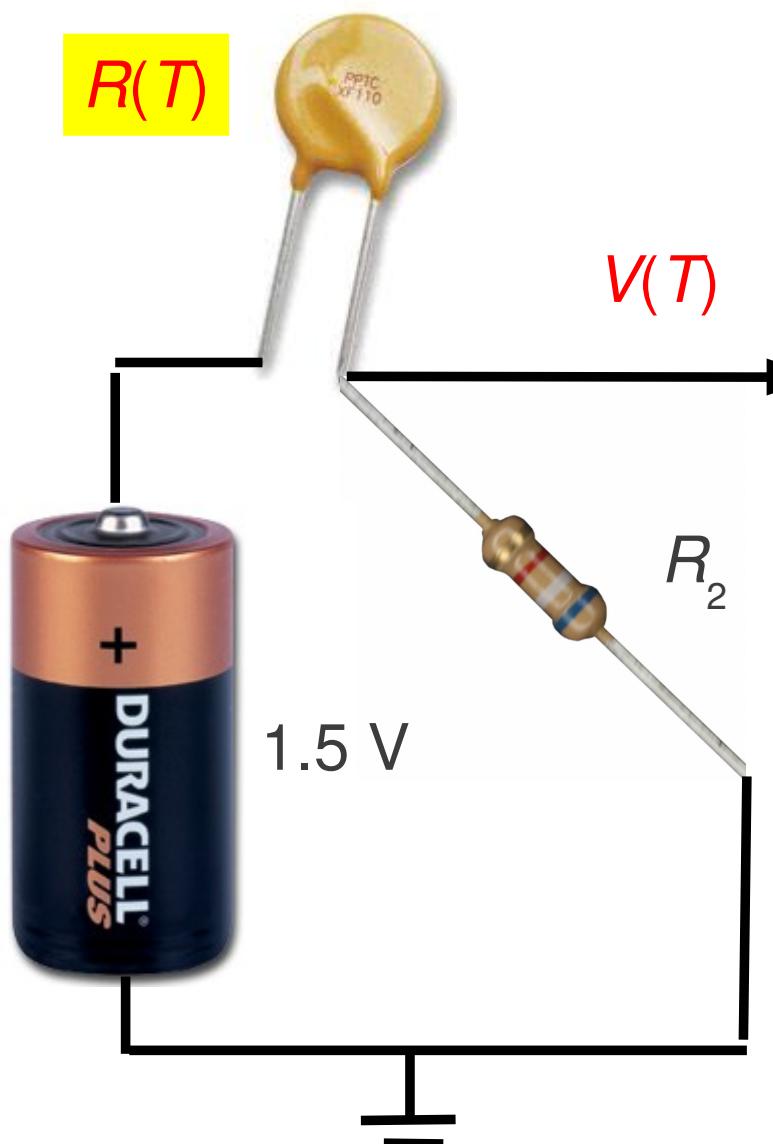

ADC:

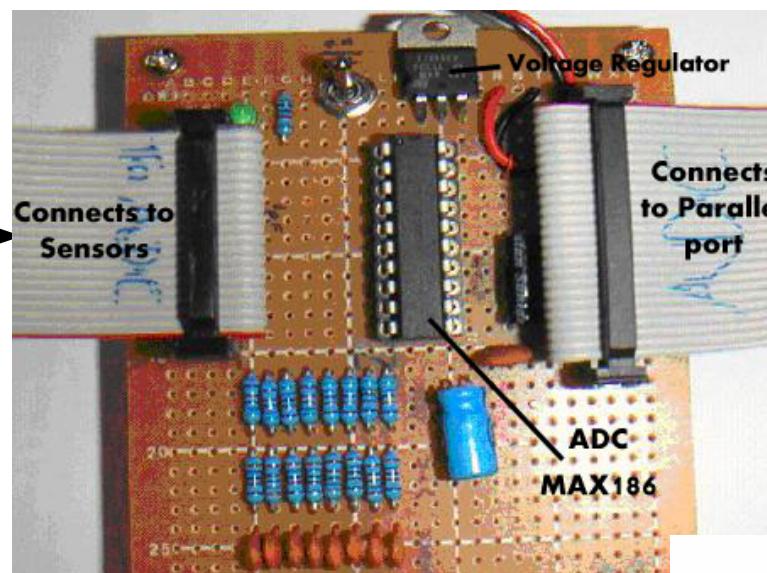

$N(T)$




$N$  is a function of  $T$   
 $T$  is a function of  $N$   
Computer can calculate  $T$


# A system: temperature measurement

Sensor      Volt. divider ADC

Temperature → Resistance → Volt → Number

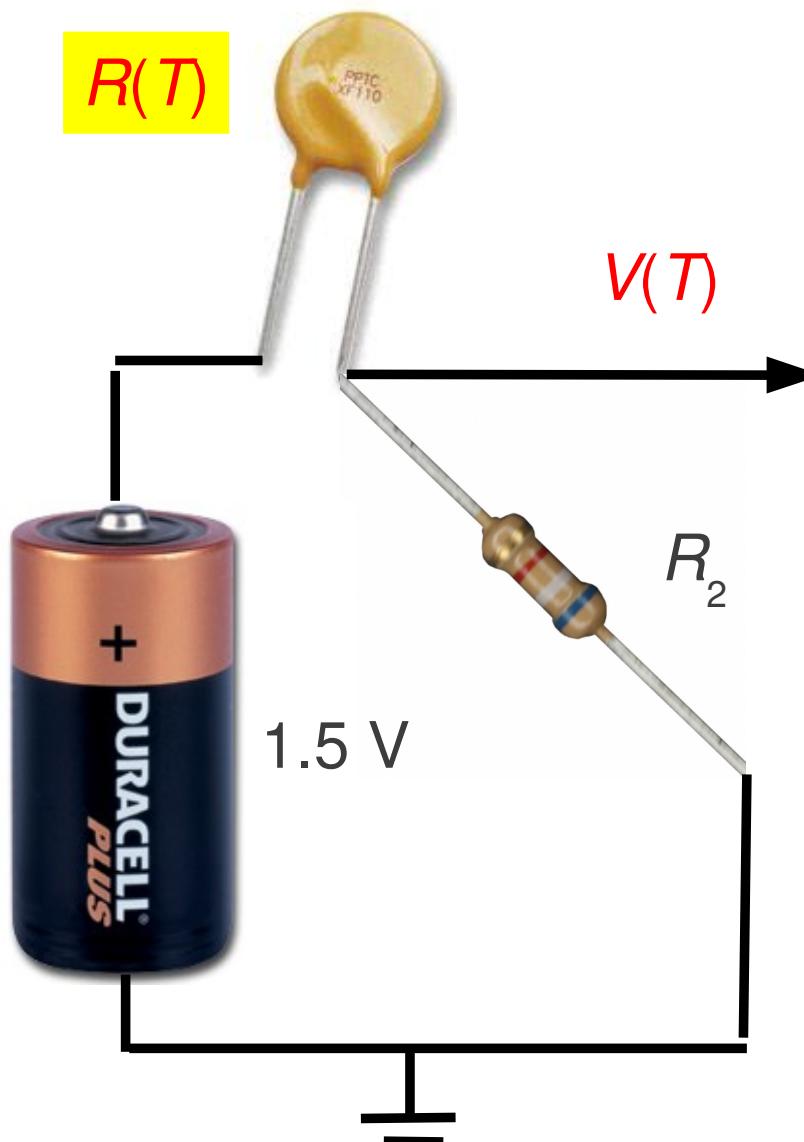

ADC:

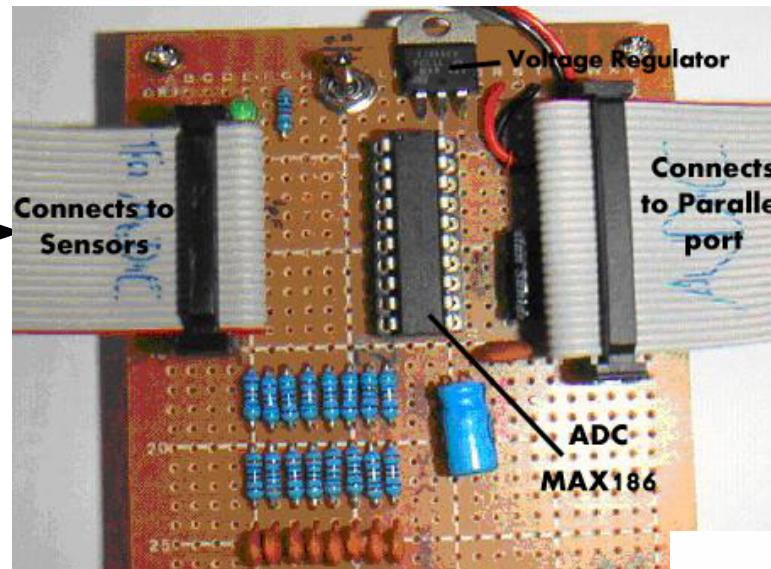


$N(T)$




$N$  is a function of  $T$   
 $T$  is a function of  $N$   
Computer can calculate  $T$

# A system: PID control of temperature

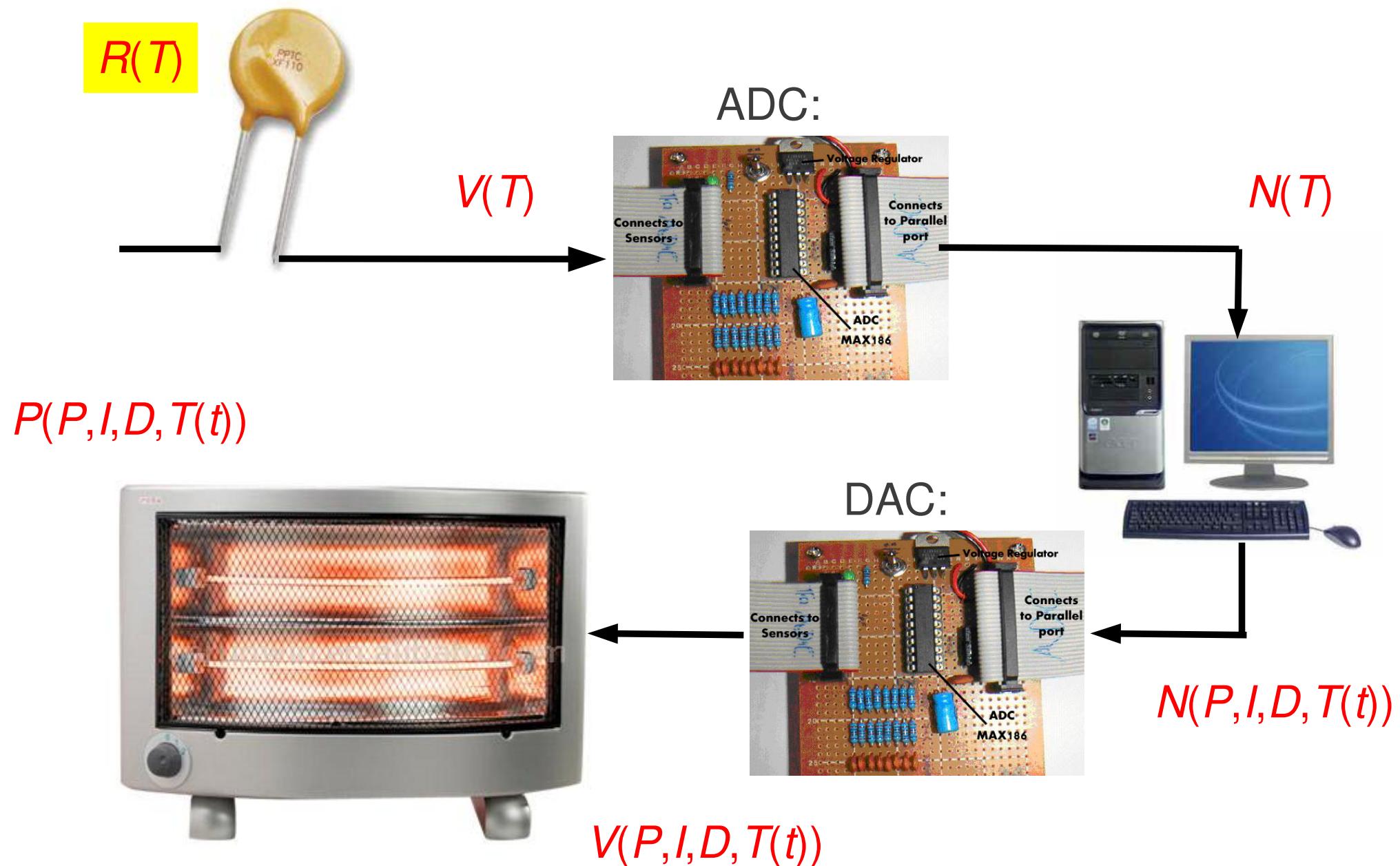
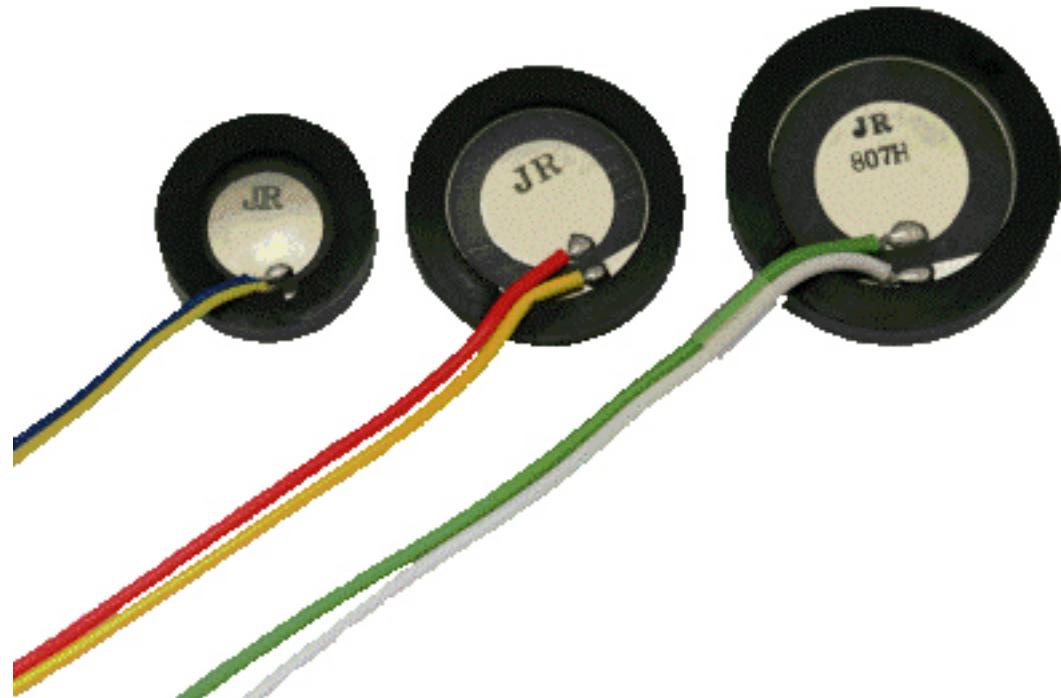
# Parameters of transducers

What are important parameters of transducers?




*Piezoelectric acoustic sensors*


# Parameters of transducers

- Price
- Transfer function (ex.  $V(T)$ )
- Sensitivity (ex.  $dV/dT$ )
- Offset
- Selectivity
- Linearity
- Range
- Accuracy
- Reproducibility/precision, (analog) resolution
- (Digital) resolution
- Shelf life & operational life
- Speed
- Durability
- Interference
- S/N Noise
- Ease of operation /maintenance
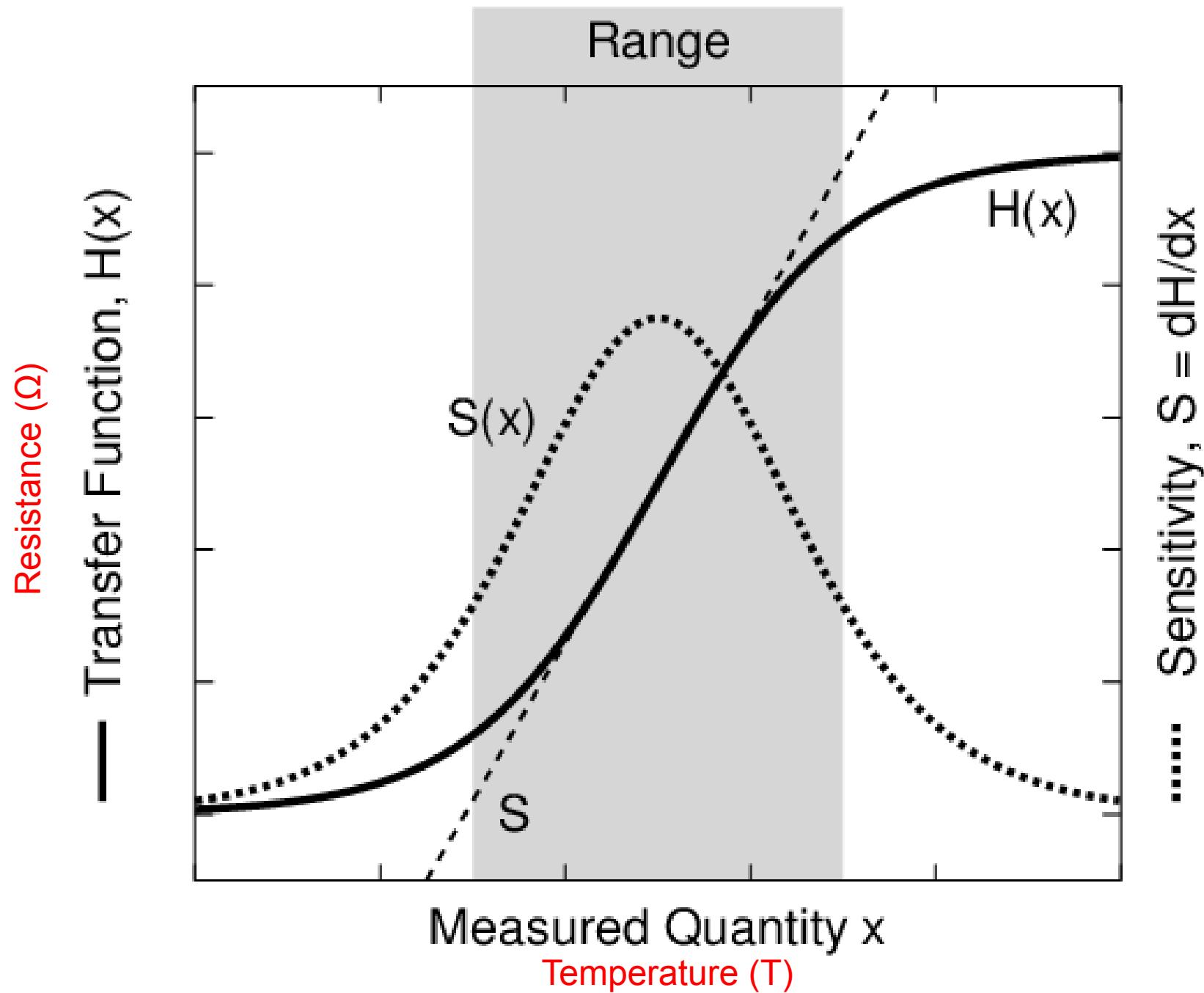
# Transfer function, sensitivity, linearity & range



# Resolution, Accuracy & Precision

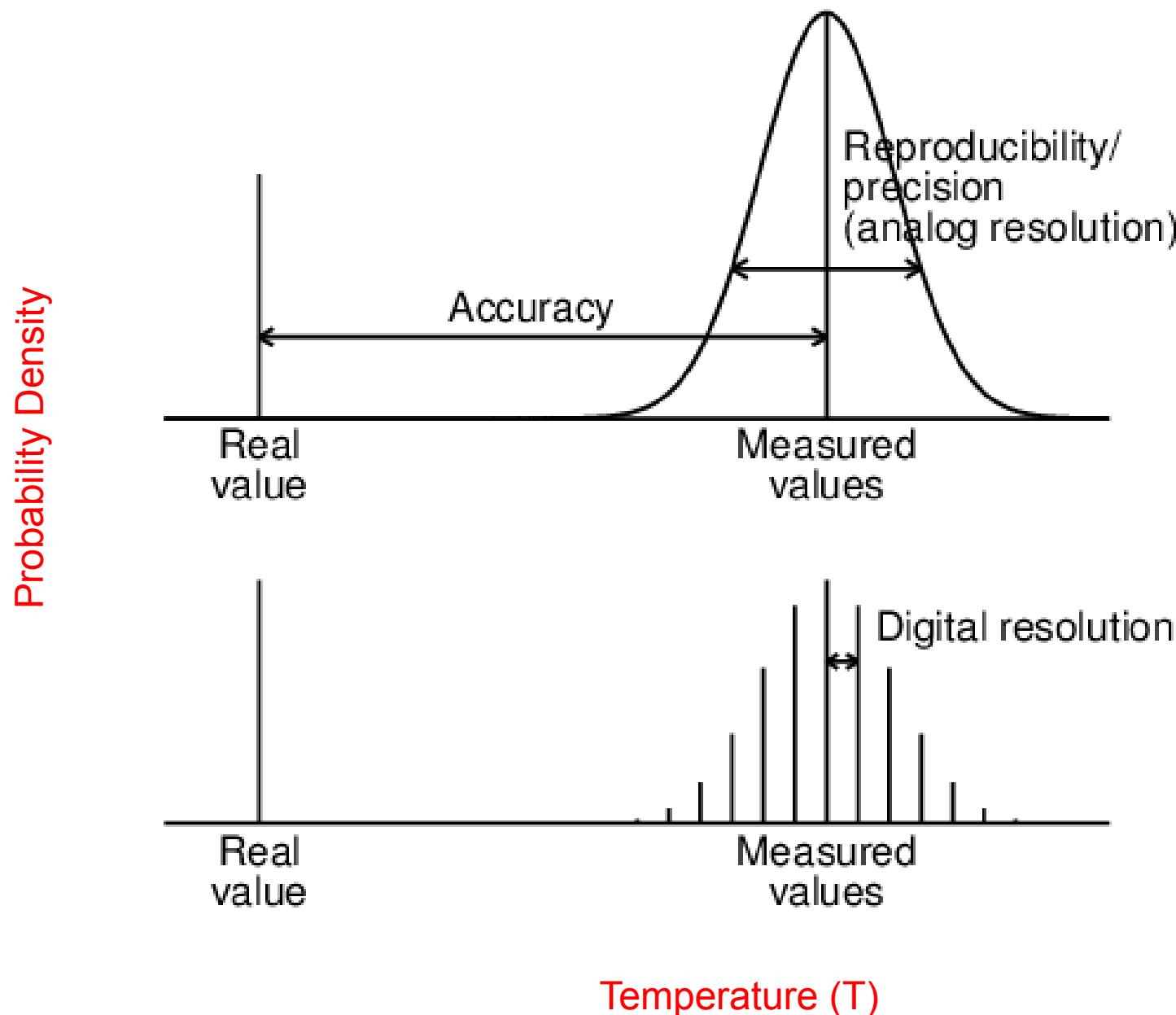


# Examples: Pissing sensor



2 transducers:

IR light source (LED)

IR light detector (photo-transistor)

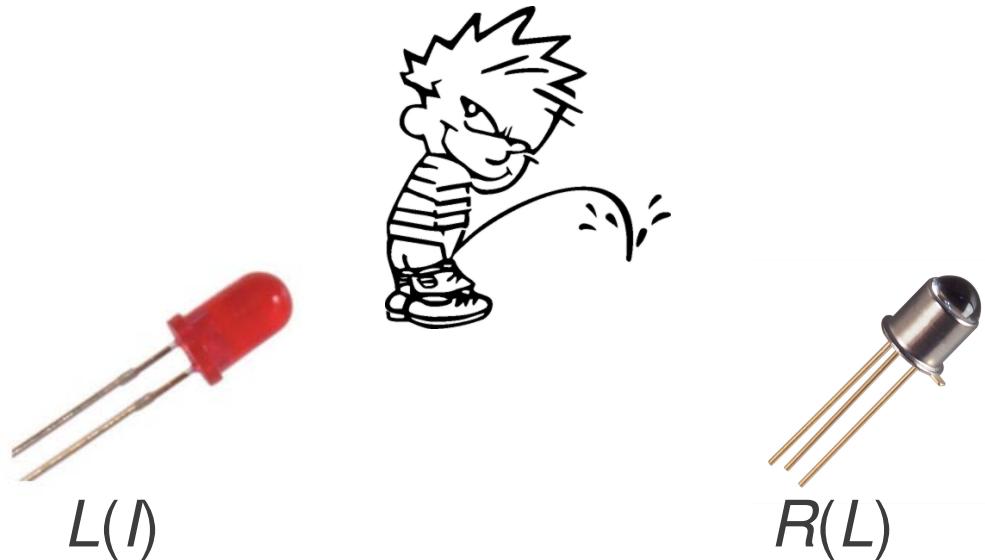

(Actuator) LED emits light. Person modulates light. Photo-transistor sensor's current depends on light intensity.

# Examples: Parking sensors



Speakers /  
microphones

Speakers emit (ultra)sound. Objects reflect sound. Sensor microphones detect sound. Processor calculates time difference and (thus) distance