

7/II/2011

Question 1) See lecture notes

Question 2) When a signal arrives at V_i , the transistor Q is conducting, shorting TRR and TRJ (x) to ground. The capacitor instantaneously discharges. This stays like this as long as V_i is high. The moment V_i is 'released', the transistor stops conducting and the capacitor starts charging

$$V_x(t=0) = 0 \quad \text{because } C \text{ begins discharged}$$

$$V_x(t=\infty) = V_{cc} \quad \text{because then } I=0$$

$$\tau = RC$$

$$V_x(t) = V_{cc} \left(1 - \exp(-t/RC) \right)$$

When this overtakes $1/3 V_{cc}$ nothing happens

(second opamp goes from $+V_{cc}$ to 0, without effect)

When it overtakes $2/3 V_{cc}$ the first opamp commutates.


This happens at

$$V_{cc} \left(1 - \exp(-t/RC) \right) = 2/3 V_{cc}$$

$$\text{thus } t = RC \ln(3).$$

The output of the flip flop is reset.

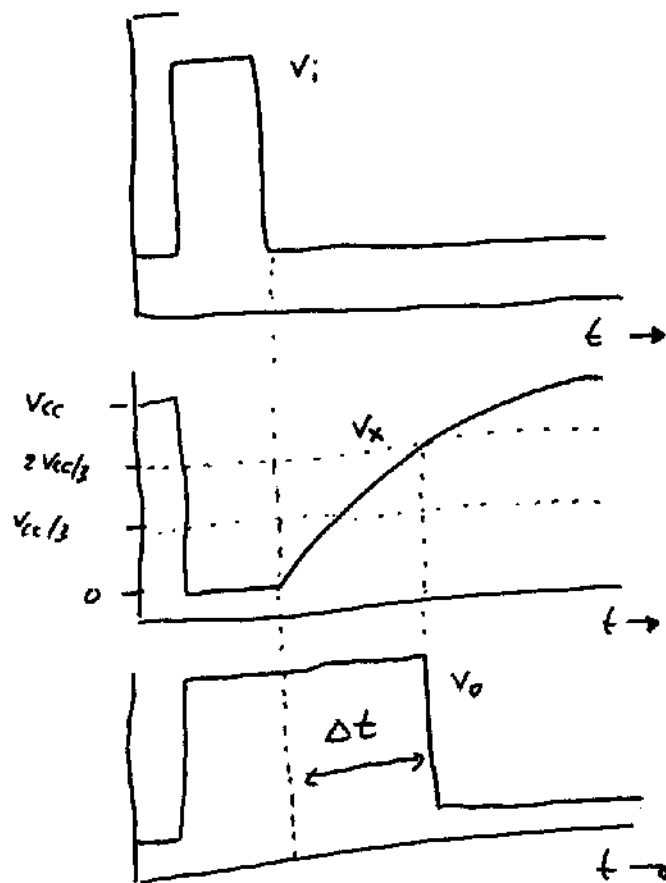Conclusion: after a time $\Delta t = RC \ln(3)$ after the input went low again, the output goes low.



$$b) RC \ln(3) = 10^{-3} \text{ s}$$

$$\text{ex. } C = 1 \mu\text{F} \Rightarrow R = 910 \Omega$$

Question 3)

$$a) f = \frac{\sqrt{\gamma \rho}}{2M}$$

$$f = 5 \times 10^6 \text{ Hz}$$

$$\gamma = 2.947 \times 10^{10} \text{ kg/m}^2 \text{ s}^2$$

$$\rho = 2.648 \times 10^3 \text{ kg/m}^3$$

$$\Rightarrow M = \frac{\sqrt{\gamma \rho}}{2f} = 0.883 \text{ kg/m}^2$$

$$M = \frac{m}{A} \Rightarrow m = MA$$

$$A = \pi \left(\frac{2.5 \times 10^{-3}}{2} \right)^2 = 4.9 \times 10^{-9} \text{ m}^2 \quad \left. \vphantom{A} \right\} m = 4.33 \times 10^{-4} \text{ kg}$$

$\Delta f = 1 \text{ Hz}$. repeat calculations for $f = 4.99999 \text{ MHz}$

or


$$\Delta m = \frac{\Delta f}{df/dm} \quad \frac{df}{dm} = \frac{df}{dM} \frac{dM}{dm} = - \frac{\sqrt{\gamma \rho}}{2M^2} \cdot \frac{1}{A} = - \frac{f}{m}$$

$$\Delta m = \frac{1 \text{ Hz}}{5 \text{ MHz}} / 4.33 \times 10^{-9} \text{ kg} = 8.7 \times 10^{-11} \text{ kg}$$


b) see lecture notes

Question 4)

Two-bit DAC

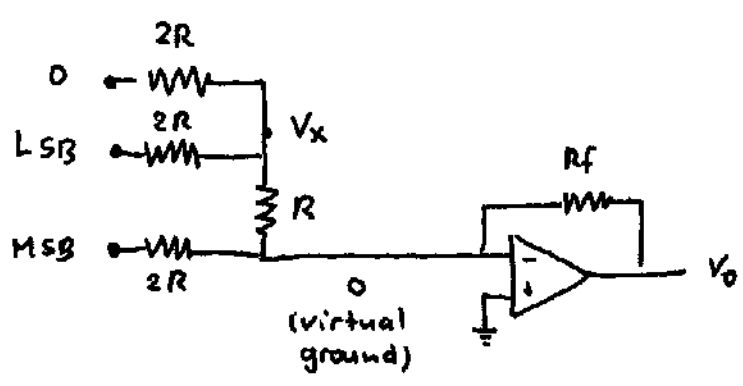

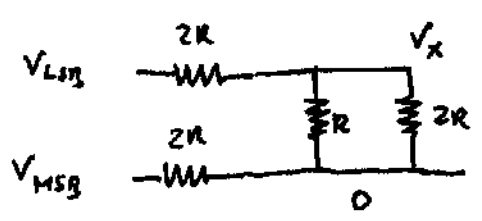
To find V_x we can make equivalent circuit:



$$V_x = V_{LSB} \times \frac{R // 2R}{R // 2R + 2R} = \frac{1}{4} V_{LSB}$$

$(R // 2R = \frac{2}{3} R)$

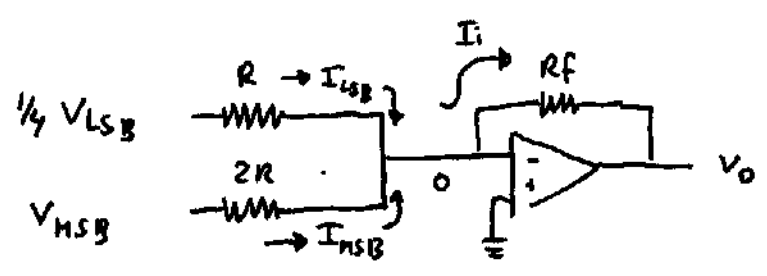So we have the following circuit (effectively):



This is a normal standard 'adder'

$$I_{LSB} = (1/4 V_{LSB} - 0) / R = \frac{V_{LSB}}{4R}$$

$$I_{MSB} = (V_{MSB} - 0) / 2R = \frac{V_{MSB}}{2R} +$$

$$I_i = I_{LSB} + I_{MSB} = \frac{1}{2R} (V_{MSB} + \frac{1}{2} V_{LSB})$$

$$V_o = 0 - I_i R_f$$

$$= - \frac{R_f}{2R} (V_{MSB} + \frac{1}{2} V_{LSB})$$

For example
 $R = 1 \text{ k}\Omega$, $R_f = 2 \text{ k}\Omega$

#n	MSB	LSB	V_{MSB}	V_{LSB}	V_o
0	0	0	0	0	0
1	0	1	0	-1V	-0.5V
2	1	0	-1V	0	-1.0V
3	1	1	-1V	-1V	-1.5V


$$V_o = (-0.5 \text{ V}) \times \#n \quad \text{DAC!}$$

b) see lecture notes

Question 5)

- a) Saturation? no, then $V_p = V_n$
 $I_{in} = \infty$ (no current goes into entrances)
 $I_{out} = 0$ (can supply any current necessary to maintain)

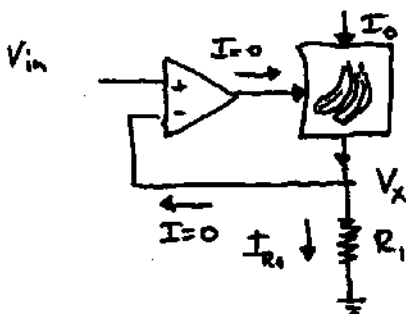- b) Because the MOS-FET draws no current, I_o must be equal to I_{R_1} . There is nowhere any point where current can be coming from or going to. We might even have connected a bunch of bananas; it would make no difference !!!



I_o must be I_{R_1} !!

But $(V_p = V_n)$: $V_x = V_{in}$


$$\text{thus } I_{R_1} = \frac{V_{in}}{R_1} \implies$$

$$I_o = \frac{V_{in}}{R_1}$$



Question 6) see lecture notes.

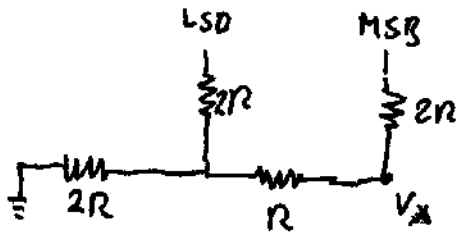Question 4) alternative

2-bit DAC (right version with voltage follower)



=> Superposition principle

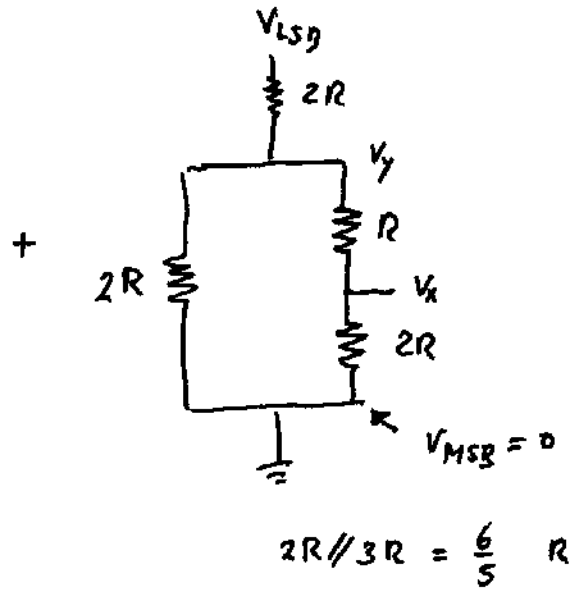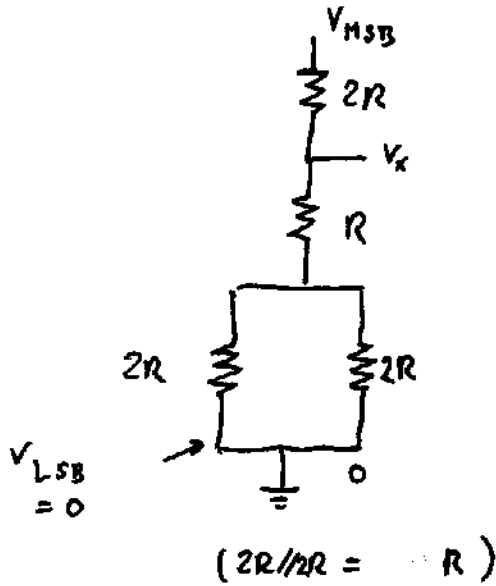

$$V_x = V_{MSB} \times \frac{2R}{2R + 2R}$$

$$= \frac{1}{2} V_{MSB}$$

$$V_y = \frac{\frac{6}{5} R}{\frac{6}{5} R + \frac{10}{3} R} V_{LSD} = \frac{6}{16} V_{LSD}$$

$$V_x = \frac{2R}{2R + R} V_y = \frac{2}{3} V_y = \frac{1}{4} V_{LSD}$$

$$V_x = \frac{1}{2} V_{MSB} + \frac{1}{4} V_{LSD}$$

$$V_0 = \frac{1}{2} V_{MSB} + \frac{1}{4} V_{LSD} \quad (\text{voltage follower})$$

#n	MSB	LSD	V _{MSB}	V _{LSD}	V ₀
0	0	0	0	0	0
1	0	1	0	1V	0.25 V
2	1	0	1V	0	0.5 V
3	1	1	1V	1V	0.75 V

$$V_0 = (0.25 V) \times \#n$$