
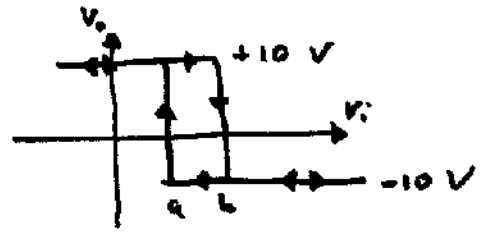


Solution Exam Instrumentation

9/07/2008 16:30

① see lecture notes

②

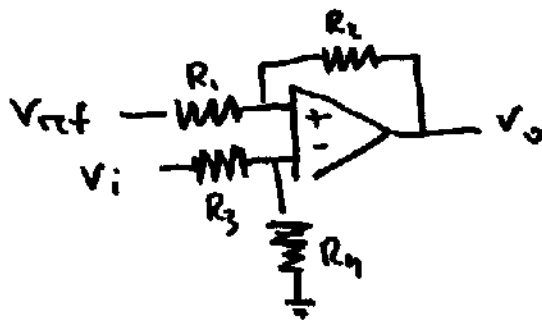

a) Type I, because for $v_i = -\infty$; $V_o = +V_{cc}$
and for $v_i = +\infty$: $V_o = -V_{cc}$

$$b) \quad \beta_1 = R_1 / (R_1 + R_2)$$

$$\quad \beta_2 = R_4 / (R_3 + R_4)$$

$$V_p = \beta_1 V_o + (1 - \beta_1) V_{ref}$$

$$V_n = \beta_2 V_i$$

$$a: \quad V_o = -10, \quad v_i = a, \quad V_n = V_p$$

$$-10 \beta_1 + (1 - \beta_1) V_{ref} = a \beta_2 \quad (I)$$

$$b: \quad V_o = +10, \quad v_i = b, \quad V_n = V_p$$

$$10 \beta_1 + (1 - \beta_1) V_{ref} = b \beta_2 \quad (II)$$

$$II - I: \quad 20 \beta_1 = (b - a) \beta_2$$

In this case $b = 2, a = 1 \Rightarrow$

$$20 \beta_1 = \beta_2$$

in II

$$10 \beta_1 + (1 - \beta_1) V_{ref} = 40 \beta_1$$

$$V_{ref} = 30 \frac{\beta_1}{1-\beta_1}$$

$$(30 + V_{ref}) \beta_1 = V_{ref}$$

$$\beta_1 = \frac{V_{ref}}{30 + V_{ref}}$$

• For example

$$V_{ref} = +5V$$

$$\beta_1 = \frac{5}{35} = \frac{1}{7}$$

$$\beta_2 = 20 \beta_1 = \frac{20}{7} \quad (\text{not possible, } \beta_2 \leq 1)$$

③

a) see lecture notes

$$\frac{dR/R}{dL/L} = 1 + 2\alpha + \frac{d\epsilon/\epsilon}{dL/L}$$

b) $\alpha = 0.33$, $\frac{d\epsilon/\epsilon}{dL/L} = 0$

$dL/L = 1\% \Rightarrow$

$$\frac{dR/R}{1\%} = 1 + 2 \cdot 0.33$$


$dR/R = 1.66\%$, $R = 1k\Omega$

$\Rightarrow dR = 17\Omega$

$R = 1017\Omega$

c) $+1\% \rightarrow R = 1017\Omega$

$-1\% \rightarrow R = 983\Omega$

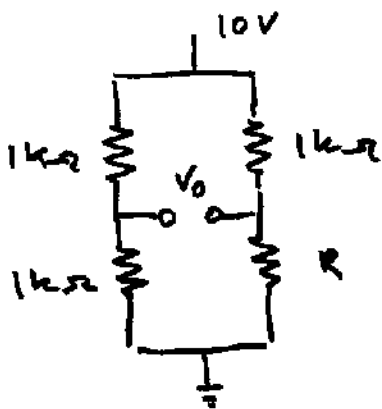

$$V_o = 5V - 10 \cdot \frac{R}{R + 1k\Omega}$$

min = $5 - 4.9571V$

= $0.0429V$


max = $5 - 5.0421V$ } $\Delta V \approx 85mV$

= $-0.0421V$

We need an amplifier that has a gain of

$\frac{5000}{85}$ and an offset so that for $V = -0.0421V$

the output is zero.

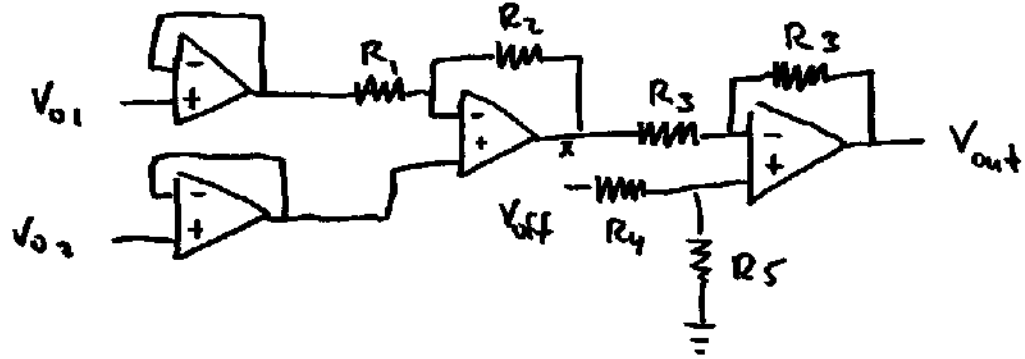

to put $r_{in} = \infty$ diff. amplifier

$$V_x = \frac{R_2}{R_1} (V_{02} - V_{01})$$

$$\frac{R_2}{R_1} = \frac{5000}{85}, \text{ ex.}$$

50 k Ω & 850 Ω

-1 X amplifier plus offset ($r_{out} = 0$)

$$V_{out} = -V_x + \beta V_{off}$$


βV_{off} should be 2.5 V

d) The ADC has 10 bit, so the number of levels is $2^{10} = 1024$.
The sensor and system are linear for (such) small perturbations.

$$-1\% - +2\% = 2\% = 2 \text{ mm}$$

$$\text{resolution is } \frac{2 \text{ mm}}{1024} \sim 2 \mu\text{m}$$


4

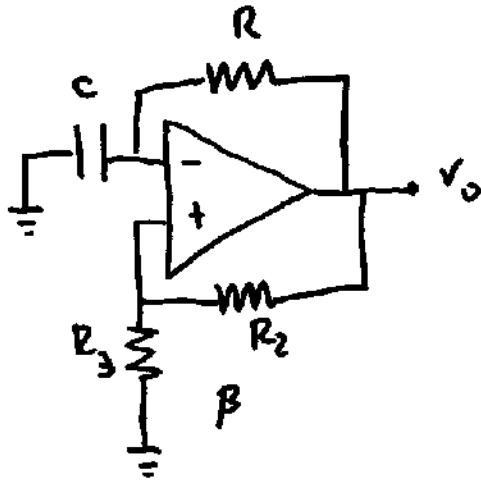

Imagine : $V_o = +V_{cc} \Rightarrow V_p = +\beta V_{cc}$, C is

empty $\Rightarrow \Delta V_c = 0 \Rightarrow V_n = 0 \Rightarrow$

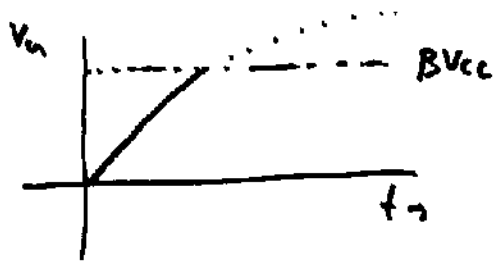
$\Delta V_R = V_{cc} \Rightarrow I_R = \frac{+V_{cc}}{R}$. This charges



C and ΔV_c will increase, until V_n

becomes larger than $+\beta V_{cc}$

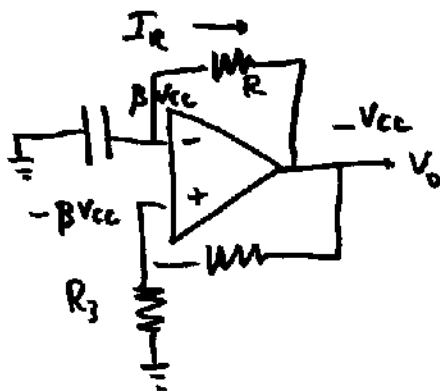At this moment the op amp commutes and we have the following situation



We set the time at $t=0$.

$I_R = \frac{\beta V_{cc} - (-V_{cc})}{R}$ will

discharge the capacitor with a characteristic time


$\tau = RC$. (note that the

charging /discharging current is not constant and the system has exponential behavior)

The discharging continues until $V_n < V_p$,
 thus $V_n < -\beta V_{cc}$.

Thus, for V_n we have

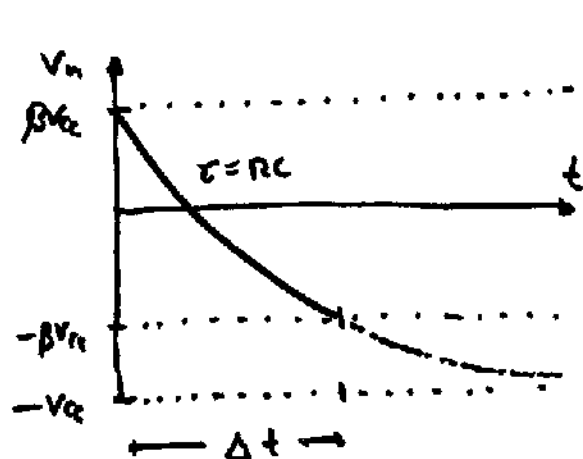- $V_n(t=0) = \beta V_{cc}$
- $V_n(t=\infty) = -V_{cc}$
- commutes at $V_n = -\beta V_{cc}$
- $\tau = RC$



$$V_n(t) = -V_{cc} + (\beta + 1)V_{cc} \exp(-t/RC)$$


commutes at t :

$$-\beta V_{cc} = -V_{cc} + (\beta + 1)V_{cc} \exp(-t/RC)$$

\Rightarrow

$$\Delta t = RC \ln\left(\frac{1+\beta}{1-\beta}\right)$$

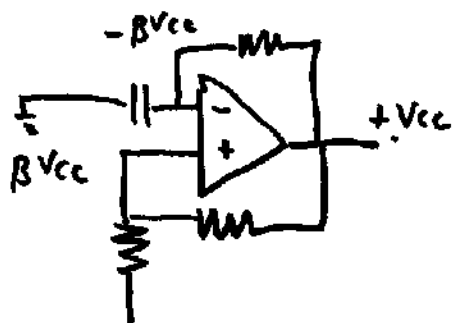At this moment we have the following situation:



Again we set $t=0$.
 The current through R is discharging / charging the capacitor with a time


constant equal to $\tau = RC$.

The charging continues until $V_n > V_p$,

thus $V_n > +\beta V_{cc}$.

thus for V_n we have

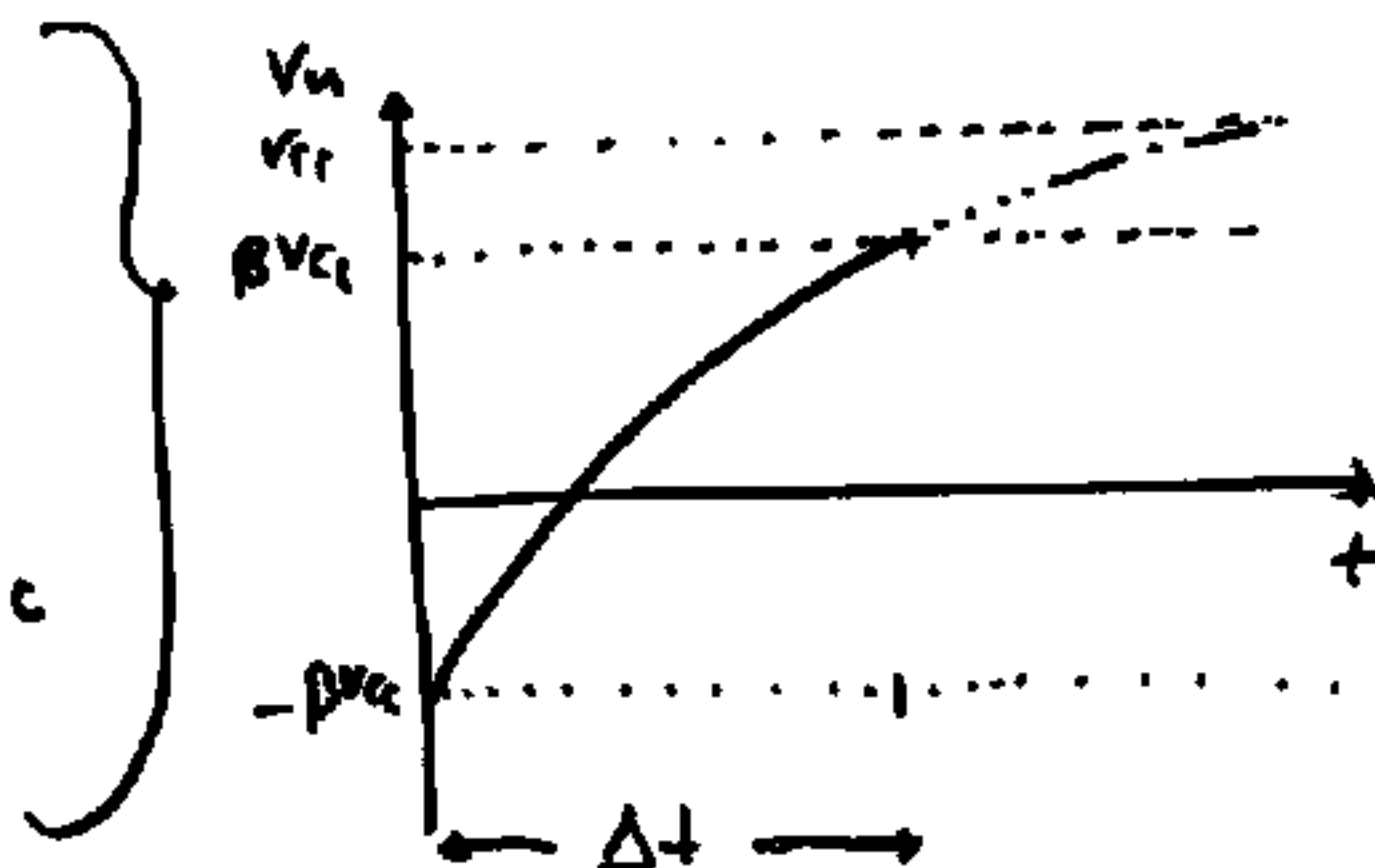- $V_n(t=0) = -\beta V_{cc}$
- $V_n(t=\infty) = V_{cc}$
- commutes at $V_n = +\beta V_{cc}$
- $\tau = RC$



$$V_n(t) = V_{cc} - (\beta+1)V_{cc} \exp(-t/RC)$$

commutes when

$$\beta V_{cc} = V_{cc} - (\beta+1)V_{cc} \exp(-t/RC)$$

\Rightarrow

$$\Delta t = RC \ln\left(\frac{1+\beta}{1-\beta}\right) \quad (\text{equal to other})$$

The frequency is thus

$$f = \frac{1}{2\Delta t} = \frac{1}{2RC \ln\left(\frac{1+\beta}{1-\beta}\right)}$$

b) $f = 10 \text{ kHz}$

$$\beta = \frac{11}{3} \Rightarrow \ln\left(\frac{1+\beta}{1-\beta}\right) = \ln\left(\frac{4/3}{2/3}\right) = \ln 2$$


$$C = 1 \text{ nF}$$

$$\Rightarrow R = \frac{1}{10 \text{ kHz} \cdot 2 \cdot 1 \text{ nF} \cdot \ln 2} = 72 \text{ k} \quad 7$$

⑤ a) op-amp 2 is a tension follower,

thus at the v_{p2} we have v_o


At op-amp 1 we thus have

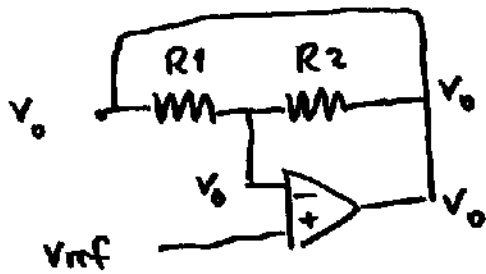

At v_n we always have
 v_o (because $r_{in} = \infty$)

$$v_n = v_p = v_{ref} \Rightarrow v_o = v_{ref}$$

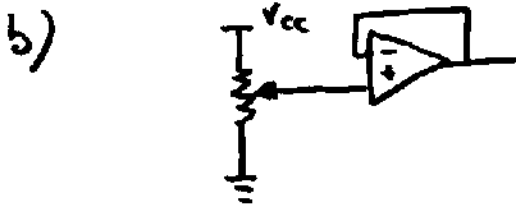This circuit is just a fancy tension follower



c) See subent a

⑥ A solar panel does not have information
at its output (when used only as a power supply)