

Electronic Instrumentation

Re exam 15/2/2011

Question 1

see lecture notes


Question 2

a) $A = \infty \Rightarrow V_p = V_n$ or saturation

$r_{in} = \infty$


$r_{out} = 0$

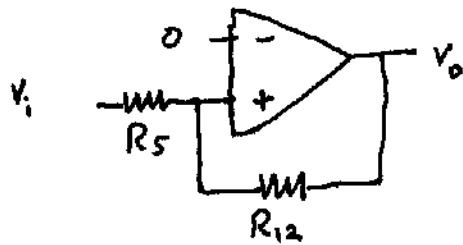b) The left opamp is configured as a comparator with hysteresis, (positive feedback)



$R_{12} = R_1 + R_2$

$\beta = \frac{R_5}{R_5 + R_{12}}$

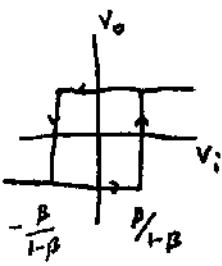

$V_o = -V_{cc} , \quad V_p = -V_{cc} \beta + V_i (1 - \beta)$

commutation : $V_p = V_n = 0 \Rightarrow -\beta V_{cc} + V_i (1 - \beta) = 0$

$\Rightarrow V_i = \frac{\beta}{1 - \beta} V_{cc}$


$V_o = +V_{cc} , \quad V_p = +V_{cc} \beta + V_i (1 - \beta)$

commutation : $V_p = V_n = 0 \Rightarrow \beta V_{cc} + V_i (1 - \beta) = 0$

$\Rightarrow V_i = -\frac{\beta}{1 - \beta} V_{cc}$

The right opamp is configured as an ~~comparator~~ integrator, see


lecture notes

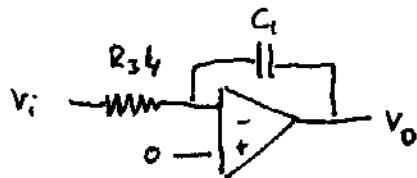

$V_o = -\frac{1}{R_{34} C_1} \int V_i(t) dt + V_{og}$

Combining the two circuits results in an oscillator

Imagine output 2 is high (+Vcc).

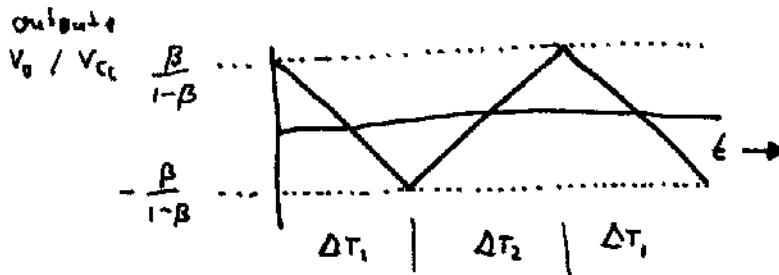


amplitude = $\frac{\beta}{1-\beta} V_{cc}$

$$= \frac{R_5}{R_5 + R_{12}} V_{cc} = \frac{R_5}{R_{12}} V_{cc}$$

$$\Delta T_1: V_o = \frac{\beta}{1-\beta} V_{cc} - \frac{V_{cc}}{R_{34} C_1} t = -\frac{\beta}{1-\beta} V_{cc}$$
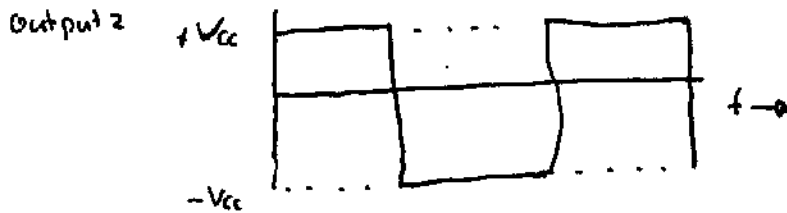
$$\Delta T_1 = \Delta T_2 \Rightarrow t = \frac{2R_5}{R_{12}} \times R_{34} C_1 \quad \Delta T_1 + \Delta T_2 = \Delta T =$$



$$\frac{4R_5}{R_{12}} \times R_{34} C_1$$

c) 1V and 1 kHz : example

$$R_5 = 10 \text{ k}\Omega, \quad V_{cc} = 10 \text{ V}$$

$$R_1 = 10 \text{ k}\Omega, \quad R_2 = 90 \text{ k}\Omega$$

$$C_1 = 1 \text{ }\mu\text{F}, \quad R_{34} = 2.5 \text{ k}\Omega$$


$$(R_4 = 2.2 \text{ k}\Omega, \quad R_3 = 0.3 \text{ k}\Omega)$$

Question 3

See lecture notes (it is for removing offset)

Question 4

similar to example in lecture notes.

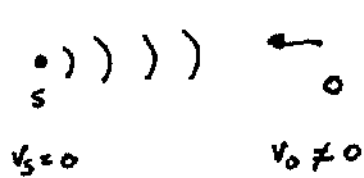


$$f_o = \left(\frac{v+v_o}{v}\right) f_s$$

reflected $f'_s = f_o$

$$f_r = \left(\frac{v}{v-v_o}\right) f'_s = \left(\frac{v+v_o}{v-v_o}\right) f_s$$
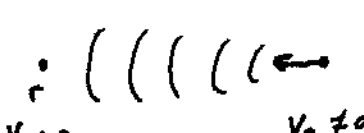
$$\approx \left(\frac{v+2v_o}{v}\right) f_s = \left(1 + 2\frac{v_o}{v}\right) f_s$$




$v = 300 \text{ m/s}$, $f_s = 40 \text{ kHz}$

$f_r - f_s = (1 + 2 \frac{v_0}{v}) f_s - f_s = \frac{2 v_0}{v} f_s < 10 \text{ Hz}$

$v_0 < \frac{(10 \text{ Hz}) \times v}{2 f_s}$

$< \frac{(10 \text{ Hz}) \times (300 \text{ m/s})}{2 \times (40 \text{ kHz})} = 3.75 \text{ cm/s}$

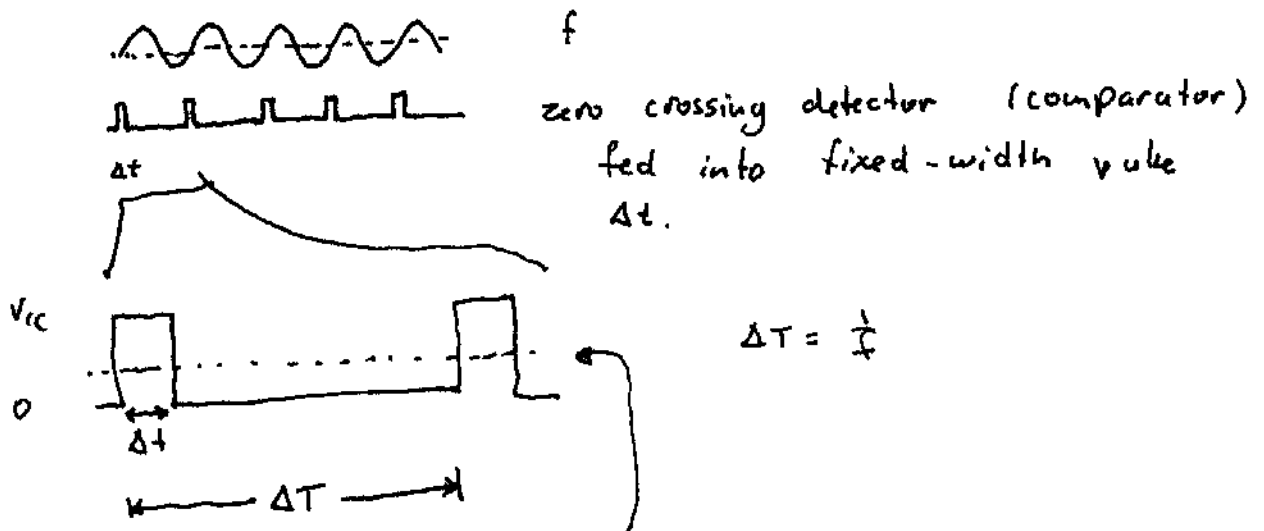
- Frequency can be converted into voltage by a PLL (phase-locked loop) or by a NESSS pulse generator



RC (low pass) filter. Average:

$V(f) = V_{cc} \frac{\Delta t}{\Delta T} = \Delta t V_{cc} f$

Question 5

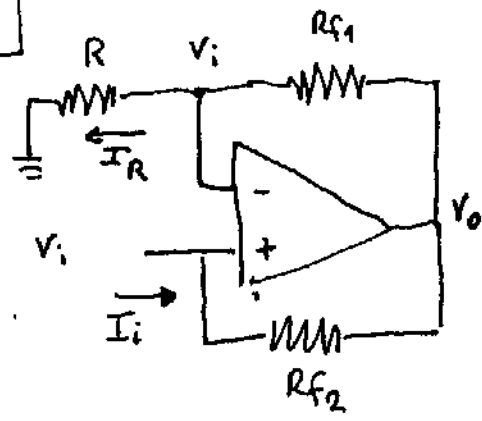


$v_p = v_n = v_i$

$\Rightarrow I_R = \frac{v_i}{R}$

This current cannot come from v_n (input of opamp). Must come from R_{f1}

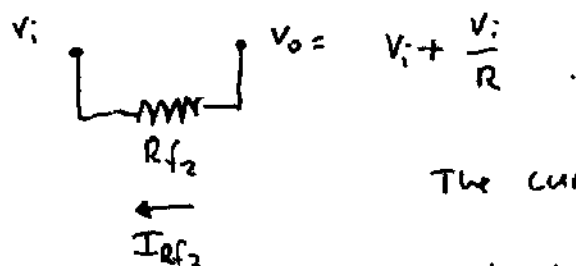That makes V_o equal to $V_i + I_{R_f} = V_i + \frac{V_i}{R} R_f$




The current I_{R_f} is then

$$I_{R_f} = \frac{V_o - V_i}{R_f} = \frac{\left(V_i + \frac{V_i}{R} R_f\right) - V_i}{R_f} = \frac{V_i}{R}$$

This current must come from outside (V_i) because input resistance of V_p of op amp is infinite.

Thus

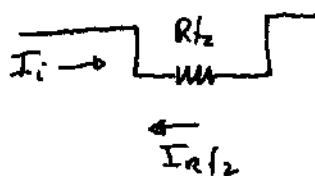

$$I_i = -I_{R_f} = -\frac{V_i}{R}$$

Ohm's Law: $R_i = \frac{V_i}{I_i} = \frac{V_i}{-V_i/R} = -R$

Question 6

$$a) R(L, r, \rho) = \frac{\rho L}{\pi r^2} = \frac{\rho(L)}{\pi r(L)^2}$$

$$\frac{dR}{dL} = \frac{\rho}{\pi r^2} \frac{dL}{dL} = \frac{2\rho L}{\pi r^3} \frac{dr}{dL} + \frac{L}{\pi r^2} \frac{d\rho}{dL}$$

$$K \equiv \frac{dR/R}{dL/L} = \frac{dR}{dL} \cdot \frac{L}{R} = \frac{dR}{dL} \cdot \frac{\pi r^2}{\rho}$$

$$= \frac{\rho}{\pi r^2} \frac{dL}{dL} \cdot \frac{\pi r^2}{\rho} - \frac{2\rho L}{\pi r^3} \frac{dr}{dL} \cdot \frac{\pi r^2}{\rho} + \frac{L}{\pi r^2} \frac{d\rho}{dL} \cdot \frac{\pi r^2}{\rho}$$

$$= 1 - 2 \frac{L}{r} \frac{dr}{dL} + \frac{L}{\rho} \frac{d\rho}{dL} = 1 - 2 \frac{dr/r}{dL/L} + \frac{d\rho/\rho}{dL/L}$$

$$= 1 + 2\nu + \frac{d\rho/\rho}{\epsilon} \quad \text{q.e.d.}$$

$$b) \quad V = L \pi r^2 = L \pi r(L)^2$$

$$\frac{dV}{dL} = \pi r^2 \cdot \frac{dL}{dL} + 2\pi L r \frac{dr}{dL} = 0$$

divide by πr^2

$$1 + 2 \frac{L}{r} \cdot \frac{dr}{dL} = 0 \Rightarrow$$

$$\frac{dr/r}{dL/L} = -0.5 \Rightarrow \nu = +0.5$$

$$K = 1 + 2\nu = 2.0$$

$$c) \quad \frac{\Delta L}{L} = 1\% \Rightarrow \frac{\Delta R}{R} = K \frac{\Delta L}{L} = 2\%$$

$$R = 1 \text{ k}\Omega \Rightarrow \Delta R = 20 \Omega$$

$$R' = R + \Delta R = 1020 \Omega$$

d) us an extensometer, that is for example for measuring earthquakes.