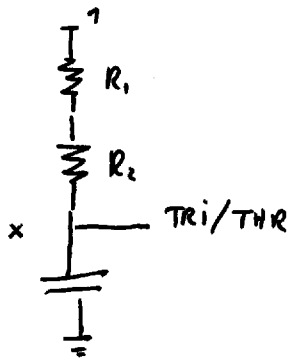


All voltages divided by V_{CC}
 $(\frac{2}{3} \Rightarrow \frac{2}{3} V_{CC}, \text{etc})$

Charging cycle (Q open circuit) \bar{Q} is low, $OUT = \text{high}$ (1)




note: no current enters in the opamps

← This is an RC circuit that shows exponential behavior

$t = \infty \Rightarrow V_x = 1$ (no current through R_1 and R_2)

$t = 0 \Rightarrow V_x = \frac{1}{3}$ (see note later)

$$\tau = (R_1 + R_2)C$$

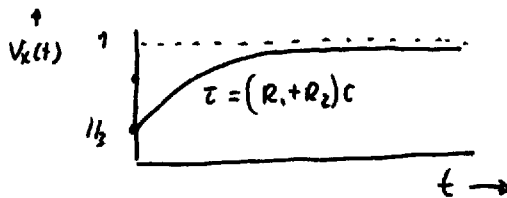


$$V_x(t) = 1 - \frac{2}{3} \exp(-t/\tau)$$

When V_x reaches $\frac{2}{3}$, the top op-amp (OA1) goes from low to high \uparrow . Or, in other words a reset of the flip flop F occurs, $OUT \downarrow$ and $\bar{Q} \uparrow$. Transistor Q opens, shorting point y to ground.

When does this occur? $V_x(t) = \frac{2}{3} \Rightarrow$


$$t_1 = (R_1 + R_2)C \ln 2$$

Now we have

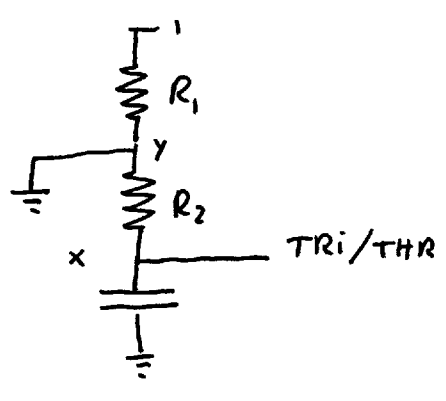

This is an RC circuit that shows exponential behavior

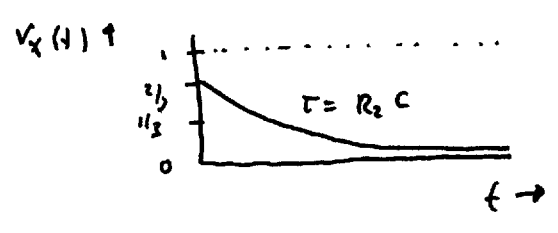
$t = \infty, V_x = 0$
 $t = 0, V_x = \frac{2}{3}$ (see prev. page)
 $\tau = R_2 C$ (R_1 does nothing!)



$V_x(t) = \frac{2}{3} \exp(-t/\tau)$

When V_x reaches $1/3$, the bottom op-amp (OA2) goes from low to high \uparrow . Or, in other words, a set of the flip-flop occurs, $OUT \uparrow, \bar{Q} \downarrow$. Transistor Q closes (open circuit), removing the ground from point y. When does this occur? $V_x(t) = 1/3 \Rightarrow$

$t_2 = R_2 C \ln 2$

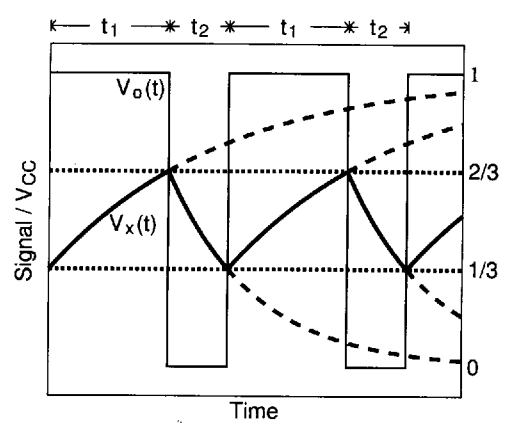

$T = t_1 + t_2 = C(R_1 + 2R_2) \ln 2$

$f = 1 \text{ kHz} \Rightarrow T = 1 \text{ ms}, C = 100 \text{ nF} \Rightarrow R_1 + 2R_2 = 10 \text{ k}\Omega$
 example $R_2 = 3.9 \text{ k}\Omega, R_1 = 2.2 \text{ k}\Omega$