

Electronic Instrumentation

Problem sheet: Wheatstone

2011/2012 module 2

P. Stallinga




MIEET 3º ano

Determine the temperature resolution of a system based on a thermistor in a voltage divider configuration (a) and a Wheatstone bridge configuration (b)


- The multimeter used has 4 digits scale. So, for instance, if the scale is 2 V, a typical reading is 1.346 V, so the resolution is 1 mV.
- Maximum scale of multimeter: 200 V.
- Minimum scale of multimeter: 20 mV.
- The thermistor has a response of $0.1\%/^{\circ}\text{C}$, meaning that the resistance changes 0.1% if the temperature changes 1°C , for instance from $10\text{ k}\Omega$ to $10.01\text{ k}\Omega$.

a)

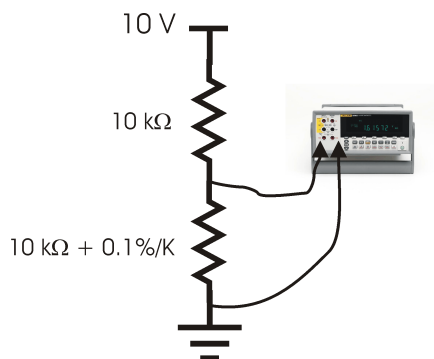

Voltage divider setup

b)

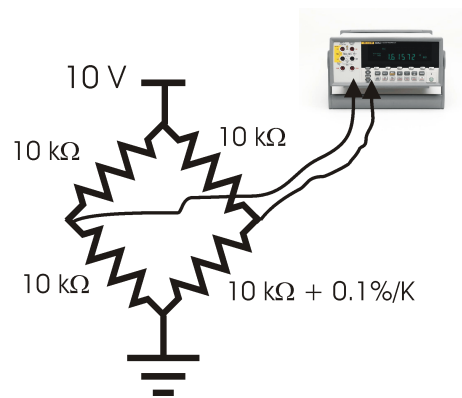

Wheatstone bridge setup