

Instrumentação Electrónica Sensor de temperatura

2011/2012 módulo 2
P. Stallinga



MIEET 3º ano

Develop a system to measure the temperature based on a diode.
The current through a diode is given by (Ebers-Moll)

$$I_D = I_s(T) [\exp(qV_D/nkT) - 1]$$

Suggestion: Connect the diode in series with a current source (or resistor) to guarantee a constant current.

- Determine the relation between T and V_D theoretically and experimentally.
- Determine the linearity of the system (defined as the range of temperatures where the deviation from linearity is less than 5%).
- Determine the sensitivity of the system ($V/^\circ\text{C}$)
- Determine the ideality factor n .

A warning LED has to light up when the temperatures is larger than 40°C .



====> SYSTEM ====>

