

Instrumentação Electrónica

Oscilador NE555

2011/2012 módulo 2
P. Stallingsa

- Design and implement a circuit, based on an NE555 timer IC, hat oscillates at 1 kHz.
- Calculate and determine the 'duty cycle' of the wave (% of time at $V_o = V_{cc}$).

